

1. a) Label node after  $R_1$  as A  
and node after  $C_2$  as B

$$Z_1 = \frac{1}{j\omega C_1} \quad Z_2 = \frac{1}{j\omega C_2}$$

17 pt

3 digits

Impedance seen from node A

$$Z_f = Z_2 + R_2 = \frac{1}{j\omega C_2} + R_2$$

Shunt at node A

$$Z_p = Z_1 \parallel Z_f = \frac{Z_f + Z_1}{Z_f + Z_1}$$

3 pt

$$V_A = V_i \frac{Z_p}{R_1 + Z_p}$$

$$V_B = V_o = V_A \frac{R_2}{R_2 + Z_2}$$

4 pt

$$H(\omega) = \frac{R_2}{R_2 + \frac{1}{j\omega C_2}} \cdot \frac{\frac{1}{j\omega C_1} \left( R_2 + \frac{1}{j\omega C_2} \right)}{\left[ \frac{1}{j\omega C_1} + \left( R_2 + \frac{1}{j\omega C_2} \right) \right] \left[ R_1 + \left( \frac{1}{j\omega C_1} \parallel R_2 + \frac{1}{j\omega C_2} \right) \right]}$$

7

$$H(\omega) = \frac{j\omega C_2 R_2}{1 + j\omega(R_1 C_1 + R_1 C_2 + R_2 C_2) - \omega^2 R_2 C_1 R_2}$$

5) Magnitude and phase plots



17 pt

3 digits

$$\omega_{c1} = \frac{1}{1 \cdot 10^{-6}} = 10^6 \text{ rad/s}$$

$$\omega_{c2} = \frac{1}{R_2 C_2} = 2.5 \cdot 10^5 \text{ rad/s}$$

8 pt

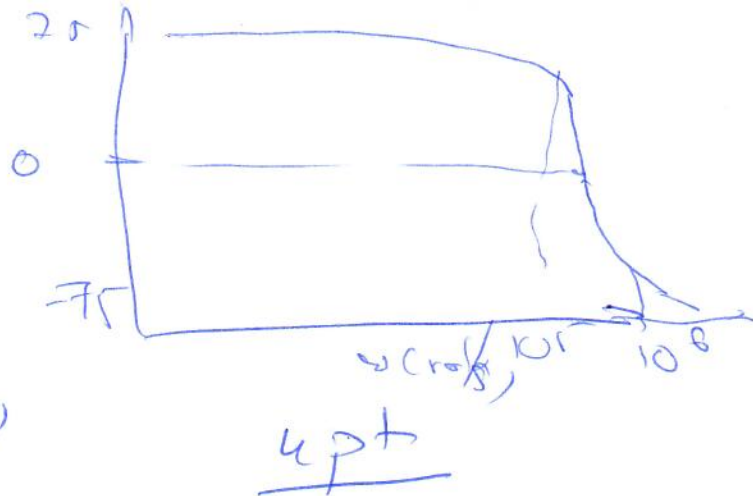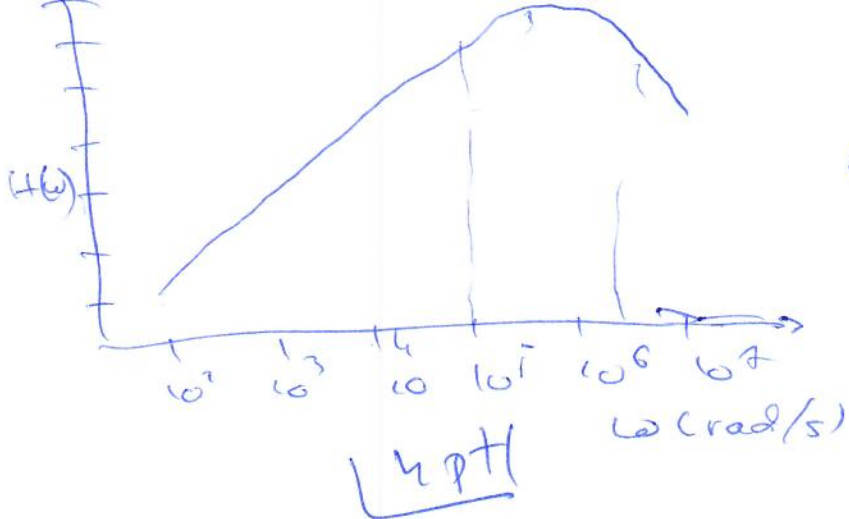

c) cut off and pole/slope

first pole  $\omega_c = \frac{1}{R_1 C_2} = 2.5 \times 10^5 \text{ rad/s}$  1.2pt  
3 types

$\omega \ll \omega_c \quad |H(j\omega)| \approx \text{const}$

$\omega \gg \omega_c \quad \text{slope } -20 \text{ dB/dec}$

$\omega \gg 10^6 \quad \text{slope } -40 \text{ dB/dec}$  (2pt)

[20]

1)  $Z_L = j\omega L \quad Z_C = \frac{1}{j\omega C} \quad Z_R = R$   
 $Z_{in} = Z_R \parallel Z_C = \frac{R}{1 + j\omega RC}$  (3pt)

Voltage divider (3pt)

$V_o = V_i \frac{Z_{in}}{Z_{in} + Z_L} \Rightarrow |H(j\omega)| = \frac{Z_{in}}{Z_{in} + Z_L}$

$H(j\omega) = \frac{R}{R + j\omega L - \omega^2 RC} \quad | \quad 2pt$

ii) freq at which  $H(\omega)$  is purely real

$$\boxed{5pt} \quad j\omega L - \omega^2 LC$$

imaginary part

16pt  
3 to 5/2

zero @  $\omega=0$  because  $L > 0$   
8pt

iii)

$Z_S \rightarrow j\infty$  open

$H(\omega) \rightarrow 0$

$Z_C \rightarrow 0$  short

4pt

12pt  
3 to 5/2  
at  $\omega=0$

$Z_C = j\omega L \rightarrow 0$  short

$Z_C \rightarrow \infty$  open 4pt

$$H(0) = \frac{R}{R} = 1$$

This filter rejects high freq 6pt

and passes DC Low  
pass