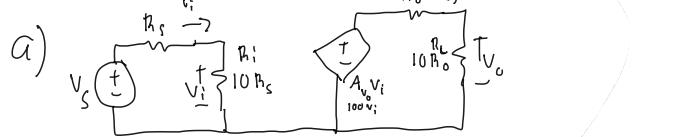


A1. For the circuit below where $A_{vo}=100 \text{ V/V}$, calculate voltage gain, v_o/v_s , for the following three conditions (express your answers both directly and in decibels):


- (a) $R_i=10R_s, R_L=10R_o$
- (b) $R_i=R_s, R_L=R_o$
- (c) $R_i=R_s/10, R_L=R_o/10$



$$\frac{V_o}{V_s} = 100 \left(\frac{10 R_s}{R_s + 10 R_s} \right) \left(\frac{10 R_o}{R_o + 10 R_o} \right)$$

$$\frac{V_o}{V_s} = 100 \left(\frac{10}{11} \right) \left(\frac{10}{11} \right)$$
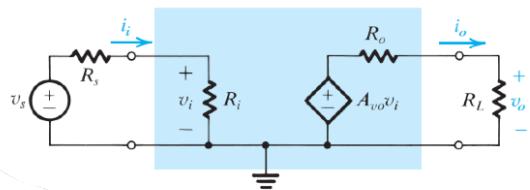
$$\boxed{\frac{V_o}{V_s} = 82.64 = 38.34 \text{ [dB]}}$$



$$v_i = V_s \left(\frac{R_i}{R_s + R_i} \right)$$

$$v_o = A_{vo} v_i \left(\frac{R_L}{R_o + R_L} \right)$$

$$V_o = A_{vo} V_s \left(\frac{R_i}{R_s + R_i} \right) \left(\frac{R_L}{R_o + R_L} \right)$$

$$\frac{V_o}{V_s} = A_{vo} \left(\frac{R_i}{R_s + R_i} \right) \left(\frac{R_L}{R_o + R_L} \right)$$

$$\frac{V_o}{V_s} = 100 \left(\frac{R_i}{R_s + R_i} \right) \left(\frac{R_L}{R_o + R_L} \right)$$

$$b) \quad \frac{V_o}{V_s} = 100 \left(\frac{R_i}{R_s + R_i} \right) \left(\frac{R_L}{R_o + R_L} \right)$$

$$c) \quad \frac{V_o}{V_s} = 100 \left(\frac{R_i}{R_s + R_i} \right) \left(\frac{R_L}{R_o + R_L} \right)$$

$$\frac{V_o}{V_s} = 100 \left(\frac{R_s}{R_s + R_s} \right) \left(\frac{R_o}{R_o + R_o} \right)$$

$$\frac{V_o}{V_s} = 100 \left(\frac{\frac{R_s}{10}}{R_s + \frac{R_s}{10}} \right) \left(\frac{\frac{R_o}{10}}{R_o + \frac{R_o}{10}} \right)$$

$$\frac{V_o}{V_s} = 100 \left(\frac{R_s}{10R_s + R_s} \right) \left(\frac{R_o}{10R_o + R_o} \right)$$


$$\frac{V_o}{V_s} = 100 \left(\frac{1}{11} \right) \left(\frac{1}{11} \right)$$

$$\boxed{\frac{V_o}{V_s} = 0.826 = -1.456 \text{ [dB]}}$$

$$\frac{V_o}{V_s} = 100 \left(\frac{1}{2} \right) \left(\frac{1}{2} \right)$$

$$\boxed{\frac{V_o}{V_s} = 2.5 = 27.94 \text{ [dB]}}$$

A2. An amplifier with 40 dB of small-signal, open-circuit voltage gain, an input resistance of $1 \text{ M}\Omega$, and an output resistance of 100Ω , drives a load of 500Ω . What voltage and power gains (expressed in dB) would you expect with the load connected? If the amplifier has a peak output-current limitation of 20 mA, what is the rms value of the largest sine-wave input for which an undistorted output is possible? What is the corresponding output power available?

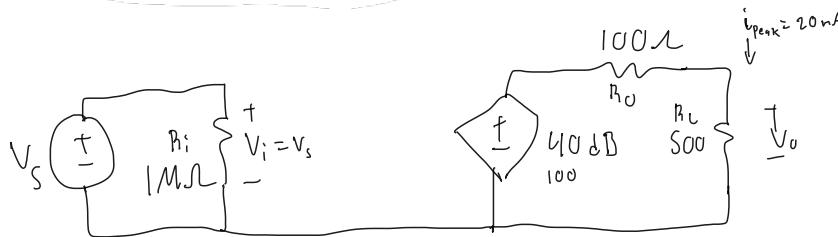

$$\frac{V_o}{V_s} = \frac{V_o}{V_i} = 100 \left(\frac{R_L}{R_o + R_L} \right)$$

$$\frac{V_o}{V_i} = 100 \left(\frac{500}{100 + 500} \right)$$

$$\frac{V_o}{V_i} = 100 \left(\frac{5}{6} \right)$$

$$A_v = \boxed{\frac{V_o}{V_i} = \sqrt{83.33} = 38.42 \text{ [dB]}}$$

$$P = V^2 I = \frac{V^2}{R} = I^2 R$$

power gain: $\frac{P_o}{P_i} = \frac{\frac{V_o^2}{R_L}}{\frac{V_i^2}{R_i}} = \frac{V_o^2 R_i}{V_i^2 R_L}$

$$A_p = \left(\frac{V_o}{V_i} \right)^2 \frac{R_i}{R_L}$$

$$A_p = (83.33)^2 \frac{1M}{500}$$

$$\boxed{A_p = 13.88 \text{ M} = 71.43 \text{ [dB]}}$$

$$V_{o,peak} = i_{peak} \cdot R_L \\ = (20 \text{ mA}) \cdot 500$$

$$V_{o,peak} = 10 \text{ [V]}$$

$$\frac{V_{o,peak}}{V_{i,peak}} = A_{v,peak}$$

$$V_{i,peak} = \frac{V_{o,peak}}{A_{v,peak}}$$

$$V_{i,peak} = \frac{10}{83.33}$$

$$V_{i,peak} = 120 \text{ [mV]}$$

$$V_{i,peak,RMS} = \frac{V_{i,peak}}{\sqrt{2}}$$

$$= \frac{120}{\sqrt{2}}$$


$$\boxed{= 84.85 \text{ [mV]}}$$

$$V_{o,peak,RMS} = \frac{10}{\sqrt{2}}$$

$$P_{V_{o,peak,RMS}} = \frac{V_{o,peak,RMS}^2}{R_L} \\ = \frac{\left(\frac{10}{\sqrt{2}}\right)^2}{500} \\ = \frac{100}{2} \frac{1}{500}$$

$$\boxed{= 0.1 \text{ [W]}}$$

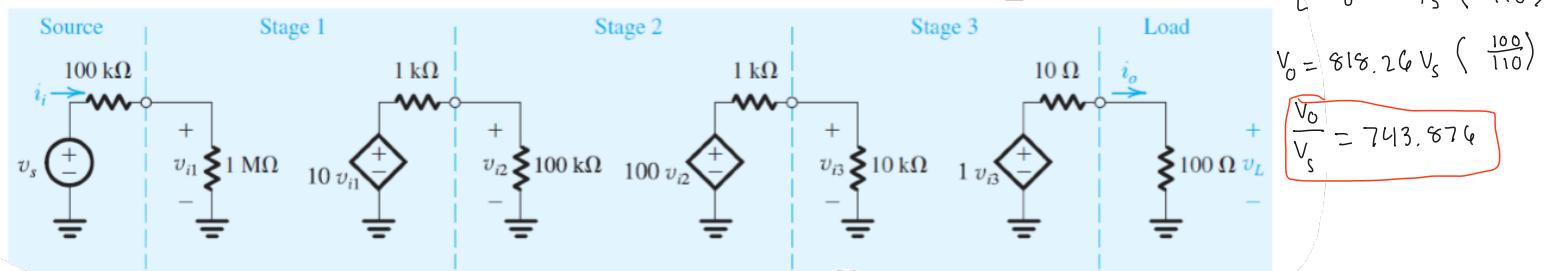A3. Find the overall voltage gain v_o/v_s and compare to the overall voltage gain obtained when the first and second stages are interchanged.



$$V_{i1} = V_s \left(\frac{1M}{100k+1M} \right)$$

$$V_{i2} = 10 V_{i1} \left(\frac{100k}{1k+100k} \right)$$

$$V_{i2} = 10 V_s \left(\frac{1M}{100k+1M} \right) \left(\frac{100k}{1k+100k} \right)$$

$$V_{i3} = 100 V_{i2} \left(\frac{10k}{1k+10k} \right)$$

$$V_{i3} = 100 \cdot 10 V_s \left(\frac{1M}{100k+1M} \right) \left(\frac{100k}{1k+100k} \right) \left(\frac{10k}{1k+10k} \right)$$

$$= 818.24 V_s$$

$$V_L = V_o = V_{i3} \left(\frac{100}{110} \right)$$

$$V_o = 818.24 V_s \left(\frac{100}{110} \right)$$

$$\frac{V_o}{V_s} = 743.874$$

If stage 1 \leftrightarrow stage 2:

$$V_{i2} = V_s \left(\frac{100k}{200k} \right) = \frac{1}{2} V_s$$

$$V_{i1} = 100 V_{i2} \left(\frac{1M}{1k+1M} \right)$$

$$V_{i1} = 50 V_s \left(\frac{1M}{1k+1M} \right)$$

$$V_{i3} = 10 V_{i1} \left(\frac{10k}{1k} \right)$$

$$V_{i3} = \frac{5000}{11} \left(\frac{1M}{1k+1M} \right) V_s$$


$$V_L = V_o = V_{i3} \left(\frac{10}{110} \right)$$

$$V_o = \frac{5000}{11} \left(\frac{1M}{1k+1M} \right) V_s \left(\frac{10}{11} \right)$$


$$\frac{V_o}{V_s} = 412.81$$

A4. You are given two amplifiers, A and B, to connect in cascade between a 10-mV, 100-k Ω source and a 100- Ω load. The amplifiers have voltage gain, input resistance, and output resistance as follows: for A, 100 V/V, 100 k Ω , 10 k Ω , respectively; for B, 10 V/V, 10 k Ω , 1 k Ω , respectively. Your problem is to decide how the amplifiers should be connected. To proceed, evaluate the two possible connections between source S and load L, namely, SABL and SBAL. Find the voltage gain for each both as a ratio and in decibels. Which amplifier arrangement is best?

SABL:

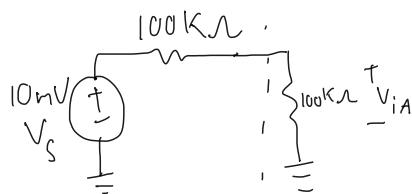

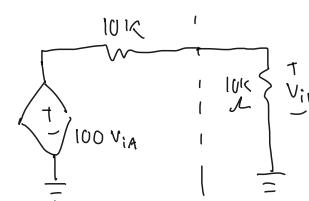
$$V_{iA} = V_s \left(\frac{100k}{200k} \right) = \frac{1}{2} V_s$$



$$V_{iB} = 100 V_{iA} \left(\frac{10k}{20k} \right)$$

$$V_{iB} = 100 \left(\frac{1}{2} V_s \right) \left(\frac{1}{2} \right)$$

$$V_{iB} = 25 V_s$$

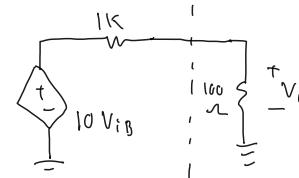


$$V_o = 10 V_{iB} \left(\frac{100}{1100} \right)$$


$$V_o = \frac{10}{11} (25 V_s)$$

$$A_{SABL} = \frac{V_o}{V_s} = \frac{250}{11} = 22.72 = 27.13 \text{ [dB]}$$


SBAL:

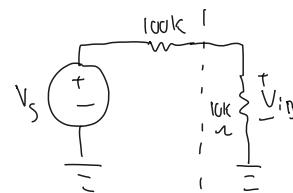
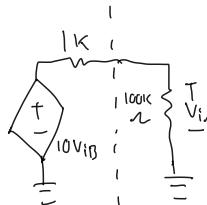
$$V_{iB} = V_s \left(\frac{10k}{110k} \right) = \frac{1}{11} V_s$$


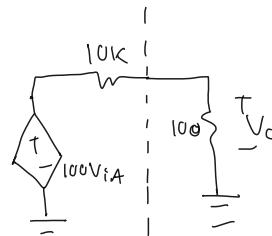
$$V_{iA} = 10 V_{iB} \left(\frac{100k}{10k} \right) = \frac{1000}{101} \cdot \frac{1}{11} V_s$$



$$V_o = 100 V_{iA} \left(\frac{100}{10k+100} \right) = 100 \left(\frac{1}{11} \cdot \frac{1000}{101} \right) V_s \left(\frac{100}{10k+100} \right)$$

$$\frac{V_o}{V_s} = 0.891 = -1 \text{ [dB]}$$

Clearly, SABL is the better amplifier arrangement since SBAL actually attenuates the signal.

A5. Design an amplifier that provides 0.5W of signal power to a 100Ω load resistance. The signal source provides a 30-mV rms signal and has a resistance of $0.5M\Omega$. Three types of voltage-amplifier stages are available:



- A high-input-resistance type with $R_i = 1 M\Omega$, $A_{vo} = 10$, and $R_o = 10 k\Omega$
- A high-gain type with $R_i = 10 k\Omega$, $A_{vo} = 100$, and $R_o = 1 k\Omega$
- A low-output-resistance type with $R_i = 10 k\Omega$, $A_{vo} = 1$, and $R_o = 20\Omega$

Design a suitable amplifier using a combination of these stages. Your design should utilize the minimum number of stages and should ensure that the signal level is not reduced below 10 mV at any point in the amplifier chain. Find the load voltage and power output realized.

$$P_L = 0.5 = \frac{V_o^2}{R_L} = \frac{V_o^2}{100}$$

$$V_o = \sqrt{50} [V] \quad \text{low-output for final stage}$$

$$I_o = \frac{V_o}{R_o} = 70.71 [mA]$$

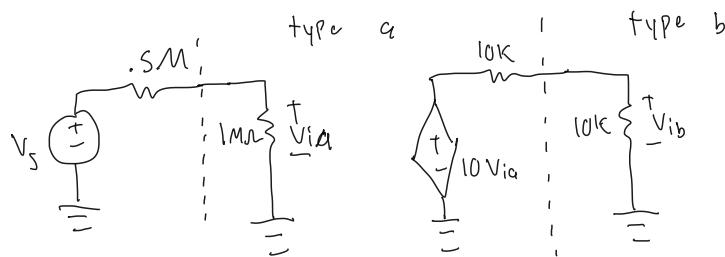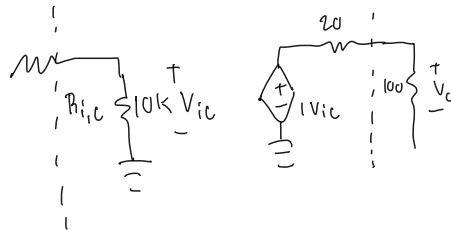

Due to high signal resistance, need high-input resistance to minimize voltage loss. \therefore type a

$$V_{ia} = V_s \left(\frac{1M}{1.5M} \right)$$


$$V_{ia} = \frac{2}{3} V_s$$

$$\text{check: above 10mV: } V_{ia} = \frac{2}{3}(30m) = 20mV$$

$$V_{ib} = 10V_{ia} \left(\frac{10k}{20k} \right) = 10 \left(\frac{2}{3} V_s \right) \left(\frac{1}{2} \right)$$

$$V_{ib} = \frac{10}{3} V_s$$
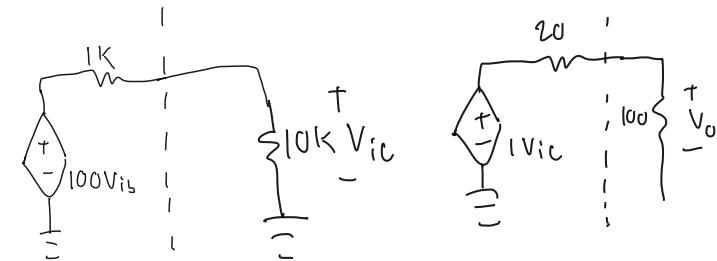
$$\text{check: } \frac{10}{3}(30m) = 100mV$$



Try: add c to realize minimum stages before trying more stages unnecessarily,

$$V_o = V_{ic} \left(\frac{100}{100} \right) = \frac{10k}{33} V_s \left(\frac{5}{4} \right)$$

$$V_o = \frac{25k}{99} (30m) = \frac{250}{33} [V] = V_L$$

$$P_L = \frac{V_L^2}{R_L} = \frac{\left(\frac{250}{33}\right)^2}{100}$$

$$P_L = 0.5741 [W]$$

Can't use type b or c as 1st stage since $R_i \ll R_L$ and wouldn't provide sufficient voltage. \therefore add (a) first. If a connected directly to c, not enough power to drive load. ex. $V_{ic} = 10V_{ia} \left(\frac{10k}{20k} \right) = 5 \left(\frac{2}{3} V_s \right)$

Source \rightarrow a \rightarrow b \rightarrow c \rightarrow load


$$\text{check: } 10mV : \frac{10}{3}(30m) = .1V = 100mV$$

$$V_o = V_{ic} \left(\frac{100}{100} \right) = \frac{10}{3} V_s \left(\frac{10}{10} \right) = \frac{25}{3} V_s$$

$$V_o = 83.3 [V] = V_L$$


$$P_L = \frac{(83.3m)^2}{100} = 69 [mW] < 0.5 [W]$$

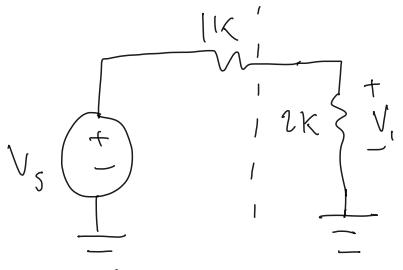A6. A transconductance amplifier with $R_i = 2 \text{ k}\Omega$, $G_m = 60 \text{ mA/V}$, and $R_o = 20 \text{ k}\Omega$ is fed with a voltage source having a source resistance of $1 \text{ k}\Omega$ and is loaded with a $1\text{-k}\Omega$ resistance. Find the voltage gain realized.



$$V_i = V_s \left(\frac{2k}{3k} \right)$$

$$V_i = \frac{2}{3} V_s$$

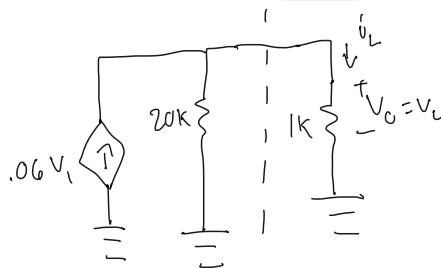

$$\text{Current divide: } i_L = 0.06 V_i \left(\frac{20k}{21k} \right)$$

$$= \frac{2}{35} \left(\frac{2}{3} V_s \right)$$


$$= \frac{4}{105} V_s$$

$$V_L = V_o = i_L R_L$$

$$V_o = \left(\frac{4}{105} V_s \right) (1k)$$

$$\frac{V_o}{V_s} = 38.045 = 38.1 = 31.62 [\text{dB}]$$

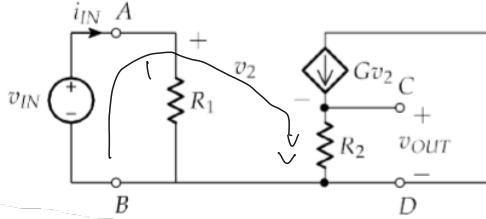A7. For the following circuits, find the voltage gain, v_0/v_{IN} , and the input and output resistances.



$$Gv_2 R_2 = V_{out}$$

$$V_2 = \frac{V_{out}}{G R_2}$$

$$\text{KVL: } V_{IN} = V_2 + V_{out}$$

$$V_{IN} = \frac{V_{out}}{G R_2} + V_{out}$$

$$V_{IN} = V_{out} \left(1 + \frac{1}{G R_2} \right)$$

$$\frac{V_{out}}{V_{IN}} = \frac{1}{1 + \frac{1}{G R_2}}$$


$$\frac{V_{out}}{V_{IN}} = \frac{G R_2}{G R_2 + 1}$$

$$R_{in} = R_1$$



$$R_{in} = R_1$$

$$R_{out} = R_2$$

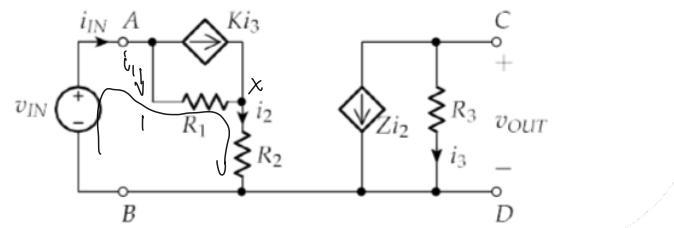

$$i_2 = \frac{V_x}{R_2}$$

$$i_2 = i_1 + K_2 i_3$$

$$i_2 (1 + K_2) = \frac{V_{IN} - V_x}{R_1}$$

$$\frac{V_x}{R_2} (1 + K_2) = \frac{V_{IN} - V_x}{R_1}$$

$$V_x (1 + K_2) = \frac{R_2}{R_1} V_{IN} - \frac{R_2}{R_1} V_x$$

$$V_x (1 + K_2 + \frac{R_2}{R_1}) = \frac{R_2}{R_1} V_{IN}$$

$$V_x = \frac{R_2}{R_1 (1 + K_2 + \frac{R_2}{R_1})} V_{IN}$$

$$V_x = \frac{R_2}{R_2 + R_1 (1 + K_2)} V_{IN}$$

$$i_3 = -2 i_2$$

$$\frac{V_{out}}{R_3} = -2 i_2$$

$$V_{out} = -2 R_3 i_2$$

$$V_{out} = -Z R_3 \frac{V_x}{R_2}$$

$$V_{out} = -Z \frac{R_2}{R_1} \left(\frac{R_2}{R_2 + R_1 (1 + K_2)} V_{IN} \right)$$

$$\frac{V_{out}}{V_{IN}} = -\frac{Z R_3}{R_2 + R_1 (1 + K_2)}$$

For R_{in} :

$i_{IN} = i_2$

$$i_2 (1 + K_2) = \frac{V_{IN} - V_x}{R_1}$$

$$i_2 (1 + K_2) + \frac{R_2 i_2}{R_1} = \frac{V_{IN}}{R_1}$$

$$i_2 R_1 (1 + K_2) + R_2 i_2 = V_{IN}$$

$$i_2 (R_1 (1 + K_2) + R_2) = V_{IN}$$

$$\frac{V_{IN}}{i_2} = \frac{V_{IN}}{i_{IN}} = R_{in} = R_2 + R_1 (1 + K_2)$$

For R_{out} :



$$R_{out} = \frac{V_I}{i_T}$$

$$i_2 = K i_3 \left(\frac{R_1}{R_1 + R_2} \right)$$

$$\text{KVL a/c: } i_T = i_3 + Z i_2$$


$$i_T = \frac{V_I}{R_3} + Z \left[K i_3 \left(\frac{R_1}{R_1 + R_2} \right) \right]$$

$$i_T = \frac{V_I}{R_3} \left[Z K \left(\frac{R_1}{R_1 + R_2} \right) \right]$$


$$\frac{V_I}{i_T} = \frac{R_3}{Z K \left(\frac{R_1}{R_1 + R_2} \right)}$$

$$\frac{V_I}{i_T} = R_{out} = \frac{R_3 (R_1 + R_2)}{R_1 + R_2 + R_1 Z K}$$



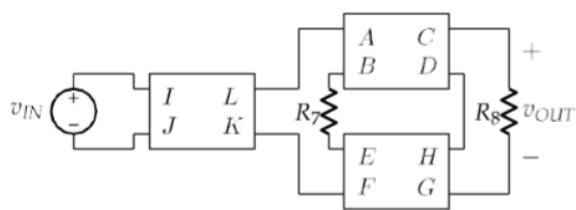
A8. For the cascaded amplifier circuit in (c), find voltage gain, v_0/v_{IN} , and the input and output resistances using the circuits in (d)-(f).



(c)

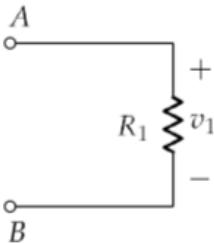

(d)

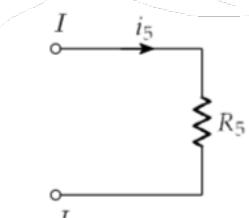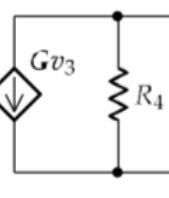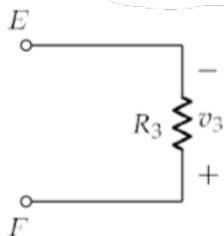

(f)


$$V_{IN} = \frac{V_{IN}}{R_S}$$

$$V_{IN} = \frac{V_{IN}}{R_S}$$

$$\text{Volt divide: } V_1 = -Z_i S \left(\frac{R_1}{R_1 + R_3 + R_4 + R_7} \right)$$

$$V_1 = -V_{IN} \left(\frac{R_1}{R_s(R_1 + R_3 + R_4 + R_7)} \right)$$
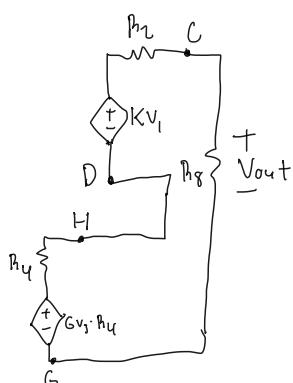
$$V_3 = -V_{IN} \left(\frac{R_3}{R_s(R_1 + R_3 + R_4 + R_7)} \right)$$



$$V_{out1} = (Gv_3 R_4 + Kv_1) \left(\frac{R_8}{R_4 + R_2 + R_8} \right)$$

$$V_{out} = (Gv_3 Z V_{IN} \left(\frac{R_3}{R_s(R_1 + R_3 + R_4 + R_7)} \right)) + Kv_1 Z V_{IN} \left(\frac{R_1}{R_s(R_1 + R_3 + R_4 + R_7)} \right) \left(\frac{R_8}{R_4 + R_2 + R_8} \right)$$

$$\frac{V_{out}}{V_{IN}} = Z \left(\frac{G R_4 R_3 - K R_1}{R_s(R_1 + R_3 + R_4 + R_7)} \right) \left(\frac{R_8}{R_4 + R_2 + R_8} \right)$$



For R_{out} :

$$V_{IN} = 0 \therefore Z_i S = 0, V_1 = 0, V_2 = 0$$

$$Kv_1 = 0, Gv_3 = 0$$

$$R_{in} = \frac{V_{IN}}{i_{in}} = \frac{V_{IN}}{i_s}$$

$$\therefore R_{in} = R_S$$

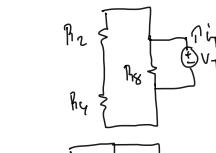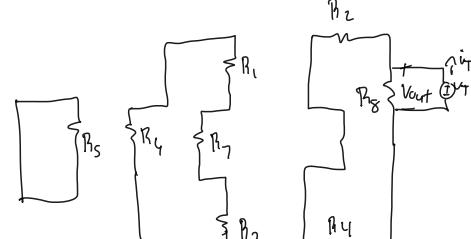

$$R_{out} = (R_2 + R_4) \parallel R_8$$