

ECE 3355: Electronics

Section 19453/18023

Spring 2022

Exam 1

Version A




March 5, 2022

Complete the exam on your own, without the help of your notes, prior examples or solutions, your book, or any communication/interaction with others. You must write a complete solution that shows the relevant steps if you want full credit for the problem. You may use a calculator and a crib sheet is provided as part of this exam. **You will have 1 hour 15 minutes to finish the exam.**






Student's Name: _____

Question	Points	Score
1	15	
2	10	
3	10	
4	20	
5	15	
6	15	
7	15	
Total:	100	

Inverting Amplifier

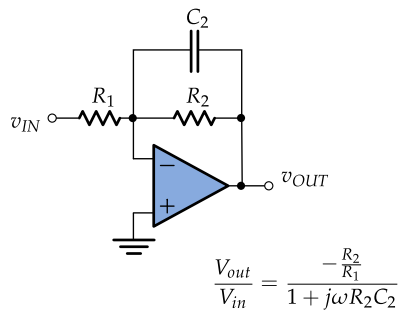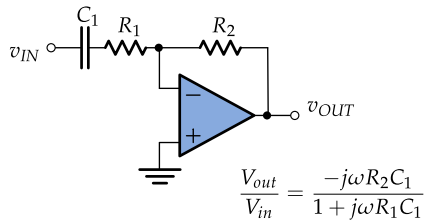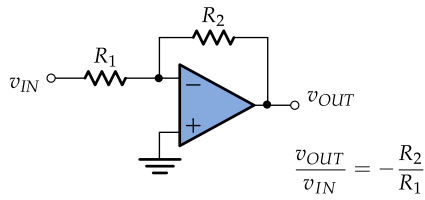


Non-inverting Amplifier

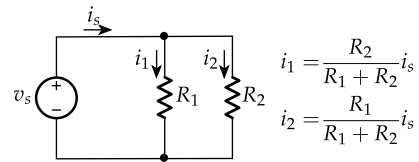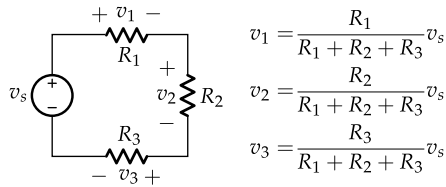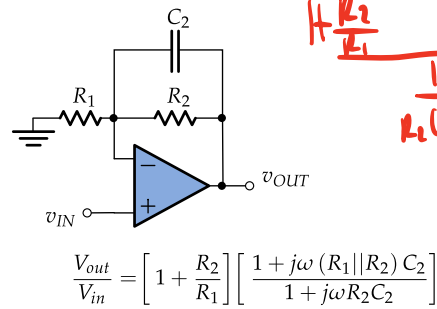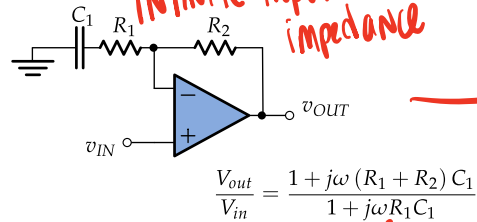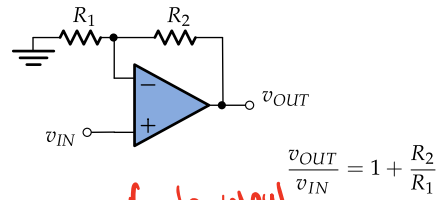

$$v_B = \underbrace{V_B}_{DC} + \underbrace{v_b}_{AC}$$

$\bar{V}_b \rightarrow$ Phasor notation

$$CMRR = 20 \log_{10} \frac{|A_d|}{|A_{cm}|}$$

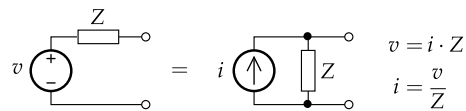

HPF

$$-\frac{R_2}{R_1}$$

$$\frac{1}{R_1 C_1}$$

LPF

$$-\frac{R_2}{R_1}$$

$$\frac{1}{R_2 C_2}$$

Step-up
 $1 + \frac{R_2}{R_1}$

infinite input impedance

$$\frac{1}{R_1 C_1}$$


$$(R_1 + R_2) C_1$$

$$H \frac{R_2}{R_1}$$

$$\frac{1}{R_2 C_2}$$

$$(R_1 || R_2) C_2$$

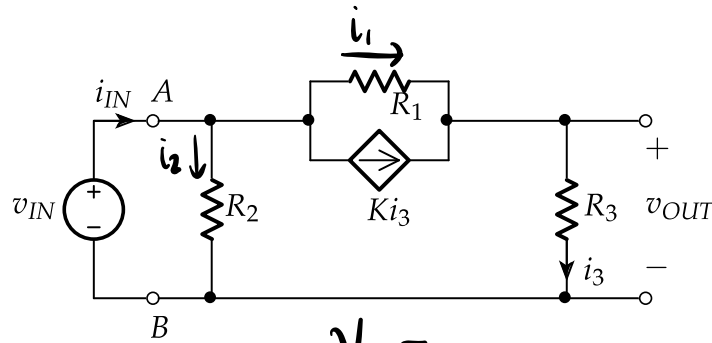1. (15 points) For the following circuit, find the voltage gain, $\frac{v_{OUT}}{v_{IN}}$, and the input and output resistances.



$$V_{OUT} = i_3 R_3 \Rightarrow i_3 = \frac{V_{OUT}}{R_3}$$


$$V_{IN} = i_2 R_2 = i_1 R_1 + V_{OUT}$$

$$i_3 = i_1 + K i_3 \Rightarrow i_1 = i_3 (1 - K) = (1 - K) \frac{V_{OUT}}{R_3}$$

$$V_{IN} = \left((1 - K) \frac{V_{OUT}}{R_3} \right) R_1 + V_{OUT} = V_{OUT} \left((1 - K) \frac{R_1}{R_3} + 1 \right)$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{1}{(1 - K) \frac{R_1}{R_3} + 1}$$

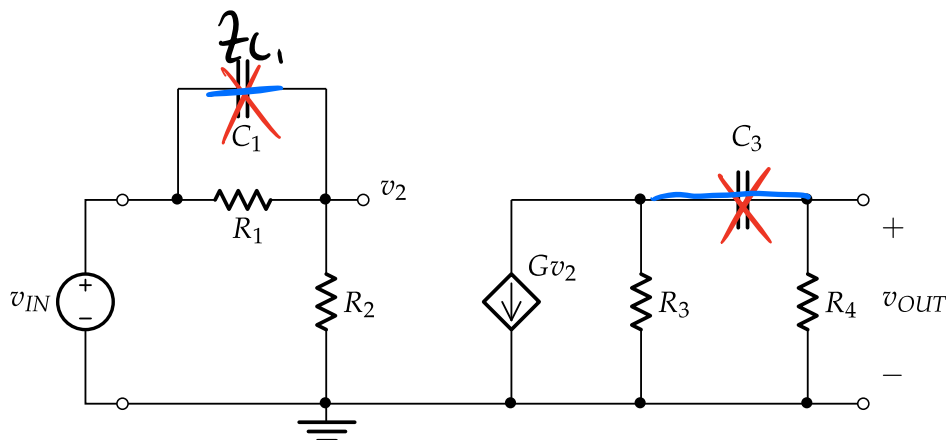2. (10 points) For the following circuit, answer the three questions below.



(a) Write an expression for $\frac{\bar{V}_{out}}{\bar{V}_{in}}$. Write the solution in the form that allows easy identification of the poles and zeros.

$$\bar{V}_2 = \frac{R_2}{R_2 + (R_1 \parallel Z_{C_1})} \bar{V}_{IN} = \left(\frac{R_2}{R_2 + \frac{R_1 \cdot \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}}} \right) \bar{V}_{IN}$$

$$= \frac{R_2 \left(R_1 + \frac{1}{j\omega C_1} \right)}{R_2 \left(R_1 + \frac{1}{j\omega C_1} \right) + R_1 \cdot \frac{1}{j\omega C_1}}$$

(b) What is the gain at low frequencies?

(b) 0


(c) What is the gain at high frequencies?

(c) $-G(R_3 \parallel R_4)$

$$= \frac{R_2 (1 + j\omega C_1 R_1)}{R_2 + j\omega C_1 R_1 R_2 + R_1}$$

$$= \frac{R_2}{R_2 + R_1} \frac{1 + j\omega C_1 R_1}{1 + j\omega \frac{C_1 R_1 R_2}{R_2 + R_1}}$$

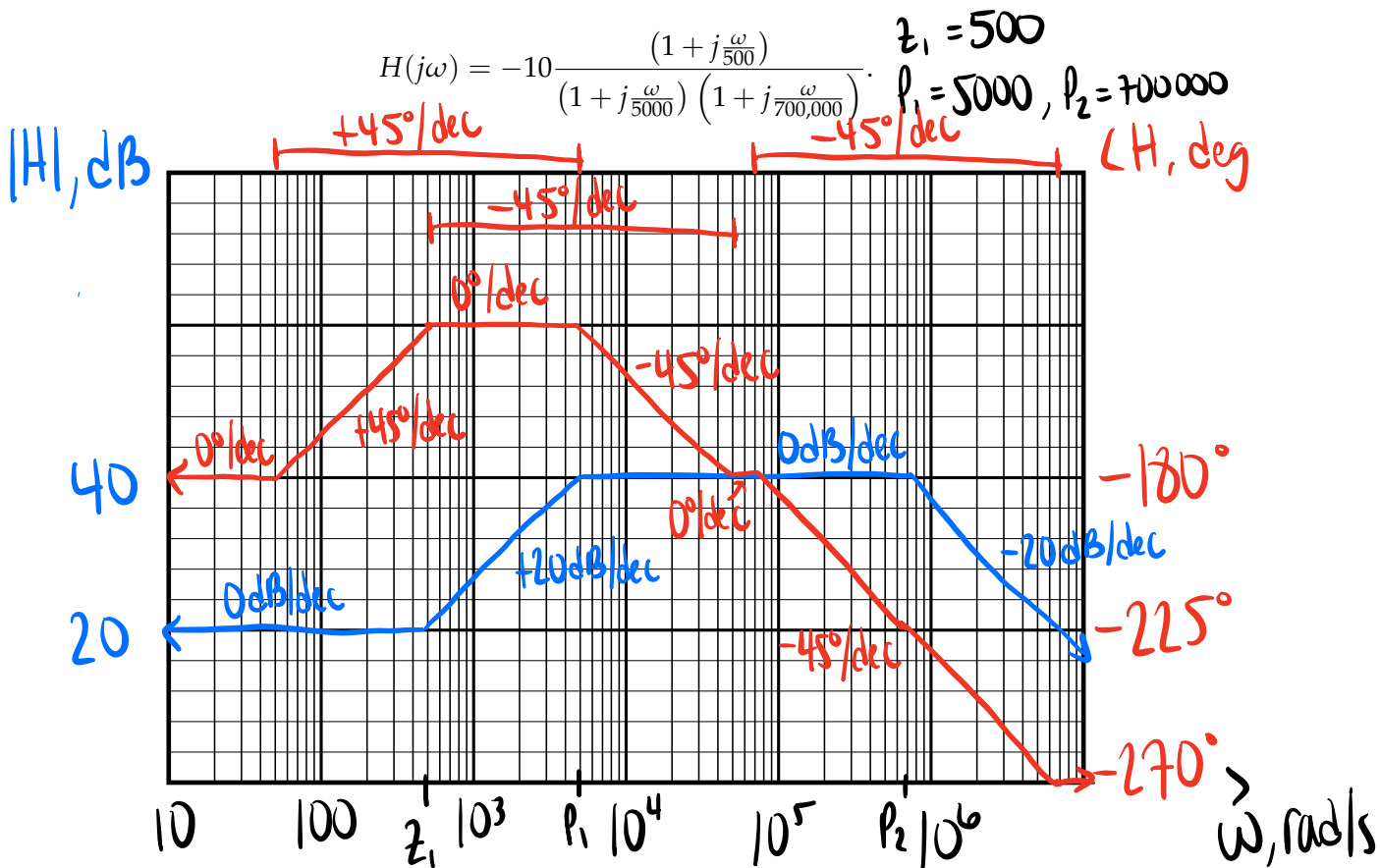3. (10 points) Plot a straight-line approximation Bode plot on the graph paper provided for both the magnitude and the phase for the following transfer function (the unit for the given values is rad/sec).



$$\omega = 50$$

$$H(j50) = -10$$

$$|H(j50)| = 10$$

$$\text{or } 20 \log_{10} 10 = 20 \text{ dB}$$

$$\angle H(j50) = -180^\circ / 180^\circ$$

ω large



$$H(\omega) = -\frac{1}{0.1} = -10$$

$$\angle H(\omega) = 90^\circ / -270^\circ$$

4. (20 points) For the following amplifier, determine the ratios of R_A , R_B , R_C , and R_D that allow for the circuit to be a difference amplifier **using superposition**.

① $v_2 = 0$

② $v_1 = 0$

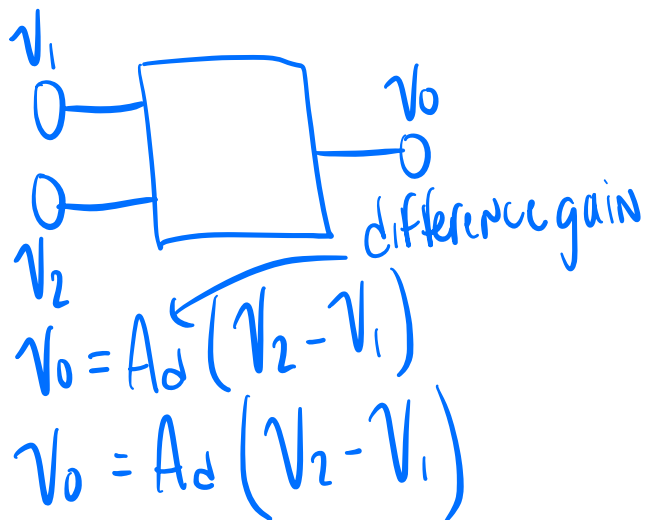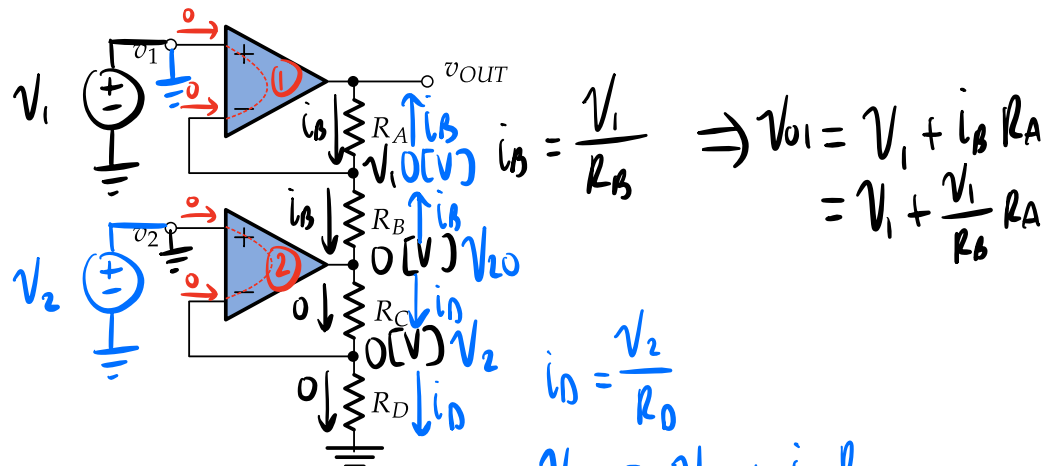

$$v_{OUT} = v_{O1} + v_{O2}$$

$$= v_1 + \frac{v_1}{R_B} R_A - R_A \left(\frac{v_2 \left(1 + \frac{R_C}{R_D}\right)}{R_B} \right)$$

$$= \underbrace{v_1 \left(1 + \frac{R_A}{R_B}\right)}_{A_d} - \underbrace{v_2 \frac{R_A}{R_B} \left(1 + \frac{R_C}{R_D}\right)}_{A_d}$$

$$1 + \frac{R_A}{R_B} = \frac{R_A}{R_B} \left(1 + \frac{R_C}{R_D}\right)$$

$$\frac{R_B + R_A}{\cancel{R_B}} = \frac{R_A}{\cancel{R_B}} \left(1 + \frac{R_C}{R_D} \right)$$

$$\frac{R_B + R_A}{R_A} = 1 + \frac{R_C}{R_D}$$

$$1 + \frac{R_B}{R_A} = 1 + \frac{R_C}{R_D}$$

$$\frac{R_B}{R_A} = \frac{R_C}{R_D}$$

what is the common mode gain?

$$V_{out} = V_1 \left(1 + \frac{R_A}{R_B} \right) - V_2 \frac{R_A}{R_B} \left(1 + \frac{R_C}{R_D} \right)$$

$$V_1 = V_2$$

$$V_{out_{cm}} = V_1 \left(1 + \frac{R_A}{R_B} - \frac{R_A}{R_B} \left(1 + \frac{R_C}{R_D} \right) \right)$$

A_{cm}

5. (15 points) Consider a difference amplifier, such as the one the previous problem. If $A_d = 10$ and $\text{CMRR} = 80 \text{ dB}$, what is the output, v_{OUT} , if

$$v_1 = 1.2[\text{V}] \cos \omega_1 t + 0.25[\text{V}] \sin \omega_2 t$$

and

$$v_2 = 1.3[\text{V}] \cos \omega_1 t$$

$$\text{CMRR} = 20 \log \frac{A_d}{A_{cm}} = 80 \text{ dB}$$

$$\frac{A_d}{A_{cm}} = 10^4 \quad A_d = 10 \Rightarrow A_{cm} = 10^{-3}$$

$20 \cdot 4 = 80$

$$v_2 - v_1 = 0.1[\text{V}] \cos \omega_1 t - 0.25[\text{V}] \sin \omega_2 t$$

$$v_{od} = 10 (v_2 - v_1)$$

$$v_{ocm} = 10^{-3} (1.2[\text{V}] \cos \omega_1 t)$$


$$v_{OUT} = v_{od} + v_{ocm}$$

$$v_{OUT} = 1[\text{V}] \cos \omega_1 t + 2.5[\text{V}] \sin \omega_2 t + 1.2[\text{mV}] \cos \omega_1 t$$

6. (15 points) For the following circuit,

(a) Find an expression for the voltage gain, $\frac{v_{OUT}}{v_{IN}}$. Hint: draw the test source at the input.

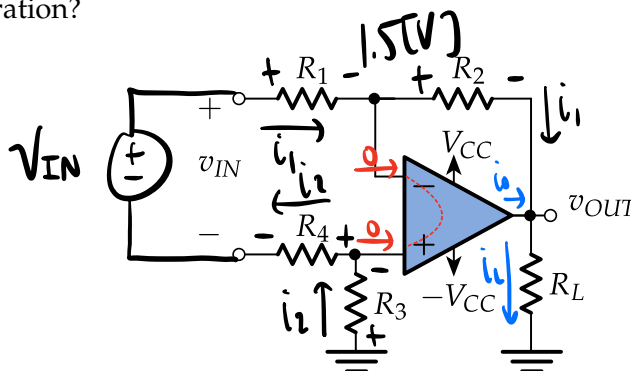(b) Using $R_1 = R_4 = 2\text{ k}\Omega$, $R_2 = R_3 = 1\text{ k}\Omega$, $v_{IN} = -6\text{ V}$, and $i_{max} = 10\text{ mA}$, what is the smallest load resistance that you can add to the circuit without having the op-amp go into saturation?



$$i_1 = i_2$$

$$V_{IN} = i_1 R_1 + i_1 R_4$$

$$\Rightarrow i_1 = \frac{V_{IN}}{R_1 + R_4} = \frac{-6[V]}{2[k\Omega] + 2[k\Omega]}$$

$$i_1 = -1.5[MA]$$

$$V_+ = 0 - i_1 R_3 = -(-1.5[MA])(1[k\Omega])$$

$$V_+ = 1.5[V]$$

$$V_{OUT} = 1.5[V] - i_1 R_2 = 1.5[V] - (-1.5[MA])(1[k\Omega]) = 3[V]$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{3[V]}{-6[V]} = -\frac{1}{2}$$



$$i_O = 1.5[MA] + i_L < 10[MA]$$

$$= 1.5[MA] + \frac{3[V]}{R_L} < 10[MA]$$

$$\frac{3[V]}{R_L} < 8.5[MA]$$

$$R_L > \frac{3[V]}{8.5[MA]} = 352.9[\Omega]$$

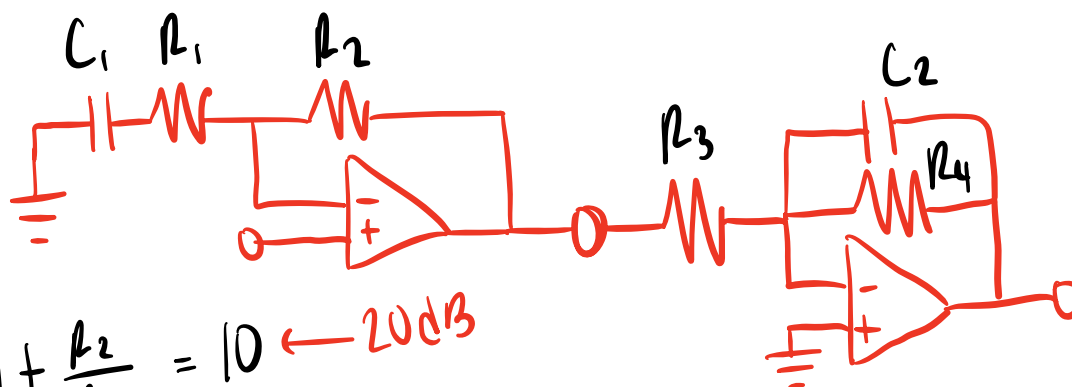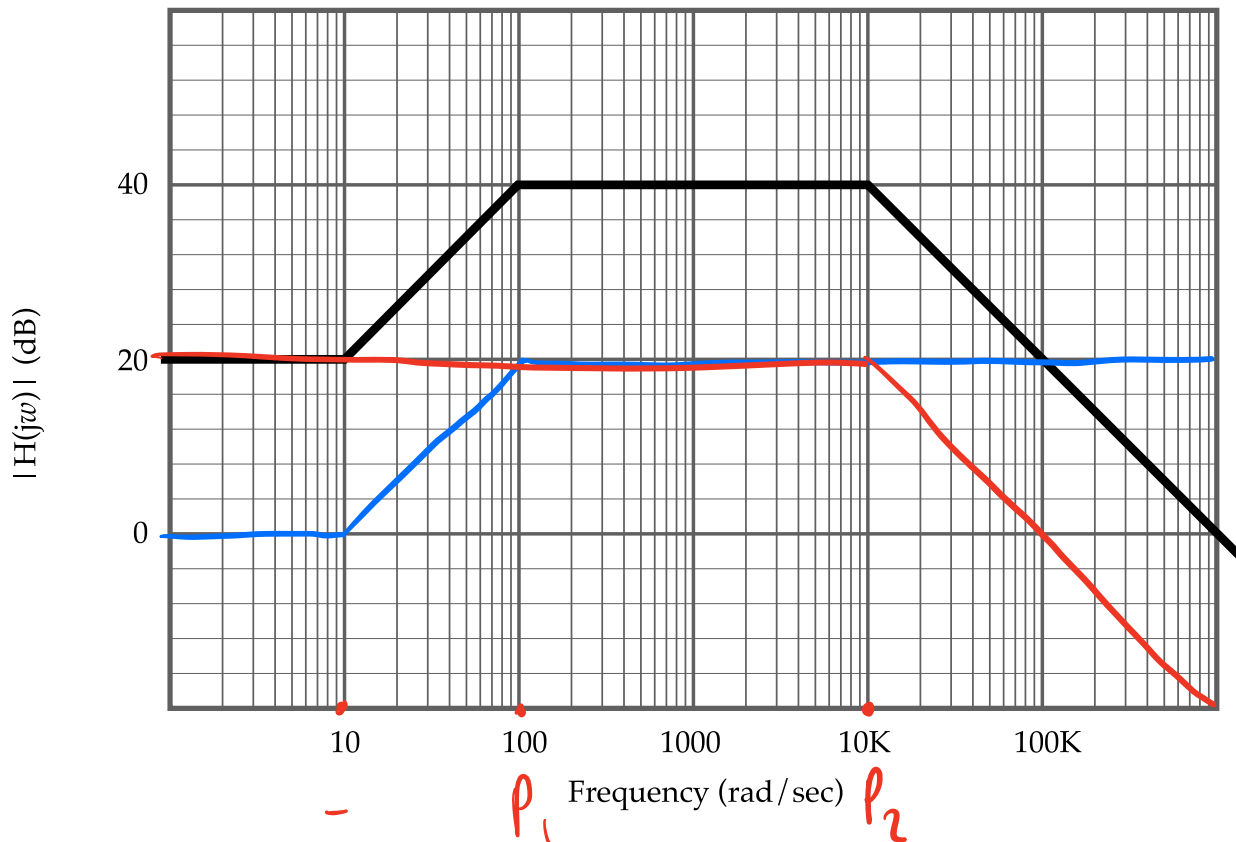7. (15 points) You have been asked to design a circuit that has the following straight-line approximation to the Bode plot. Use ideal op-amps, resistors, and capacitors to design the circuit and indicate which order the stages should be placed to ensure the circuit is not very sensitive to changes in the source resistance.



$$1 + \frac{R_2}{R_1} = 10 \leftarrow 20\text{dB}$$

$$\frac{R_2}{R_1} = 9 \Rightarrow R_2 = 9R_1$$

$$R_1 = 1\text{[k}\Omega\text{]}, R_2 = 9\text{[k}\Omega\text{]}$$

$$\frac{R_4}{R_3} = 10 \Rightarrow R_4 = 10R_3$$

$$R_4 = 10\text{[k}\Omega\text{]}, R_3 = 1\text{[k}\Omega\text{]}$$

$$\omega_{P_1} = \frac{1}{R_1 C_1} = 100$$

$$\frac{1}{1[\text{h}\mu\text{A}]\omega_1} = 100 \Rightarrow C_1 = 10^{-5}[\text{F}] = 10[\mu\text{F}]$$

$$\omega_{p2} = \frac{1}{10[\text{h}\mu\text{A}]\omega_2} = 10000 \Rightarrow C_2 = 10[\text{nF}]$$