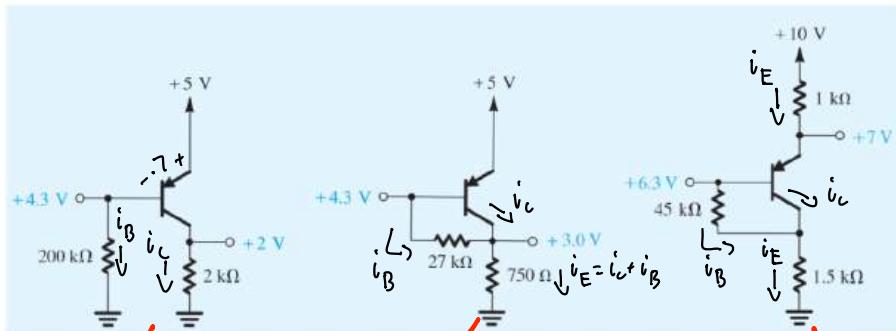


1. Measurements on the circuits below produce labeled voltages as indicated. Find the value of  $\beta$  for each transistor.



$$i_B = \frac{i_C}{\beta}$$

$$\beta = \frac{i_C}{i_B} = \frac{\left(\frac{2}{2k}\right)}{\left(\frac{4.3 - 3}{200k}\right)}$$

$$\boxed{\beta = 414.512}$$

$$i_B = \frac{i_E}{\beta+1}$$

$$\beta = \frac{i_E}{i_B} - 1$$

$$\beta = \frac{\left(\frac{3}{750}\right)}{\left(\frac{4.3 - 3}{27k}\right)} - 1$$

$$\boxed{\beta = 82.08}$$

$$i_E = \frac{10 - 7}{1k} = 3mA$$

$$6.3 = i_B 45k + i_E 1.5k$$

$$\frac{6.3 - i_E 1.5k}{45k} = i_B$$

$$i_B = .04mA$$

$$i_C = i_E - i_B$$

$$= 3 - .04$$

$$i_C = 2.96mA$$

2. For the circuits in below, find values for the labeled node voltages and branch currents. Assume  $\beta=100$  to be very high.

$$i_B = \frac{i_E}{\beta+1} = \frac{.5mA}{100+1}$$

$$i_B \approx 4.95mA$$

$$i_C = \beta i_B \approx .495mA$$

$$\frac{3 - V_2}{3.6k} = i_C$$


$$3 - i_C 3.6k = V_2$$

$$\boxed{V_2 \approx 1.218 [V]}$$

$$V_D = -i_B 43k$$

$$V_B = -0.213$$
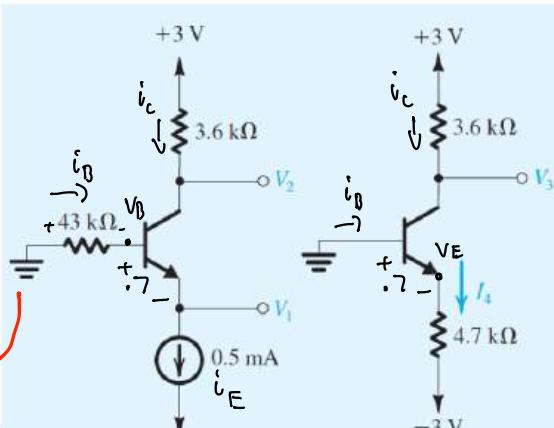
$$\boxed{V_1 = V_B - .7 \approx -0.413 [V]}$$



$$V_E = -0.7$$

$$I_4 = \frac{-0.7 - (-3)}{4.7k} = .489mA$$


$$i_B = \frac{I_4}{\beta+1} = 4.85mA$$

$$i_C = \beta i_B = .485mA$$

$$3 - V_7 = i_C 3.4k$$

$$V_3 = 3 - (0.485)(3.4k)$$

$$\boxed{V_3 \approx 1.246V}$$

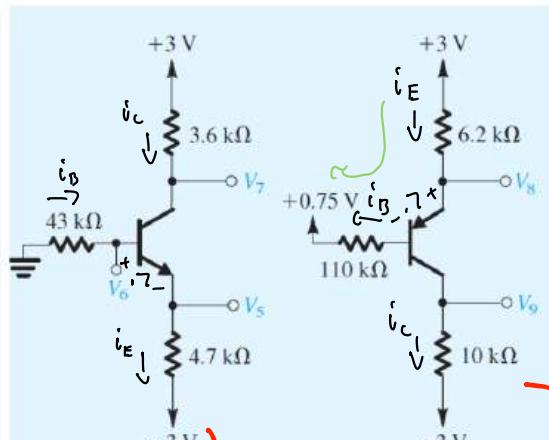

$$0 - (-3) = i_B 43k + .7 + i_E (4.7k)$$

$$3 - .7 = i_B (43k + (\beta+1)(4.7k))$$

$$i_B = \frac{2.3}{(43k + (\beta+1)(4.7k))}$$

$$i_B \approx 4.44mA$$

$$i_C = \beta i_B \approx 0.444mA$$

$$0 - V_4 = i_B 43k$$

$$\boxed{V_4 = -0.191 [V]}$$

$$V_4 - .7 = V_5$$

$$\boxed{V_5 = -0.891 [V]}$$

$$3 - V_7 = i_C 3.4k$$

$$V_7 = 3 - i_C 3.4k$$

$$\boxed{V_7 \approx 1.4 [V]}$$

$$3 - .75 = i_E 6.2k + .7 + i_B 110k$$

$$2.25 - .7 = i_B (110k + (\beta+1)6.2k)$$

$$i_B = \frac{1.55}{(110k + (\beta+1)6.2k)}$$

$$i_B \approx 2.11mA$$

$$i_E = (\beta+1) i_B = 0.213mA$$

$$3 - V_8 = i_E 6.2k \Rightarrow 3 - i_E 6.2k$$

$$\boxed{V_8 \approx 1.482 [V]}$$

$$i_C = \beta i_B = .211mA$$

$$V_9 - (-3) = i_C 10k$$

$$\boxed{V_9 = i_C 10k - 3 \approx -0.895 [V]}$$

3. Consider the circuit shown in figure below. Using  $|V_{BE}|$  and  $V_D = 0.7 \text{ V}$  independent of current, and  $\beta = \infty$ , find the voltages  $V_{B1}$ ,  $V_{E1}$ ,  $V_{C1}$ ,  $V_{B2}$ ,  $V_{E2}$ , and  $V_{C2}$ , initially with  $R$  open-circuited and then with  $R$  connected. Repeat for  $\beta = 100$ , with  $R$  open-circuited initially, then connected.

$$\beta = \infty$$

$$\frac{q - 0.7}{120k} = I \approx 49.2 \text{ mA}$$

$$q - V_{B1} = I \cdot 80k$$

$$V_{B1} \approx 3.467 \text{ [V]}$$

$$V_{E1} = V_{B1} - 0.7 \approx 2.747 \text{ [V]}$$

$$q - 0.7 - V_{c1} = i_{c1} \cdot 2k$$

$$8.3 - i_{c1} \cdot 2k = V_{c1}$$

$$V_{c1} \approx 5.533 \text{ [V]} = V_{B2}$$


$$V_{E2} - 0.7 = V_{B2}$$

$$V_{E2} = V_{B2} + 0.7 = 6.23 \text{ [V]}$$


$$i_{E2} = \frac{q - V_{E2}}{100} = 27.67 \text{ mA} = i_{c2}$$

$$V_{c2} = i_{c2} \cdot 100$$

$$V_{c2} = 2.747 \text{ [V]}$$

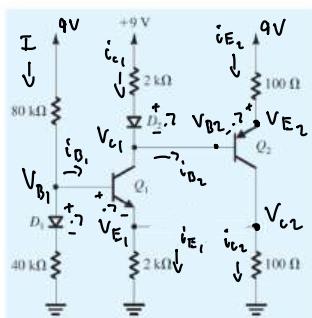

$$\beta = \infty$$

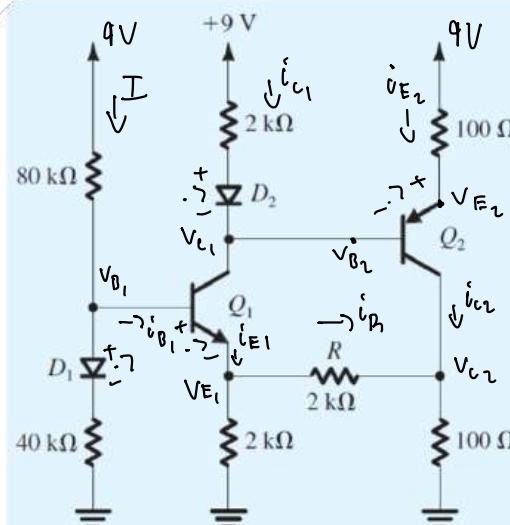

$$V_{E1} = 2.747 \text{ [V]}$$


$$V_{c2} = 2.747 \text{ [V]}$$

$$V_{B2} = \frac{V_{E1} - V_{c2}}{R}$$

$$i_R = 0$$

Voltages same whether  $R$  is connected or not ( $\beta \rightarrow \infty$ )

$$\beta = 100$$

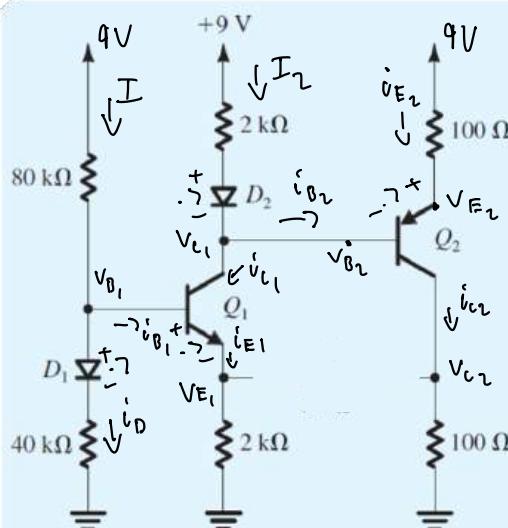

$$V_{E2} = V_{B2} + 0.7 = 5.982 \text{ [V]}$$

$$i_{E2} = \frac{q - V_{E2}}{100} = 30.18 \text{ mA}$$

$$i_{c2} = \frac{\beta}{\beta+1} i_{E2} = 29.88 \text{ mA}$$

$$V_{c2} = i_{c2} \cdot 100 = 2.98 \text{ [V]}$$

$$V_{E1} = 2k(i_{B1}(101)) = 2.444 \text{ [V]}$$

$$KCL \text{ at } V_{B1}: I = i_{B1} + i_D$$

$$i_{E1} = i_B(\beta+1) = \frac{V_{E1}}{2k} = \frac{V_{B1} - 0.7}{2k}$$

$$\frac{q - V_{B1}}{80k} = \frac{V_{B1} - 0.7}{2k(101)} + \frac{V_{B1} - 0.7}{40k}$$

$$\frac{q}{80k} + \frac{0.7}{2k(101)} + \frac{0.7}{40k} = V_{B1} \left( \frac{1}{80k} + \frac{1}{2k(101)} + \frac{1}{40k} \right)$$

$$V_{B1} = \left( \frac{q}{80k} + \frac{0.7}{2k(101)} + \frac{0.7}{40k} \right) \left( \frac{1}{80k} + \frac{1}{2k(101)} + \frac{1}{40k} \right)^{-1}$$

$$V_{B1} = 3.144$$

$$i_B = \frac{V_{B1} - 0.7}{2k(101)} = 12.1 \text{ mA} \Rightarrow i_{c1} = 1.21 \text{ mA}$$

$$KCL \text{ at } V_{c1}: I_2 = i_{c1} + i_{B2} \quad i_{B2} = \frac{i_{E2}}{\beta+1} = \frac{q - 0.7 - V_{c1}}{100(101)}$$

$$\frac{q - 0.7 - V_{c1}}{2k} = i_{c1} + i_{B2}$$


$$i_{c1} = \frac{8.3 - V_{c1}}{2k} - \frac{8.3 - V_{c1}}{100(101)}$$

$$i_{c1} - \frac{8.3}{2k} + \frac{8.3}{100(101)} = V_{c1} \left( -\frac{1}{2k} + \frac{1}{100(101)} \right) \Rightarrow$$

$$V_{c1} = \left( 1.21m - \frac{8.3}{2k} + \frac{8.3}{100(101)} \right) \left( -\frac{1}{2k} + \frac{1}{100(101)} \right)^{-1}$$

$$V_{c1} = 5.282 \text{ [V]} = V_{B2}$$

$$\beta = 100$$

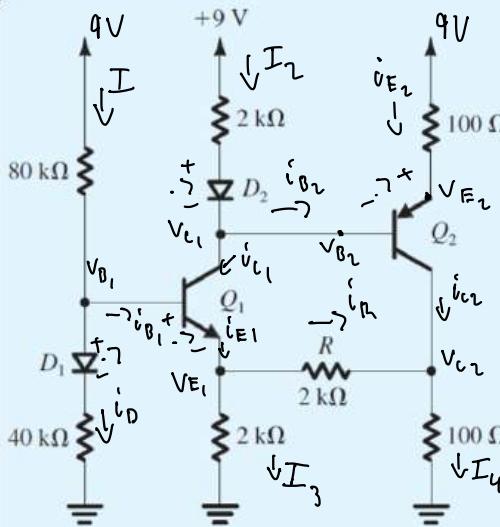

$$KCL \text{ at } V_{c1}: \frac{9 - 0.7 - V_{c1}}{2k} = i_{E1} + i_{B2}$$

$$i_{E1} = \frac{\beta}{\beta+1} i_{E2}$$

$$= \frac{100}{101} \left( \frac{V_{B1} - 0.7}{2k} + \frac{(V_{B1} - 0.7) - V_{c2}}{2k} \right)$$

$$i_{B2} = \frac{i_{E2}}{\beta+1}$$

$$= \frac{9 - 0.7 - V_{c1}}{100(101)}$$

$$\frac{V_{c1} - 8.3}{2k} + \frac{100}{101} \left( \frac{V_{B1} - 0.7}{2k} + \frac{(V_{B1} - 0.7) - V_{c2}}{2k} \right) + \frac{8.3 - V_{c1}}{100(101)} = 0$$

$$V_{c1} \left( \frac{1}{2k} - \frac{1}{100(101)} \right) + V_{B1} \left( \frac{100}{2k(101)} + \frac{100}{2k(101)} \right) - V_{c2} \left( \frac{100}{2k(101)} \right) = \frac{1.4 \cdot 100}{2k(101)} - \frac{8.3}{100(101)} + \frac{8.3}{2k}$$

$$V_{c1}(4000.98\mu) + V_{B1}(490.099\mu) - V_{c2}(495.05\mu) = 4\mu$$

$$KCL \text{ at } V_{c2}: \frac{V_{c2}}{100} = \frac{V_{E1} - V_{c2}}{2k} + i_{c2}$$

$$\frac{V_{c2}}{100} + \frac{V_{c2} - (V_{B1} - 0.7)}{2k} + \frac{V_{c1} - 8.3}{101} = 0$$

$$V_{c2} \left( \frac{1}{100} + \frac{1}{2k} \right) - V_{B1} \left( \frac{1}{2k} \right) + V_{c1} \left( \frac{1}{101} \right) = \frac{8.3}{101} - \frac{0.7}{2k}$$

$$-8.3mV_{B1} + 9.9mV_{c1} + 10.8mV_{c2} = 81.8m$$

$$KCL \text{ at } V_{B1}: \frac{9 - V_{B1}}{80k} = \frac{V_{B1} - 0.7}{40k} + i_B$$

$$i_{B1} = \frac{i_{E1}}{\beta+1} = \left( \frac{V_{E1}}{2k} + \frac{V_{E1} - V_{c2}}{2k} \right) \frac{1}{\beta+1} = \frac{1}{101} \left( \frac{V_{B1} - 0.7}{2k} + \frac{(V_{B1} - 0.7) - V_{c2}}{2k} \right)$$

$$\frac{V_{B1} - 9}{80k} + \frac{V_{B1} - 0.7}{40k} + \frac{1}{101} \left[ \frac{V_{B1} - 0.7}{2k} + \frac{V_{B1} - 0.7 - V_{c2}}{2k} \right] = 0$$

$$V_{B1} \left( \frac{1}{80k} + \frac{1}{40k} + \frac{1}{2k(101)} + \frac{1}{2k(101)} \right) - V_{c2} \left( \frac{1}{2k(101)} \right) = \frac{9}{80k} + \frac{0.7}{40k} + \frac{0.7}{2k(101)} + \frac{0.7}{2k(101)}$$

$$V_{B1}(47.401\mu) - V_{c2}(4.95\mu) = 134.931\mu$$

$$\begin{bmatrix} 47.401\mu & 0 & -4.95\mu \\ 490.099\mu & 400.099\mu & -495.05\mu \\ -8.3m & 9.9m & 10.8m \end{bmatrix}^{-1} \begin{bmatrix} 134.931\mu \\ 4\mu \\ 81.8m \end{bmatrix} = \begin{bmatrix} V_{B1} \\ V_{c1} \\ V_{c2} \end{bmatrix}$$

$$V_{B1} \approx 3.17 \text{ [V]}$$

$$V_{c1} \approx 5.55 \text{ [V]} = V_{B2}$$

$$V_{c2} \approx 2.71 \text{ [V]}$$

$$V_{E2} = V_{B2} + 0.7 = 6.25 \text{ [V]}$$


4. For the circuit shown below, find the labeled node voltages for:

a.  $\beta = \infty$

$$i_B = 0, i_C = V_E$$

$$\boxed{V_1 = 0 \text{ [V]}}$$

$$\boxed{V_2 = 0.7 \text{ [V]}}$$

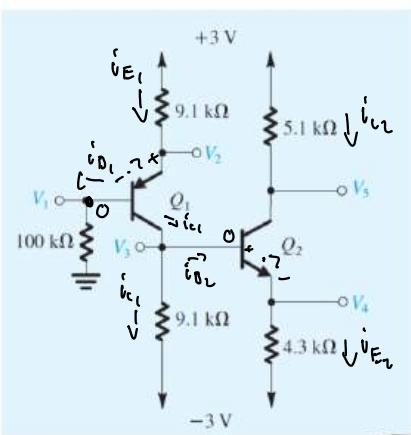

$$\frac{V_3 - (-3)}{9.1 \text{ k}\Omega} = i_{C1} = i_{E1} = \frac{3 - 0.7}{9.1 \text{ k}\Omega}$$

$$V_3 + 3 = 2.3$$


$$\boxed{V_3 = -0.7 \text{ [V]}}$$

$$V_4 = V_3 - 0.7 = -1.4 \text{ [V]}$$

$$\frac{3 - V_S}{5.1 \text{ k}\Omega} = i_{C2} = i_{E2} = \frac{V_4 + 3}{4.3 \text{ k}\Omega}$$

$$\boxed{V_S = 3 - \left(\frac{5.1}{4.3}\right)(-1.4 + 3) = 1.1 \text{ [V]}}$$

b.  $\beta = 100$

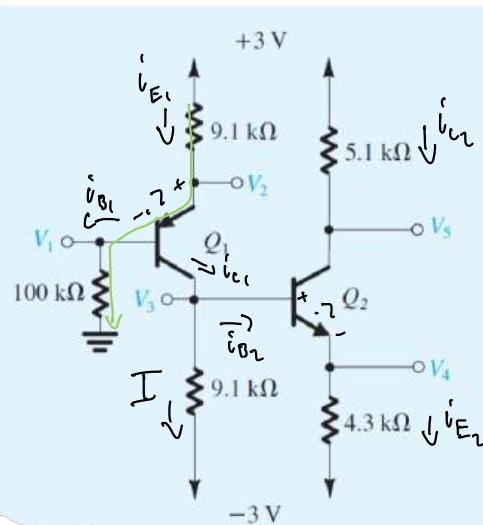

$$\boxed{V_S = V_3 - 0.7 = -1.474 \text{ [V]}}$$

KVL:  $3 - 0 = i_{E1} 9.1 \text{ k}\Omega + 0.7 + i_{B1} 100 \text{ k}\Omega$

$$2.3 = i_{B1} ((\beta + 1) 9.1 \text{ k}\Omega + 100 \text{ k}\Omega)$$

$$i_{B1} = \frac{2.3}{((100) 9.1 \text{ k}\Omega + 100 \text{ k}\Omega)} = 2.257 \text{ mA} \Rightarrow i_{E1} = i_B (\beta + 1) = 0.228 \text{ mA}$$

$$i_{C1} = \beta i_{B1} = 22.57 \text{ mA}$$

$$i_{C1} = I + i_{B2} \quad i_{B2} = \frac{i_{E2}}{\beta + 1}$$

$$i_{C1} = \frac{V_3 - (-3)}{9.1 \text{ k}\Omega} + \frac{V_3 + 2.3}{4.3 \text{ k}\Omega(100)} = \frac{V_3 - 0.7 - (-3)}{4.3 \text{ k}\Omega(100)}$$

$$i_{C1} = V_3 \left( \frac{1}{9.1 \text{ k}\Omega} + \frac{1}{4.3 \text{ k}\Omega(100)} \right) + \frac{3}{9.1 \text{ k}\Omega} + \frac{2.3}{4.3 \text{ k}\Omega(100)}$$

$$\boxed{V_3 = \frac{\left( i_{C1} - \frac{3}{9.1 \text{ k}\Omega} - \frac{2.3}{4.3 \text{ k}\Omega(100)} \right)}{\frac{1}{9.1 \text{ k}\Omega} + \frac{1}{4.3 \text{ k}\Omega(100)}} = -0.974 \text{ [V]}}$$

$$3 - V_S = i_{C2} \cdot 5.1 \text{ k}\Omega$$

$$V_S = 3 - \frac{\beta}{\beta + 1} \left( \frac{V_4 - (-3)}{4.3 \text{ k}\Omega} \right) \cdot 5.1 \text{ k}\Omega$$

$$\boxed{V_S = 1.443 \text{ [V]}}$$

5. Given the expression

$$H(j\omega) = \frac{z_1 z_2}{(1 + j \frac{\omega}{100})(1 + j \frac{\omega}{1,000})(1 + j \frac{\omega}{10,000})} = \frac{-(\frac{\omega}{100})^2}{P_1 P_2 P_3} = \left(\frac{j\omega}{100}\right)^2$$

$$j^2 \left(\frac{\omega}{100}\right) = -\left(\frac{\omega}{100}\right)$$

- (a) Find the starting slope of the Bode plot,
- (b) Find the mid-band or pass-band gain,
- (c) Determine the total phase shift,
- (d) Plot the straight-line approximation for the magnitude and phase, and
- (e) Plot the complete transfer function using your favorite software (phase and magnitude).
- (f) What happened to the  $j$  in the numerator?

a)  $|H(j\omega)| \approx \left(\frac{1}{10}\right)^2$

$$20 \log\left(\frac{1}{10}\right)^2 = 40 \log(1) - 40 \log(10)$$




$40 \text{ dB/dec}$

b)  $1K < \omega < 10K$

$$H \approx \frac{-\left(\frac{\omega}{100}\right)^2}{\left(\frac{j\omega}{100}\right)\left(\frac{j\omega}{1000}\right)(1)} = \frac{-\frac{\omega^2}{10000}}{-\frac{\omega^2}{10000}} = \frac{10000}{10000} = 10$$



$20 \log(10) = 20 \text{ dB}$

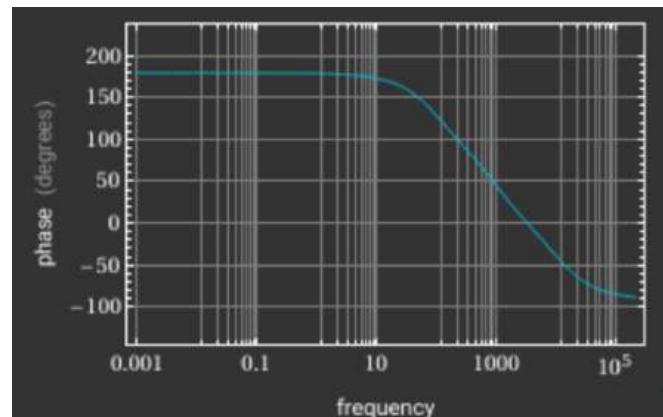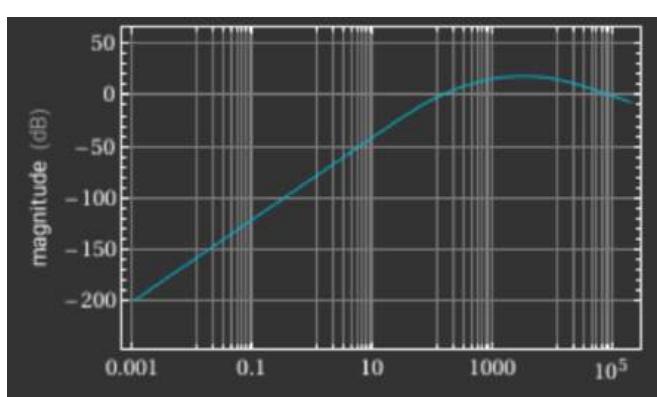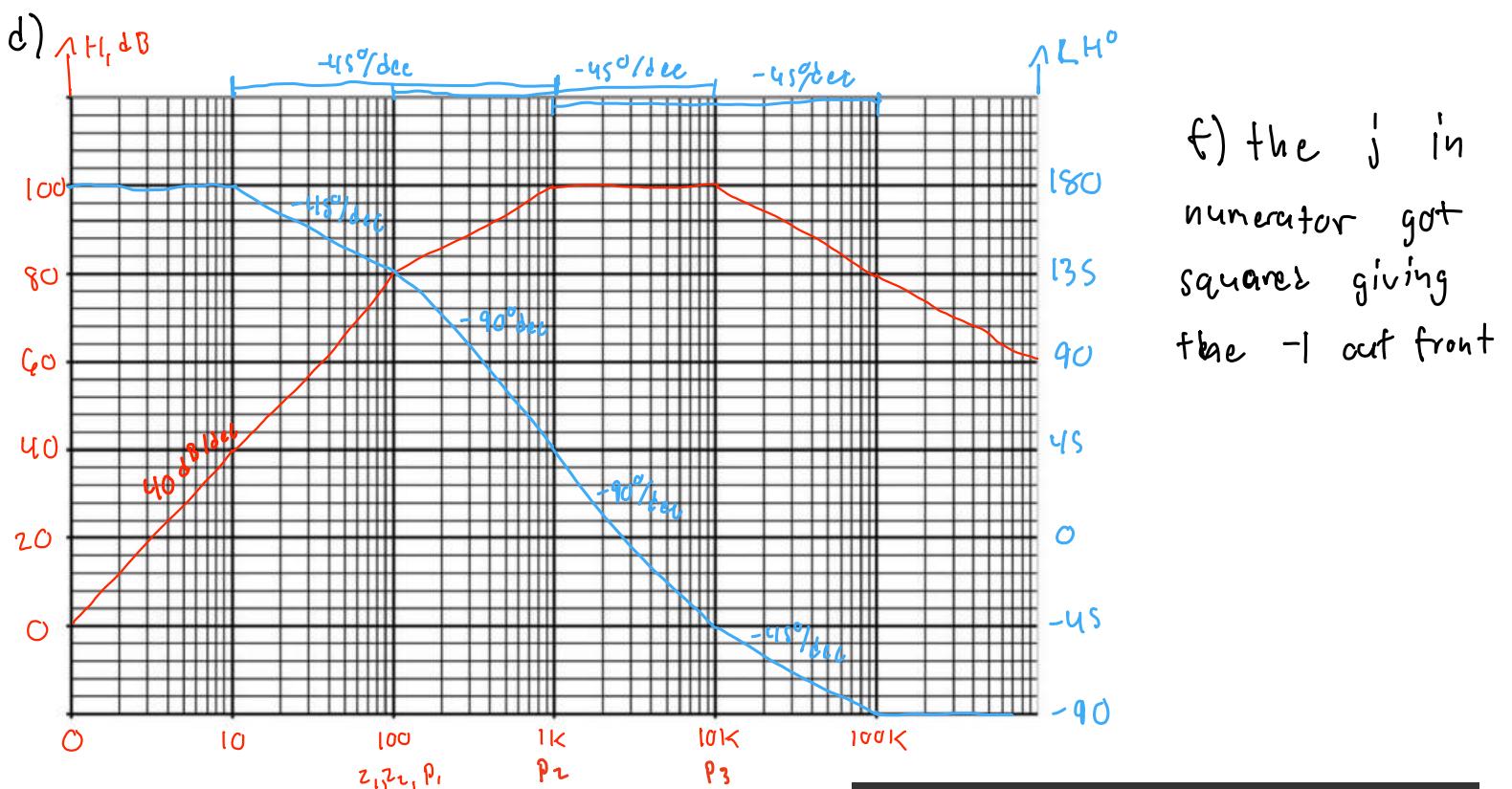c)  $+180 - \underbrace{90}_{z_1 z_2} - \underbrace{90}_{P_1} - \underbrace{90}_{P_2} - \underbrace{90}_{P_3} = -90^\circ$



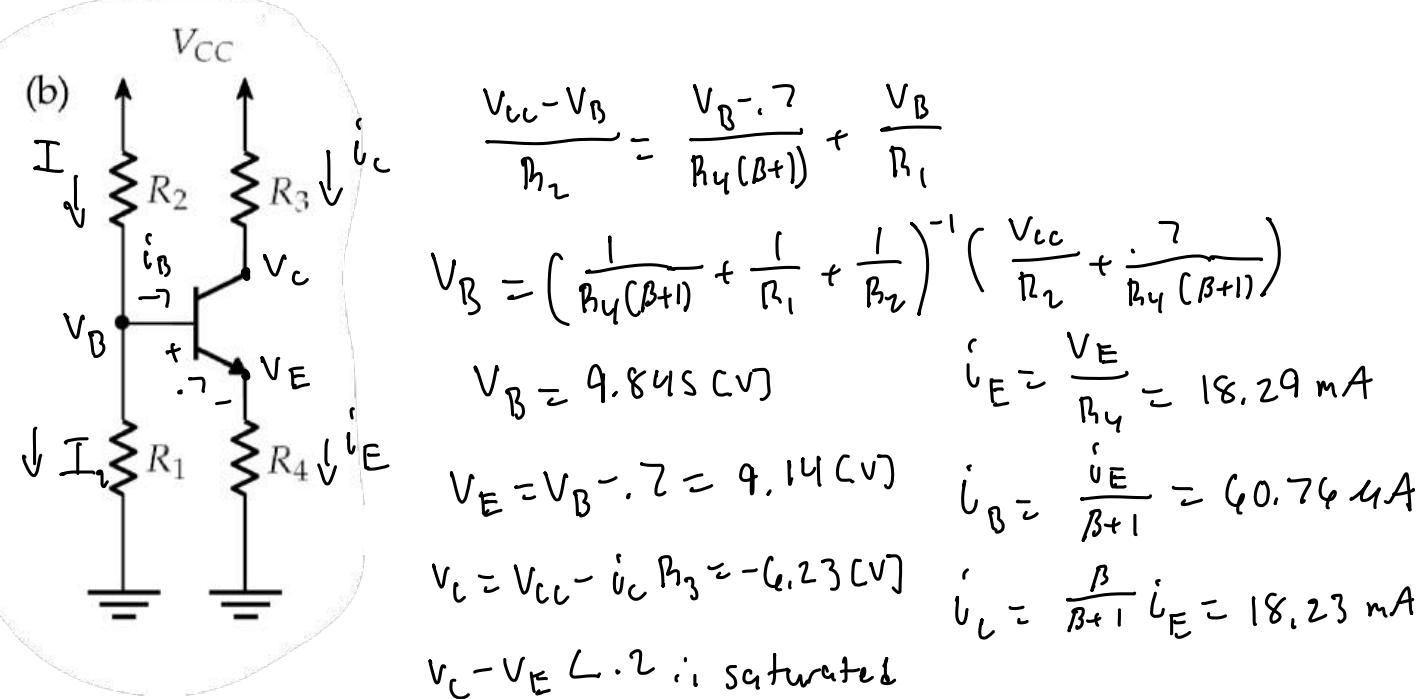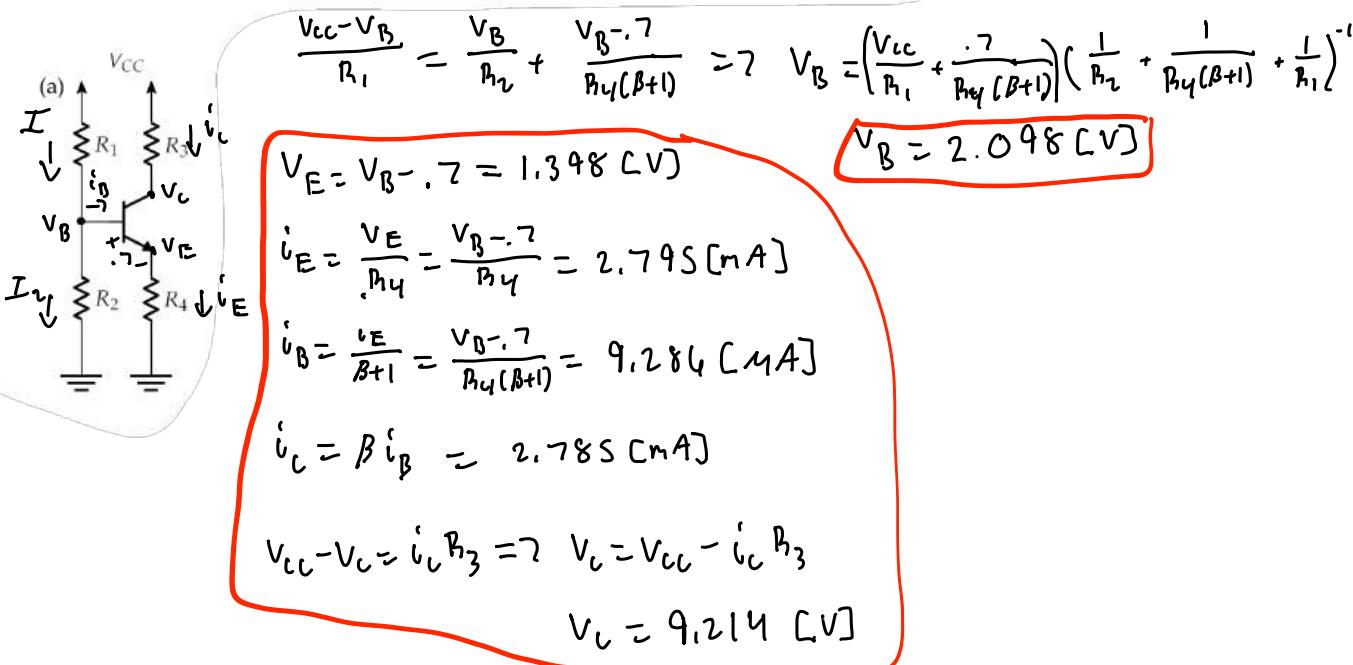6. For the following circuits, find the base, emitter, and collector voltages and currents. Use

$R_1 = 4.7 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 1 \text{ k}\Omega$ ,  $R_4 = 500 \Omega$ ,  $R_5 = 10 \text{ k}\Omega$ ,  $R_6 = 100 \text{ k}\Omega$ ,  $R_7 = 2.2 \text{ k}\Omega$ ,  $R_8 = 2.7 \text{ k}\Omega$ ,  $C_1 = 1 \mu\text{F}$ ,  $I_b = 10 \text{ mA}$ ,  $V_{CC} = +12 \text{ V}$ ,  $-V_{EE} = -12 \text{ V}$ , and  $\beta = 300$ .



$$V_C - V_E = 0.2 \text{ [V]}$$

$$V_E = V_B - .7$$

$$i_E = i_C + i_B$$

$$i_E = \frac{V_E}{R_4} = \frac{V_B - .7}{R_4}$$


$$i_C = \frac{V_{CC} - V_C}{R_3}$$

$$\frac{V_B - .7}{i_E} = \frac{V_{CC} - (.2 + (V_B - .7))}{R_3} + \left( \frac{V_{CC} - V_B}{R_2} - \frac{V_B}{R_1} \right)$$

$$V_B \left( \frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_1} \right) = V_{CC} \left( \frac{1}{R_3} + \frac{1}{R_2} \right) + \frac{.7}{R_4} + \frac{.5}{R_3}$$

$$V_B = \left( \frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_1} \right) V_{CC} \left( \frac{1}{R_3} + \frac{1}{R_2} \right) + \frac{.7}{R_4} + \frac{.5}{R_3}$$
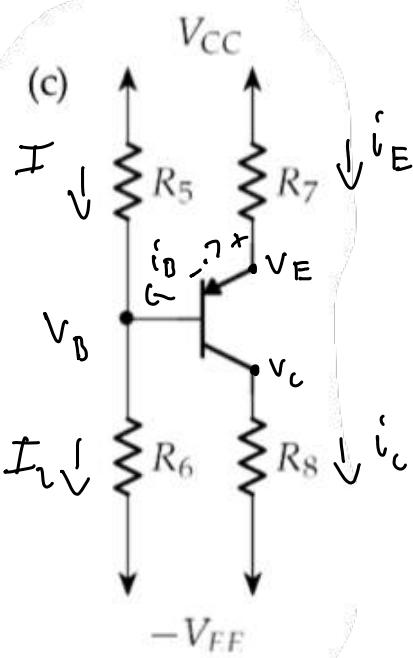
$$V_B = 6.148 \text{ [V]} \quad V_E = 5.448 \quad V_C = 5.448 \quad i_E = 10.9 \text{ mA} \quad i_C = 6.35 \text{ mA} \quad i_B = 4.54 \text{ nA}$$



$$\frac{V_{CC} - V_B}{R_S} + i_B = \frac{V_B - V_{EE}}{R_4}$$

$$i_B = \frac{i_E}{\beta+1} = \frac{V_{CC} - V_E}{R_7(\beta+1)} = \frac{V_{CC} - (V_B + 0.7)}{R_7(\beta+1)}$$

$$\frac{V_{CC} - V_B}{R_S} + \frac{V_{CC} - (V_B + 0.7)}{R_7(\beta+1)} = \frac{V_B - V_{EE}}{R_4}$$

$$V_B \left( \frac{1}{R_4} + \frac{1}{R_7(\beta+1)} + \frac{1}{R_S} \right) = V_{CC} \left( \frac{1}{R_S} + \frac{1}{R_7(\beta+1)} \right) - \frac{0.7}{R_7(\beta+1)} + \frac{V_{EE}}{R_4}$$

$$V_B = 9.84 \text{ [V]}$$

$$i_B = \frac{i_E}{\beta+1} = 2.21 \text{ mA}$$


$$V_E = V_B + 0.7 = 10.54 \text{ [V]}$$

$$i_E = \frac{V_{CC} - V_E}{R_7} = 644.4 \text{ mA}$$

$$V_C = V_{EE} + i_C R_8$$

$$i_C = \frac{\beta}{\beta+1} i_E = 642.23 \text{ mA}$$

$$V_C = -10.21 \text{ [V]}$$

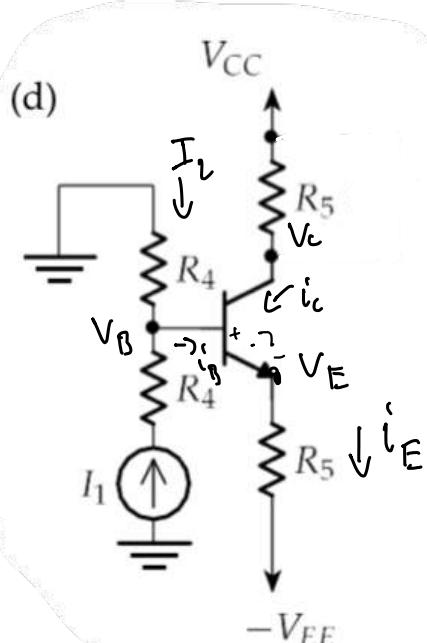

$C_L = \text{Open in dc}$

$$\frac{-V_B}{R_4} + I_1 = i_B$$

$$i_B = \frac{i_E}{\beta+1} = \frac{V_E - V_{EE}}{R_5(\beta+1)} = \frac{(V_B - 0.7) - V_{EE}}{R_5(\beta+1)}$$

$$\frac{(V_B - 0.7) - V_{EE}}{R_5(\beta+1)} + \frac{V_B}{R_4} = I_1$$

$$V_B \left( \frac{1}{R_5(\beta+1)} + \frac{1}{R_4} \right) = I_1 + \frac{V_{EE}}{R_5(\beta+1)} + \frac{0.7}{R_5(\beta+1)}$$

$$V_B = \left( \frac{1}{R_5(\beta+1)} + \frac{1}{R_4} \right)^{-1} \left( I_1 + \frac{V_{EE}}{R_5(\beta+1)} + \frac{0.7}{R_5(\beta+1)} \right)$$

$$V_B = 4.997 \text{ [V]}$$

$$V_E = V_B - 0.7 = 4.297 \text{ [V]}$$

$$i_E = \frac{V_E - V_{EE}}{R_5} = 1.43 \text{ mA}$$

$$i_E = i_C + i_B$$

$$i_E = \frac{V_E - V_{EE}}{R_5} = \frac{V_B - 0.7 - V_{EE}}{R_5}$$

$$i_B = \frac{-V_B}{R_4} + I_1$$

$$i_B = \frac{V_{CC} - V_C}{R_S} = \frac{V_{CC} - (I_1 + V_E)}{R_S} = \frac{V_{CC} - (I_1 + (V_B - 0.7))}{R_S}$$

$$\frac{V_B - 0.7 - V_{EE}}{R_5} = \frac{V_{CC} - (I_1 + (V_B - 0.7))}{R_S} + \frac{-V_B}{R_4} + I_1$$

$$V_B \left( \frac{1}{R_S} + \frac{1}{R_5} + \frac{1}{R_4} \right) = \frac{V_{CC}}{R_S} + \frac{0.7}{R_S} + \frac{V_{EE}}{R_S} + I_1$$

$$V_B = 4.46 \text{ [V]} \quad V_E = 3.9 \text{ [V]} \quad V_C = 4.7 \text{ [V]}$$

$V_C - V_E < 2 \therefore \text{saturated}$


$$i_B = 0.782 \text{ mA}$$

$$i_E = 1.59 \text{ mA}$$

$$i_C = 0.799 \text{ mA}$$

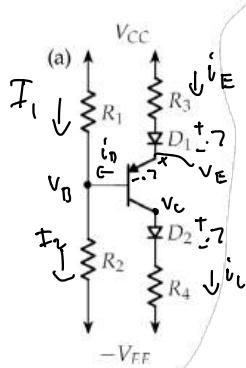7. For the following circuits, find the base, emitter, and collector voltages and currents. Use

$R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 1 \text{ k}\Omega$ ,  $R_3 = 3.3 \text{ k}\Omega$ ,  $R_4 = 5 \text{ k}\Omega$ ,  $R_5 = 10 \text{ k}\Omega$ ,  $R_6 = 1 \text{ k}\Omega$ ,  $I_b = 1 \text{ mA}$ ,  $V_{CC} = +10 \text{ V}$ ,  $-V_{EE} = -10 \text{ V}$ , and  $\beta = 150$ . Use a constant voltage drop model for the diodes with a forward bias potential of 0.7 V.



$$V_{CC} - V_B = i_E R_3 + 0.7 + 0.7$$

$$V_B = V_{CC} - i_E R_3 - 0.7 - 0.7$$

$$V_B = 8.4 - i_E R_3$$

$$V_B = 8.4 - (\beta + 1) i_B R_3$$

$$V_B = 8.4 \text{ mV}$$

$$V_E = V_B + 0.7 = 0.709 \text{ V}$$

$$V_C - V_{EE} = 0.7 + i_C R_4$$

$$V_C = V_{EE} + 0.7 + i_C R_4$$

$$V_C = 3.431 \text{ V}$$

$$i_B = \frac{V_B - V_{EE}}{R_2} = \frac{V_{CC} - V_B}{R_1}$$

$$(i_B = V_B \left( \frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{V_{CC}}{R_1} - \frac{V_{EE}}{R_2}) / 1\text{k}$$

$$1\text{k} i_B = 2V_B - 10 - (-10)$$

$$1\text{k} i_B = 2(8.4 - 498300 i_B)$$


$$996600 i_B = 17.2$$

$$996600 i_B = 17.2$$

$$i_B = 17.24 \mu\text{A}$$

$$i_E = (\beta + 1) i_B = 2.603 \text{ mA}$$

$$i_C = \beta i_B = 2.586 \text{ mA}$$

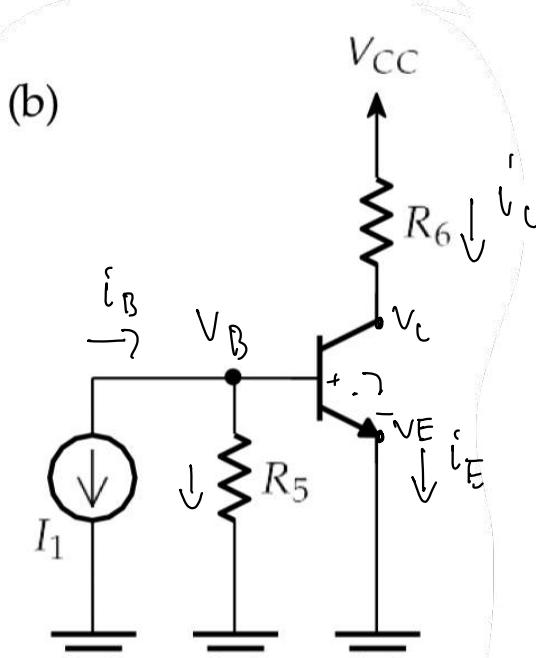

$$V_E = 0$$

$$V_B = V_E + 0.7 = 0.7 \text{ V}$$

$$i_B = -I - \frac{V_B}{R_S}$$

$i_B = -1.07 \text{ mA} < 0 \therefore \text{cutoff}$

$$\text{so } i_B = i_C = i_E = 0$$


$$V_B + I_1 R_S = 0$$

$$V_B = -I_1 R_S$$

$$V_B = -10 \text{ V}$$

$$V_E = 0$$
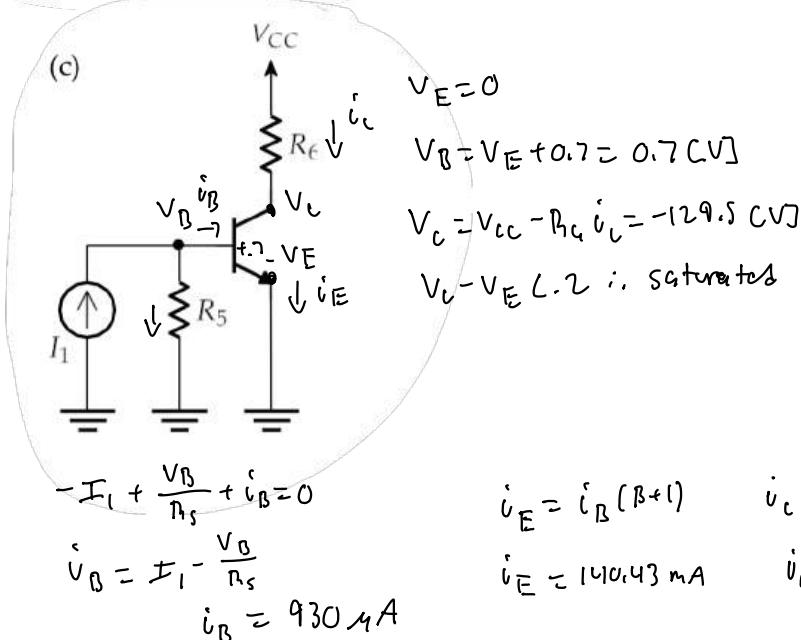
$$V_C = V_{CC} - i_C R_4 \Rightarrow V_C = 10 \text{ V}$$



$$V_E = 0$$

$$V_B = V_E + 0.7 = 0.7 \text{ V}$$

$$V_C = V_{CC} - R_4 i_C = -129.5 \text{ V}$$

$$V_C - V_E < 0.2 \therefore \text{saturated}$$

$$i_E = i_C + i_B$$

$$i_E = \frac{V_{CC} - V_C}{R_4} + I_1 - \frac{V_B}{R_S}$$

$$i_E = 10.73 \text{ mA}$$

$$i_C = \frac{V_{CC} - V_C}{R_4} = 9.8 \text{ mA}$$

$$i_B = 0.93 \text{ mA}$$

$$V_C - V_E = 0.2$$

$$V_B - V_E = 0.7$$

$$V_E = 0$$

$$V_C = 0.2$$

$$V_B = 0.7$$

$$i_E = i_B (\beta + 1)$$

$$i_E = 1410.43 \text{ mA}$$

$$i_C = \beta i_B$$

$$i_C = 139.5 \text{ mA}$$

$$i_B = 930 \mu\text{A}$$