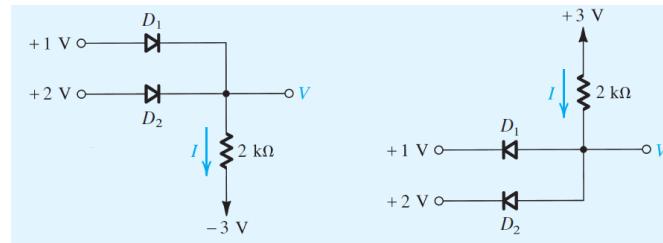



Homework 7

Topic: Diodes I


1. For the circuits shown below using ideal diodes, find the values of the labeled voltages and currents.



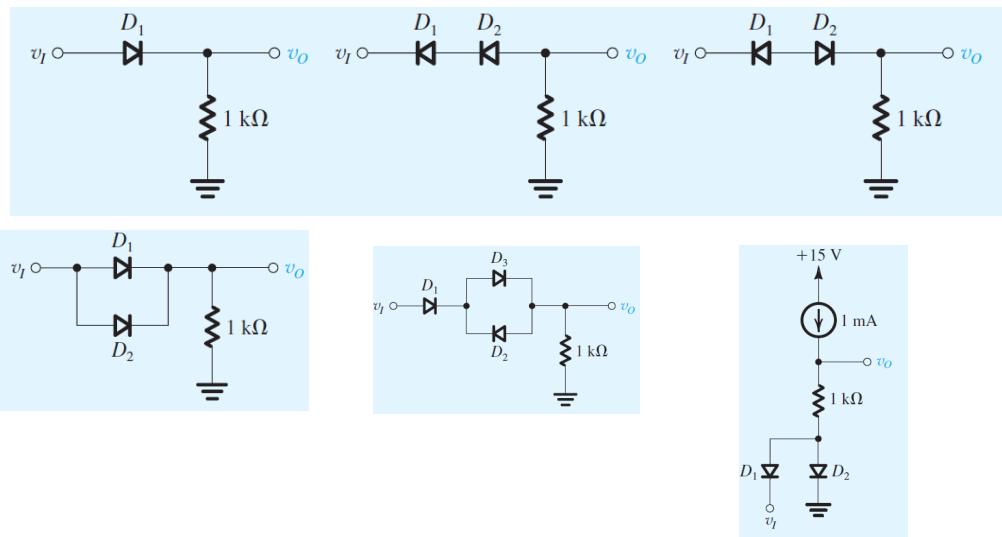
2. In each of the ideal-diode circuits shown below, v_I is a 1-kHz, 5-V peak sine wave. Sketch the waveform resulting at v_O . What are its positive and negative peak values?



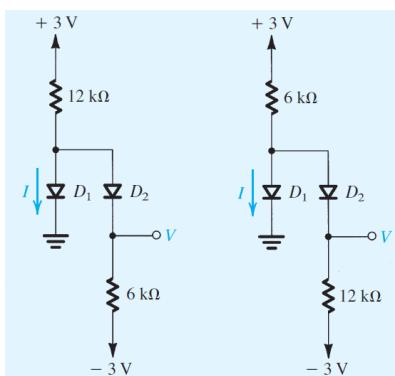
3. Assuming that the diodes in the circuits below are ideal, find the values of the labeled voltages and currents.



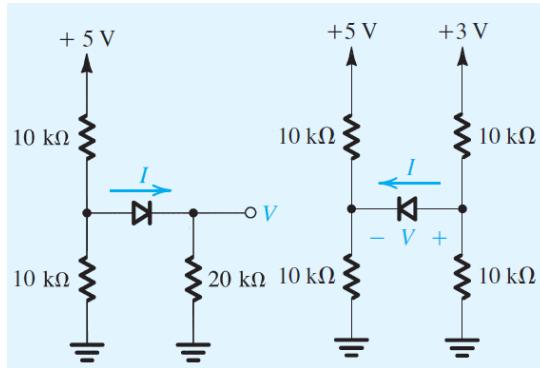
4. Assuming that the diodes in the circuits below are ideal, utilize Thevenin's theorem to simplify the circuits and thus find the values of the labeled currents and voltages.



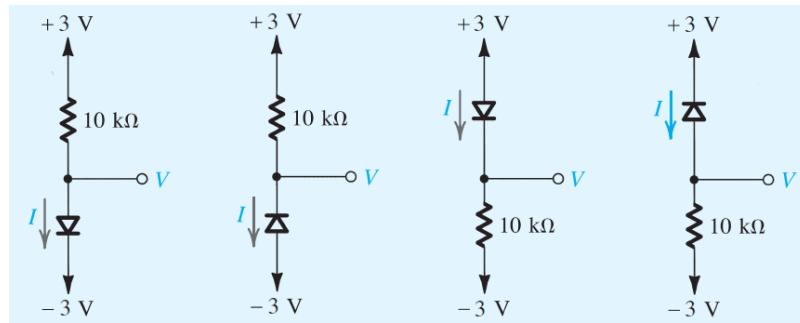5. For the circuits shown below, using the constant-voltage-drop ($V_D = 0.7 \text{ V}$) diode model, find the voltages and currents indicated.




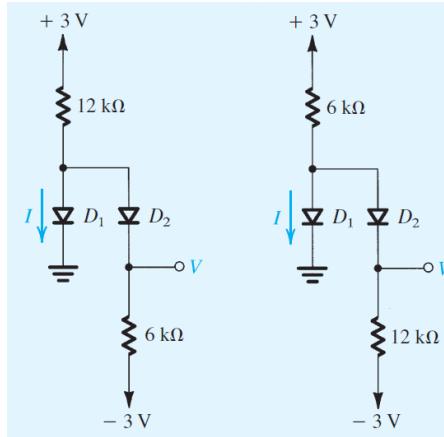6. For the circuits below, using the constant-voltage-drop ($V_D = 0.7 \text{ V}$) diode model, find the values of the labeled currents and voltages.



7. Repeat problems 3 and 4 using a piecewise linear diode model with $V_f = 0.6 \text{ V}$, $r_d = 1 \text{ k}\Omega$, and no reverse bias current.

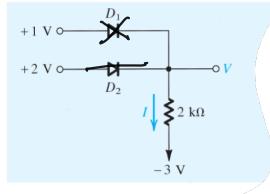1. For the circuits shown below using ideal diodes, find the values of the labeled voltages and currents.



$$V_{D_1} = V_{D_1^+} - V_{D_1^-} = 1 - (-3) = 4$$

$$V_{D_2} = 2 - (-3) = 5 \text{ on}$$

$$V = IR$$

$$I = \frac{V - (-3)}{2k\Omega}$$

$$I = \frac{2 + 3}{2k\Omega}$$


$$I = 2.5 \text{ mA}$$

$$V = V_{D_1} = 1 - 2 = -1 \text{ off}$$

$$D_2 \rightarrow \text{FB}$$

$$D_1 \rightarrow \text{RB}$$

$$V = V_{D_2} = 2 \text{ on}$$

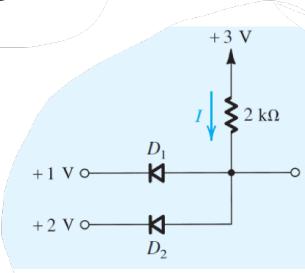

$$V_{D_1} = 3 - 1 = 2 \text{ on}$$


$$V_{D_2} = 3 - 2 = 1$$

$$D_1 \rightarrow \text{FB}$$

$$V = V_{D_1} = 1 \text{ V}$$

$$I = \frac{3 - V}{2k\Omega} = \frac{2}{2k\Omega} = 1 \text{ mA}$$

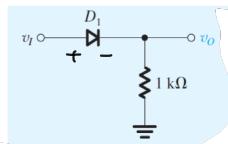2. In each of the ideal-diode circuits shown below, v_i is a 1-kHz, 5-V peak sine wave. Sketch the waveform resulting at v_o . What are its positive and negative peak values?





$$V_I > 0 \quad D_1 \rightarrow \text{FB}$$


$$V_I < 0 \quad D_1 \rightarrow \text{RB}$$

$$V_{o,\text{peak}} = 5 \text{ V}$$

$$V_{o,\text{min}} = 0 \text{ V}$$

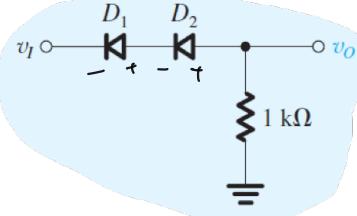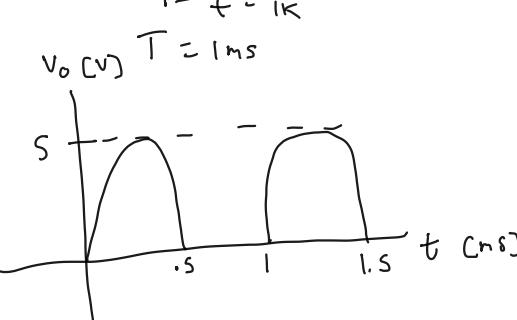
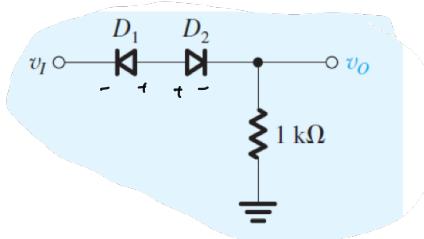
$$V_I < 0 \quad D_1, D_2 \rightarrow \text{FB}$$





$$V_I > 0$$

$$V_I > 0 \quad D_1, D_2 \rightarrow \text{RB}$$


$$V_{o,\text{max}} = 0 \text{ V}$$

$$V_{o,\text{min}} = -5 \text{ V}$$

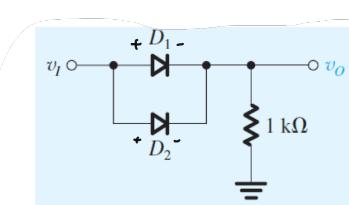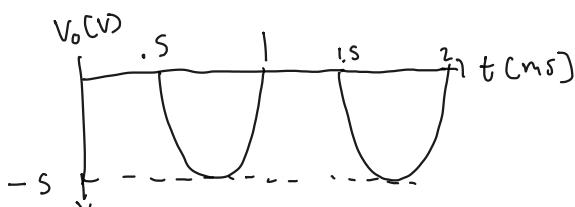

$$V_I > 0$$

$$V_I < 0$$

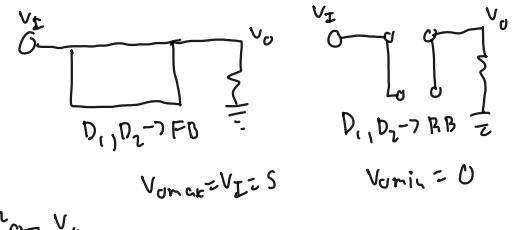










$$V_I < 0$$

$$D_1 \rightarrow \text{FB}$$




$$D_2 \rightarrow \text{FB}$$
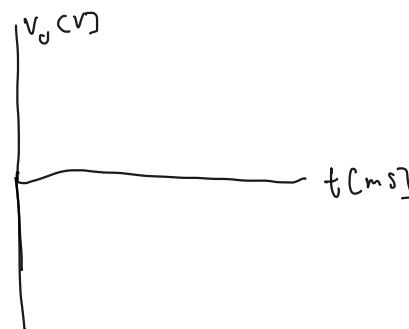
$$\therefore V_{o,\text{max}} = 0 = V_{o,\text{min}}$$



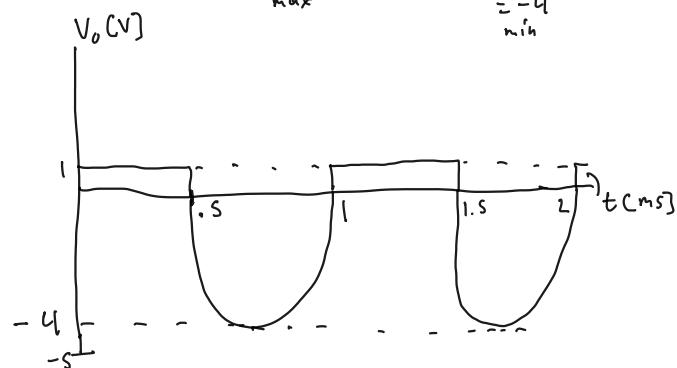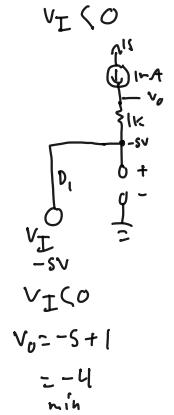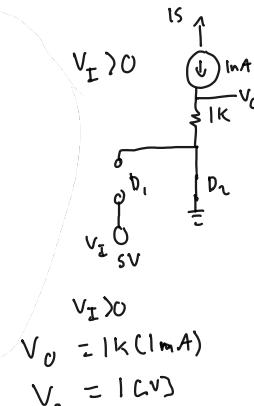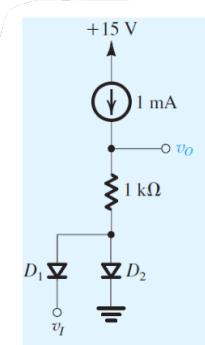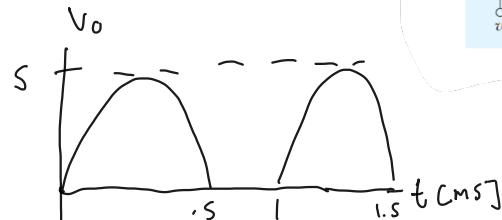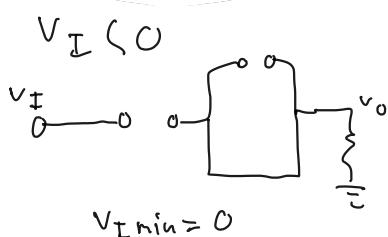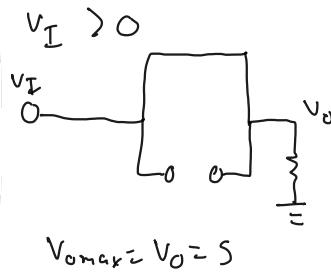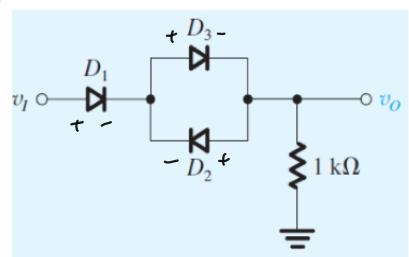

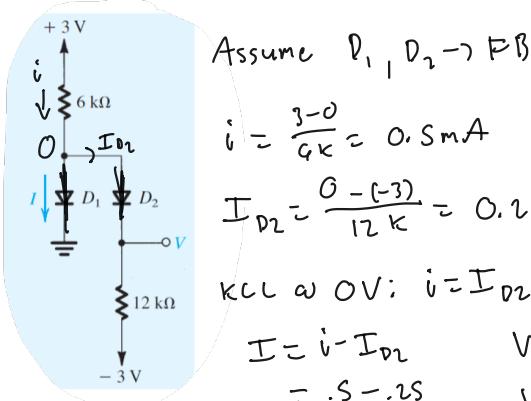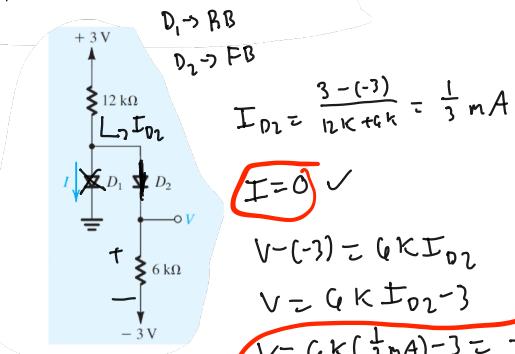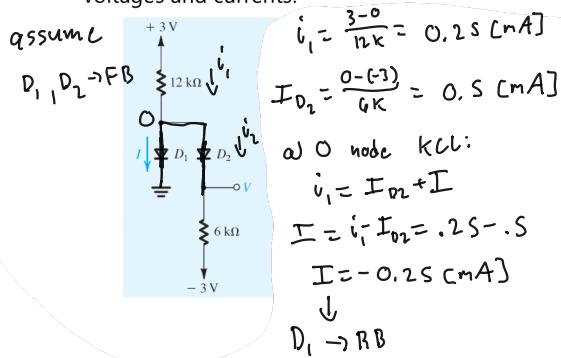3. Assuming that the diodes in the circuits below are ideal, find the values of the labeled voltages and currents.




$$V - (-3) = I_{D2} 12k$$

$$V = 12k(0.25) - 3$$

$$V = 0$$
 ✓

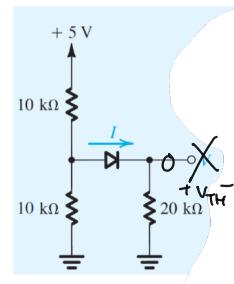4. Assuming that the diodes in the circuits below are ideal, utilize Thevenin's theorem to simplify the circuits and thus find the values of the labeled currents and voltages.



$$V_{TH} = S \left(\frac{10k}{10k+10k} \right) = S \left(\frac{1}{2} \right) = 2.5 \text{ [V]}$$

Preq:

$$\begin{aligned} & \text{---} \\ & | 10k \\ & \text{---} \\ & | 10k \quad R_{TH} = 5k \end{aligned}$$


$$I = \frac{V_{TH}}{R_{TH} + 20k} = \frac{2.5}{25k}$$

$$I = 0.1 \text{ mA}$$

$$V = V_{TH} \left(\frac{20k}{10k+20k} \right) = 2.5 \left(\frac{20k}{25k} \right)$$

$$V = 2 \text{ [V]}$$

$$\begin{aligned} V_{TH}^- &= S \\ & \text{---} \\ & | 10k \\ & \text{---} \\ & | 10k \quad R_{TH}^- = 10k \parallel 10k = 5k \Omega \end{aligned}$$

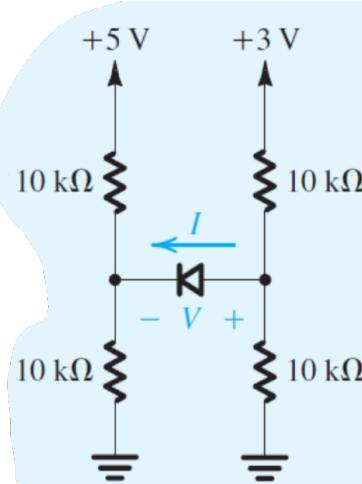

$$V_{TH}^+ = 3 \left(\frac{10k}{20k} \right) = 1.5 \text{ [V]}$$

$$R_{TH}^+ = 10k \parallel 10k = 5k \Omega \Rightarrow$$

$$\begin{aligned} & \text{---} \\ & | 5k \quad I \quad 5k \\ & \text{---} \\ & | 0k \quad -V + \quad R_{TH}^+ \\ & \text{---} \\ & | 2.5 \quad V_{TH}^+ \quad 1.5 \end{aligned}$$

$$R_{TH}^+ = 10k \parallel 10k = 5k \Omega$$

since voltage lower
on anode side



$$D \rightarrow R_B$$

$$\therefore I = 0$$

$$V = 1.5 - (2.5)$$

$$V = -1 \text{ [V]}$$

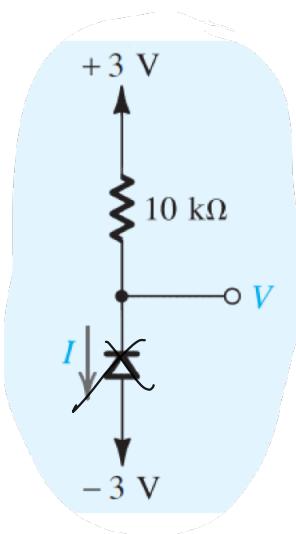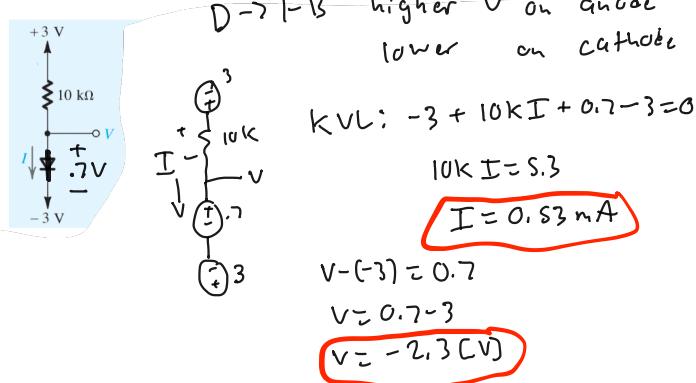
5. For the circuits shown below, using the constant-voltage-drop ($V_D = 0.7 \text{ V}$) diode model, find the voltages and currents indicated.



Anode at low V
cathode at higher V
 $\therefore D \rightarrow R-B$

$$I = 0 \text{ (A)}$$

$$V = 3 \text{ [V]}$$

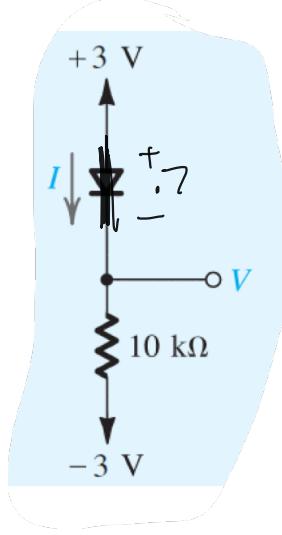

KVL: $-3 + .7 + I 10k - 3 = 0$


$I 10k = 5.3$

$I = 0.53 \text{ mA}$

$V - (-3) = I 10k$


$V = 10k(0.53\text{mA}) - 3$

$V = 2.3 \text{ [V]}$

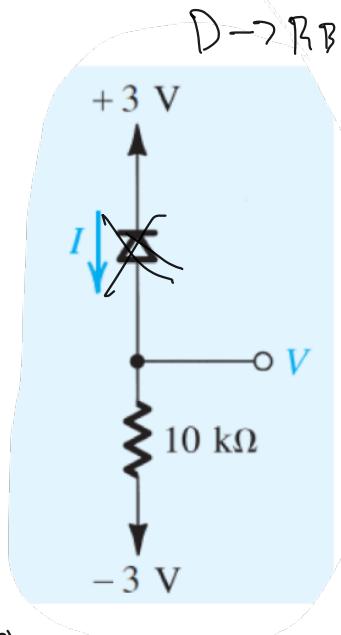

6. For the circuits below, using the constant-voltage-drop ($V_D = 0.7 \text{ V}$) diode model, find the values of the labeled currents and voltages.

Assume
 $D_1, D_2 \rightarrow FB$

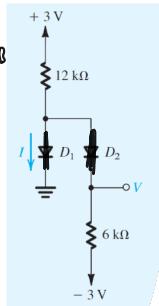

$$i = \frac{3 - 0.7}{12k} = 0.19 \text{ mA}$$

$$I_{D2} = \frac{0.7 - 0.7 - (-3)}{6k}$$

$$I_{D2} = 0.5 \text{ mA}$$


$$I = i - I_{D2}$$

$$= .19 - 0.5$$

$$I = -.31 \times$$

$$I = 0 \text{ A}$$

$$V = -3 \text{ [V]}$$

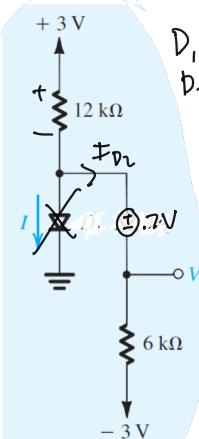


$$I_{D2} = \frac{3 - 0.7 - (-3)}{12k + 6k}$$

$$I_{D2} = 0.29 \text{ mA}$$

$$V = 3 - 12k I_{D2} - 0.7$$

$$V = 2.3 - 12k(0.29)$$

$$V = -1.23 \text{ [V]}$$

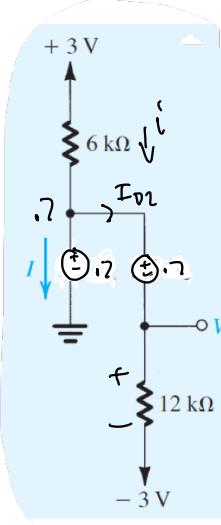

$$I_{D2} = \frac{0.7 - 0.7 - (-3)}{12k}$$

$$I_{D2} = 0.25 \text{ mA}$$

$$i = \frac{3 - 0.7}{6k} = 0.3833 \text{ mA}$$

$$I = i - I_{D2} = 0.3833 - 0.25$$


$$I = 0.133 \text{ mA}$$

$$V - (-3) = I_{D2} 12k$$

$$V = 12k I_{D2} - 3$$

$$V = 0 \text{ [V]}$$

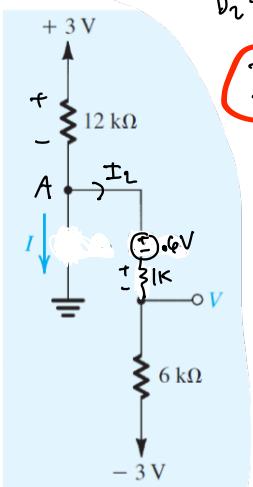7. Repeat problems 3 and 4 using a piecewise linear diode model with $V_f = 0.6 \text{ V}$, $r_d = 1 \text{ k}\Omega$, and no reverse bias current.



$D_1 \rightarrow RB$

$D_2 \rightarrow FB$

$$I = 0$$

$$I_2 = \frac{3 - 0.6 - (-3)}{12\text{k} + 1\text{k} + 6\text{k}} = 0.28 \text{ mA}$$

$$\frac{3 - V_A}{12\text{k}} = I_2$$

$$3 - V_A = 12\text{k}I_2$$

$$V_A = -0.41$$

$$V_A - V = 0.6 + I_2 1\text{k}$$

$$V = V_A - 0.6 - 1\text{k}I_2$$

$$V = -1.295 \text{ [V]}$$

$D_1, D_2 \rightarrow FB$

$$i = I_2 + I$$

$$\left(\frac{3 - V_A}{6\text{k}} = \frac{V_A - 0.6}{1\text{k}} + \frac{V_A - 0.6 - (-3)}{13\text{k}} \right) 28\text{k}$$

$$39 - 13V_A = 78V_A - 44.8 + 6V_A + 14.4$$

$$92V_A = 71.4$$

$$V_A = 0.734 > V_{T1}, V_{T2} \checkmark$$

$$I = \frac{V_A - 0.6}{1\text{k}}$$

$$I = 0.134 \text{ mA}$$

$$I_2 = \frac{V_A - 0.6 + 3}{13\text{k}}$$

$$V_A - V = 0.6 + I_2 1\text{k}$$



$$V = V_A - 0.6 - 1\text{k} \left(\frac{V_A + 2.4}{13\text{k}} \right)$$

$$V = -0.105 \text{ [V]}$$

U.

From U; $V_{TH} = 2.5 \text{ [V]}$

$R_{TH} = 5\text{k}$ $D \rightarrow FB$

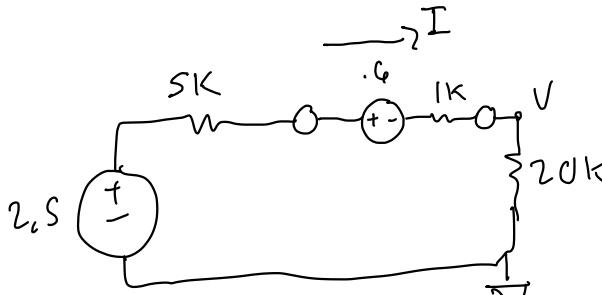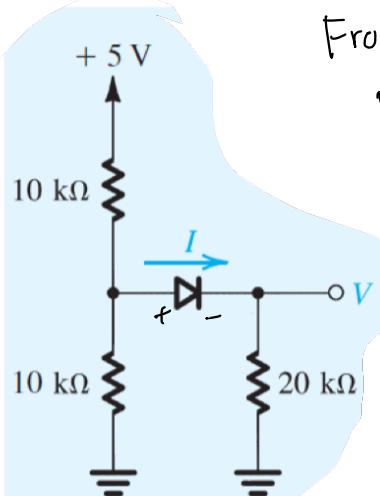



$$I = \frac{2.5 - 0.6}{5\text{k} + 1\text{k} + 20\text{k}}$$

$$I = 0.0231 \text{ mA}$$

$$V - 0 = 20\text{k}I$$


$$V = 20\text{k}(0.0231)^{\text{(n)}}$$

$$V = 1.462 \text{ [V]}$$

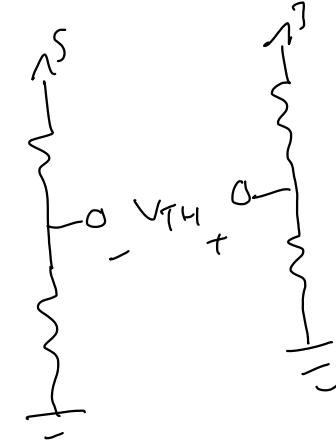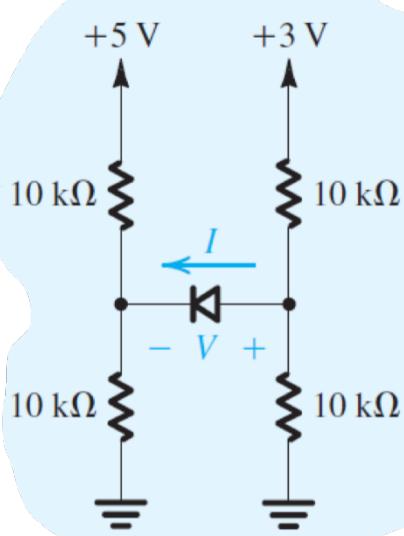

$$V_{TH} = 2.5$$

$$R_{TH} = 5\text{k}$$

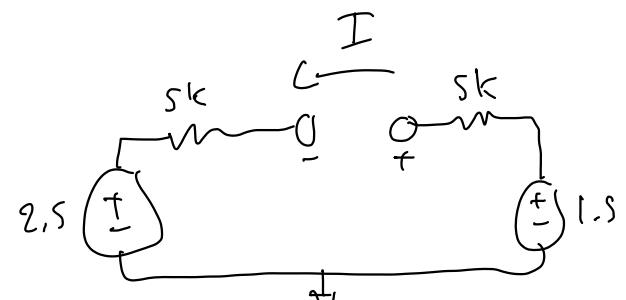

since voltage lower
on anode side $D \rightarrow RB$
and "open"

$$I = 0A \quad V = -1 \text{ [V]}$$