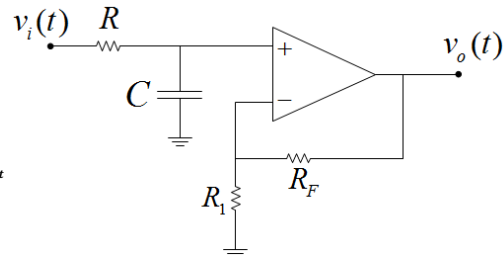
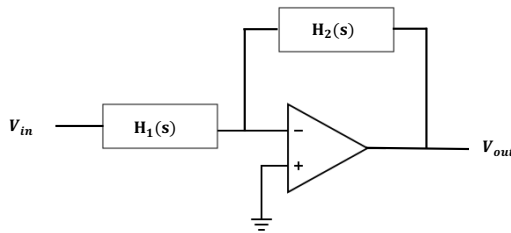


1. (40 points) For the following operational amplifier circuits:



- (5 points) Indicate whether or not each circuit has dc negative feedback. If not directly clear, indicate the conditions that will guarantee dc negative feedback.
- (10 points) determine the voltages and currents at the op-amp inputs
- (10 points) Determine the transfer function $\mathbf{H(s)} = \frac{\mathbf{V_o(s)}}{\mathbf{V_i(s)}}$.
- (15 points) For the input signal $v_i(t) = te^{-t} \sin(t) u(t)$ and $R_F = R_1 = R = 1 \Omega$, $C = 1 F$, calculate the \mathbf{s} -domain output $\mathbf{V_o(s)}$ for the second circuit.

2. (30 points) By combining the basic circuits in Table 4-3 of your textbook, devise an op-amp circuit that performs the following signal calculation:

$$y(t) = -x_1(t) + \frac{dx_2(t)}{dt} + \int_{0-}^t x_3(\tau) d\tau$$

3. (30 points) Compute the transfer function $\mathbf{H(s)} = \mathbf{Y(s)} / \mathbf{X(s)}$ for the block diagram below.

