

$$Z_1 = 6000$$


$$\rho_1 = 300$$

$$\rho_2 = 40000$$

1.)


$$|H(j\omega)| \text{ [dB]}$$
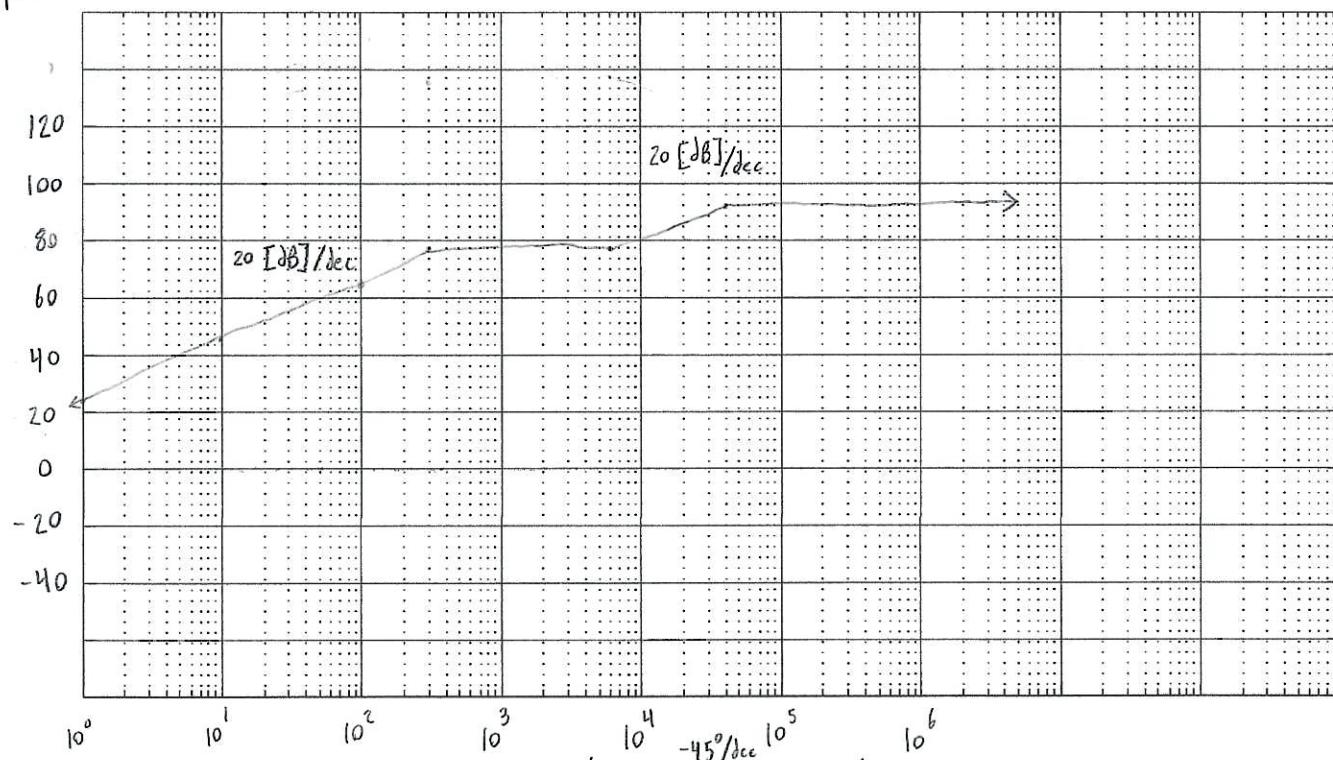
$$\omega_o = 1 \quad H(j1) = \frac{-j20}{1} \Rightarrow 20 \log(H(j1)) = 26 \text{ [dB]} \quad \phi = -90^\circ$$



$$\phi \text{ [deg]}$$
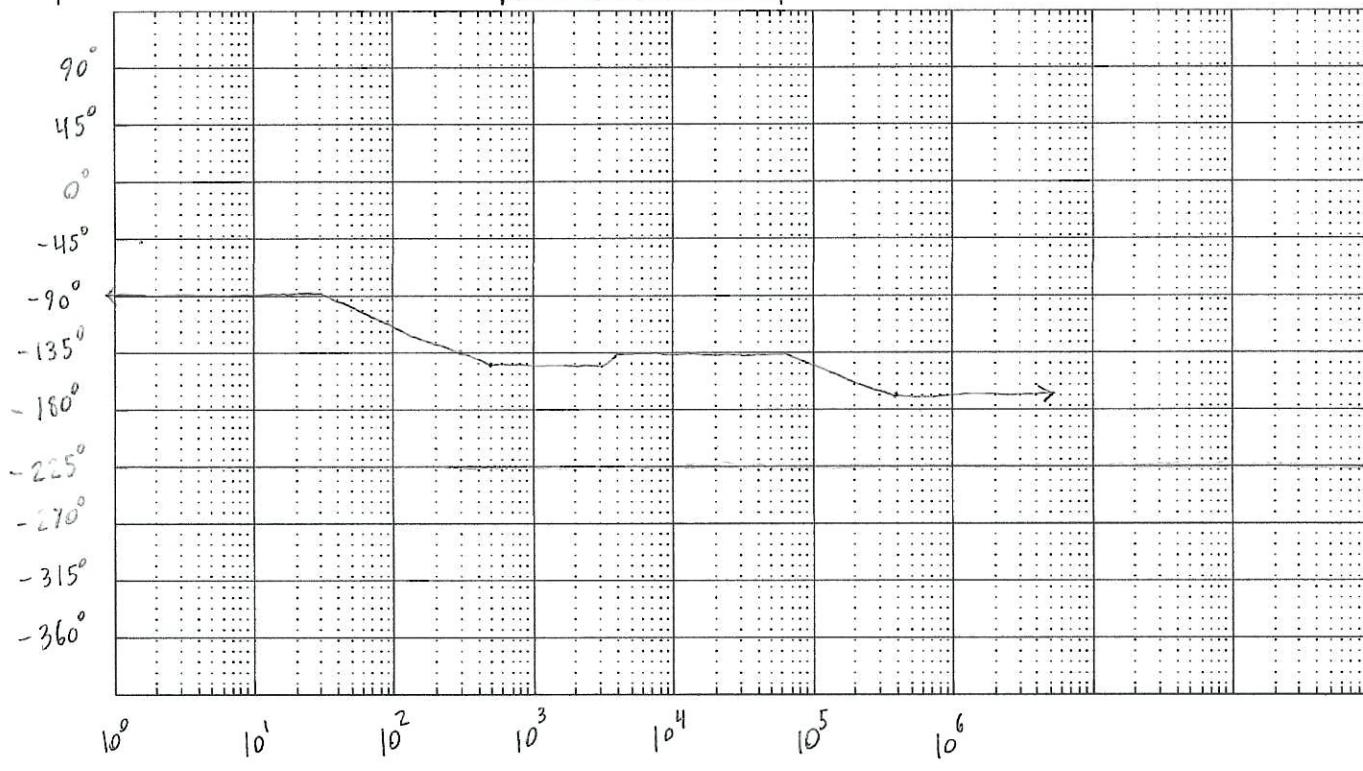
$$-45^\circ/\text{dec} \quad 45^\circ/\text{dec}$$





2.)

$$\omega_0 = 30 \quad H(j\omega) = -30^\circ \Rightarrow 29.5 [\text{dB}]$$


$$Z_1 = Z_2 = 300$$

$$P_1 = 5000$$

$$P_2 = 60000$$

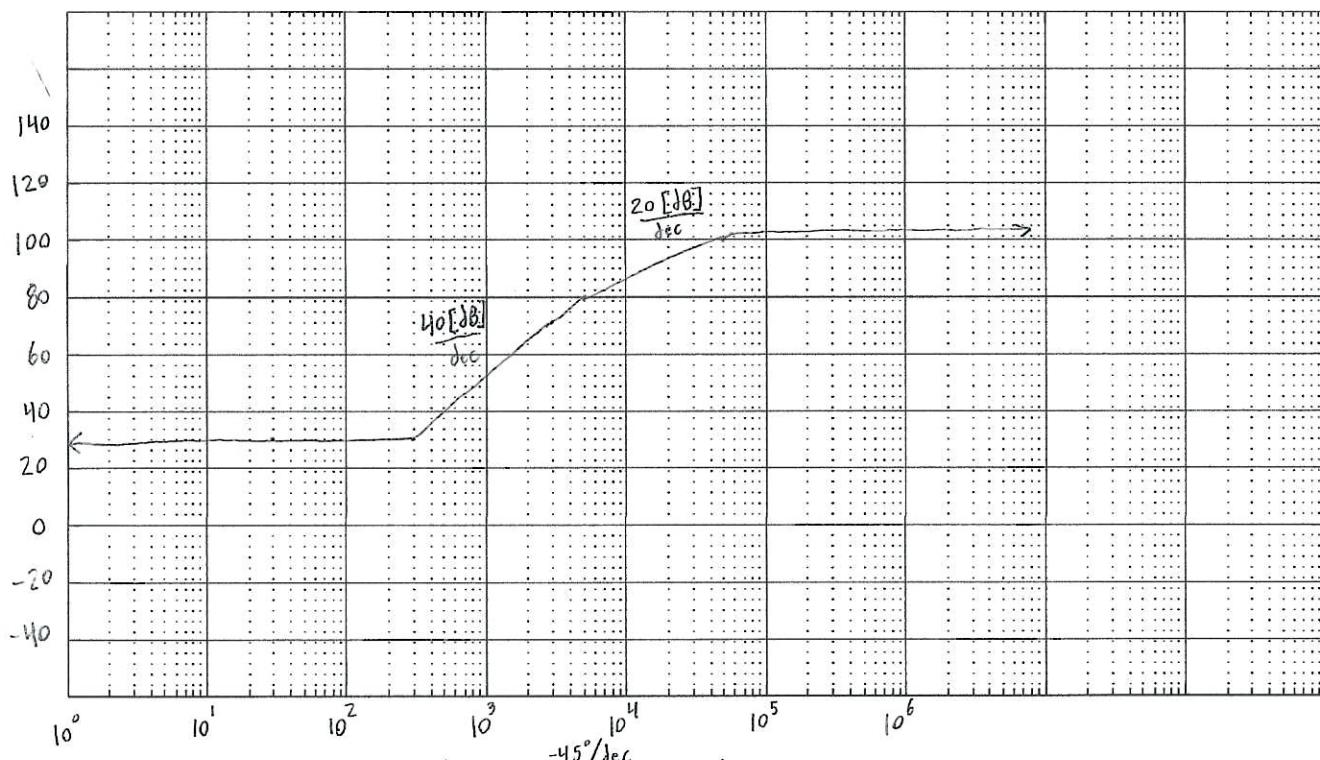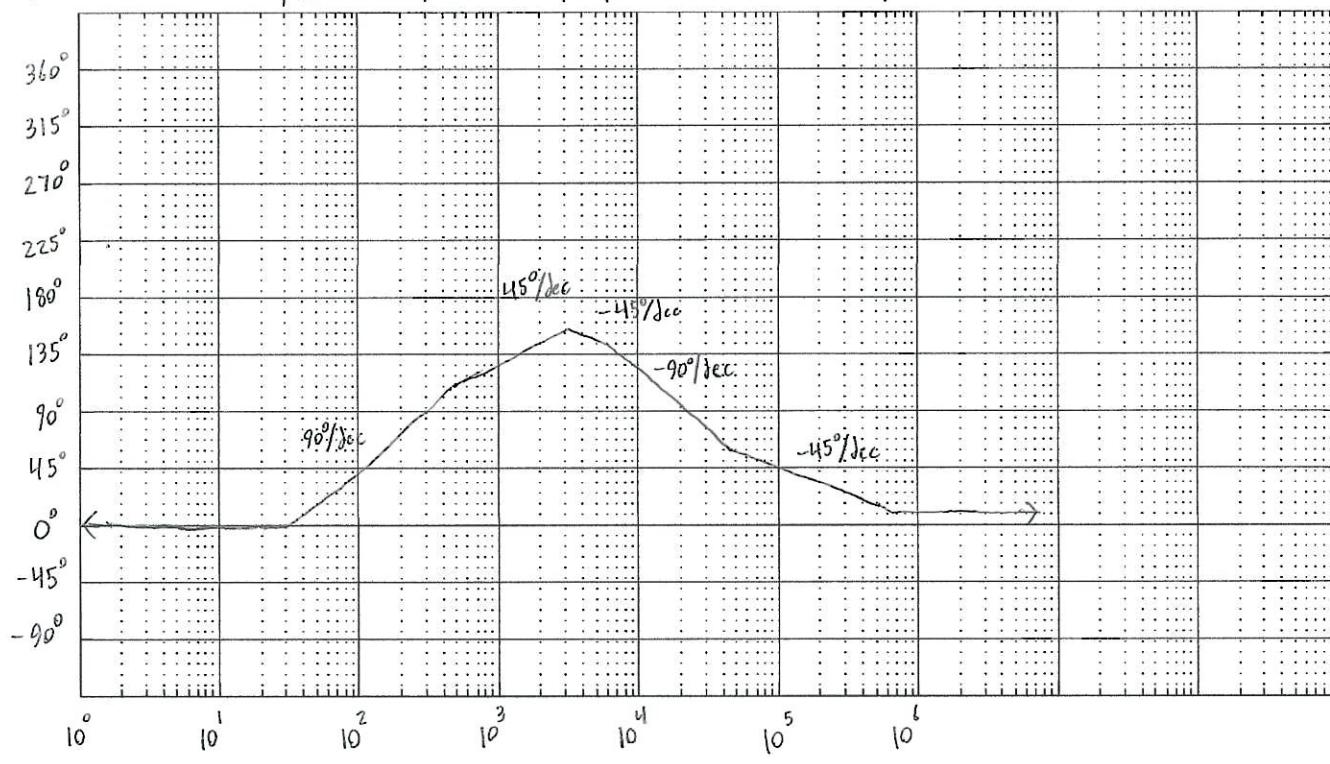 $|H(j\omega)| [\text{dB}]$  $\phi [\text{deg}]$ 

3.) a.)

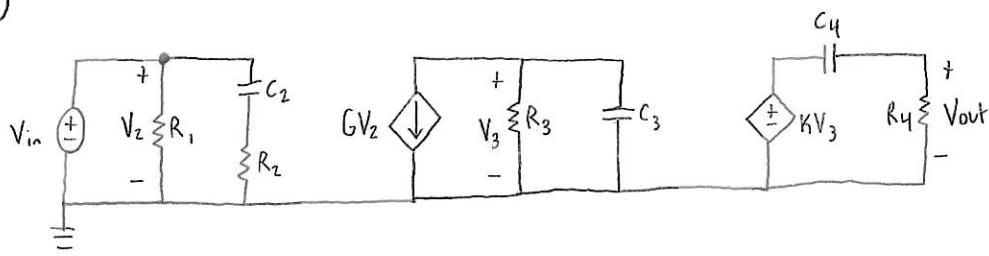

$$V_2 = V_{in}$$

$$KCL: \quad GV_2 + \frac{V_3}{R_3} + \frac{V_3}{(1/j\omega C_3)} = 0$$

(V₃)

$$GV_2 + V_3 \left(\frac{1}{R_3} + \frac{j\omega C_3}{1} \right) = 0$$

$$GV_2 + V_3 \left[\frac{1 + j\omega C_3 R_3}{R_3} \right] = 0$$

$$GV_2 + V_3 \left[\frac{1 + j\omega C_3 R_3}{R_3} \right] = 0$$

$$V_3 = -GV_2 \cdot \frac{R_3}{1 + j\omega C_3 R_3}$$

$$V_{out} = \frac{R_4}{1/j\omega C_4 + R_4} KV_3$$

$$= \frac{j\omega C_4 R_4}{1 + j\omega C_4 R_4} KV_3$$

$$= -GV_2 K R_3 \frac{j\omega C_4 R_4}{(1 + j\omega C_3 R_3)(1 + j\omega C_4 R_4)}$$

$$\boxed{\frac{V_{out}}{V_{in}} = -GR_3K \cdot \frac{j\omega C_4 R_4}{(1 + j\omega C_3 R_3)(1 + j\omega C_4 R_4)}}$$

b.)

$$H(j\omega) = -10 \cdot 10 \cdot \frac{j\omega 0.01}{(1 + j\omega 0.0001)(1 + j\omega 0.01)}$$

$$H(j\omega) = -100 \cdot \frac{j \frac{\omega}{100}}{(1 + j \frac{\omega}{10000})(1 + j \frac{\omega}{100})}$$

See next page for Bode plots

3.) b.)

$$\omega_0 = 10$$


$$H(j\omega) = -j10 \Rightarrow 20 \text{ [dB]}$$

$$|H(j\omega)| \text{ [dB]}$$

$$P_1 = 100$$

$$P_2 = 10000$$


$$\phi = -90^\circ$$

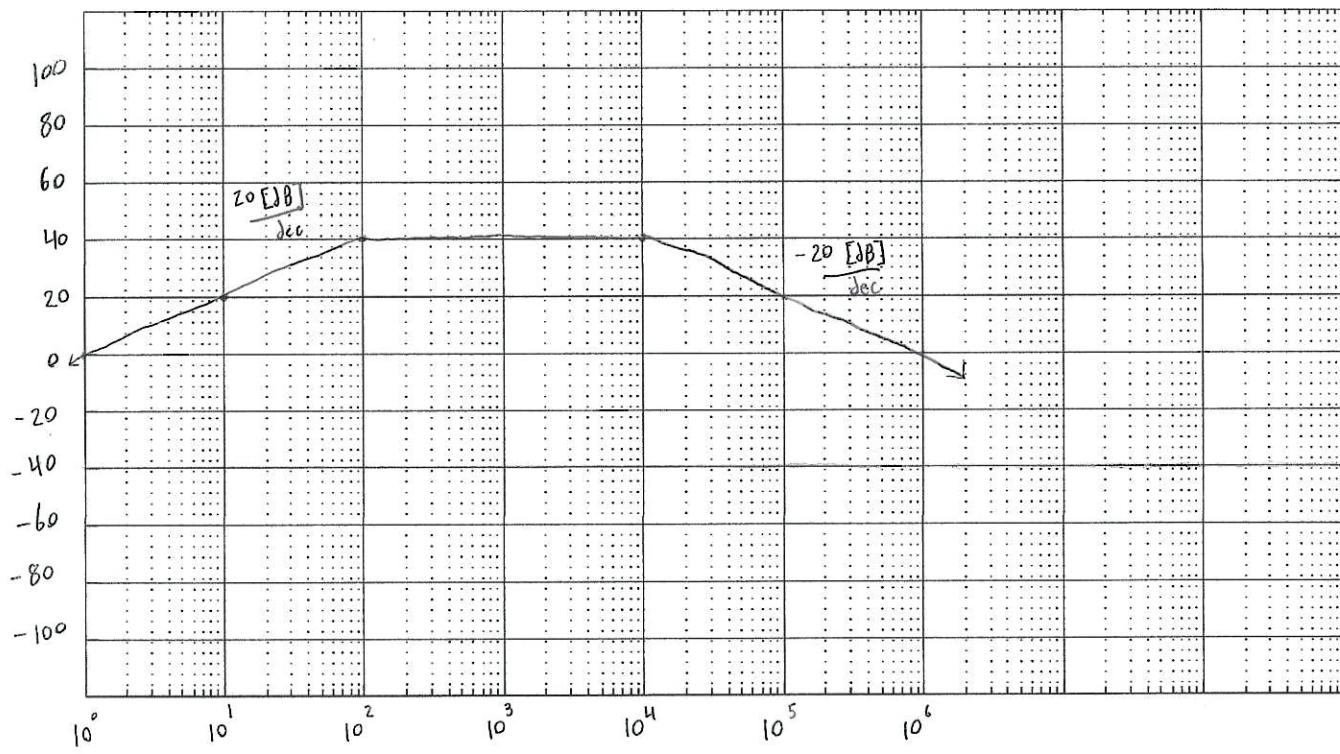


$$\phi \text{ [deg]}$$

$$-45^\circ/\text{dec}$$

$$-45^\circ/\text{dec}$$

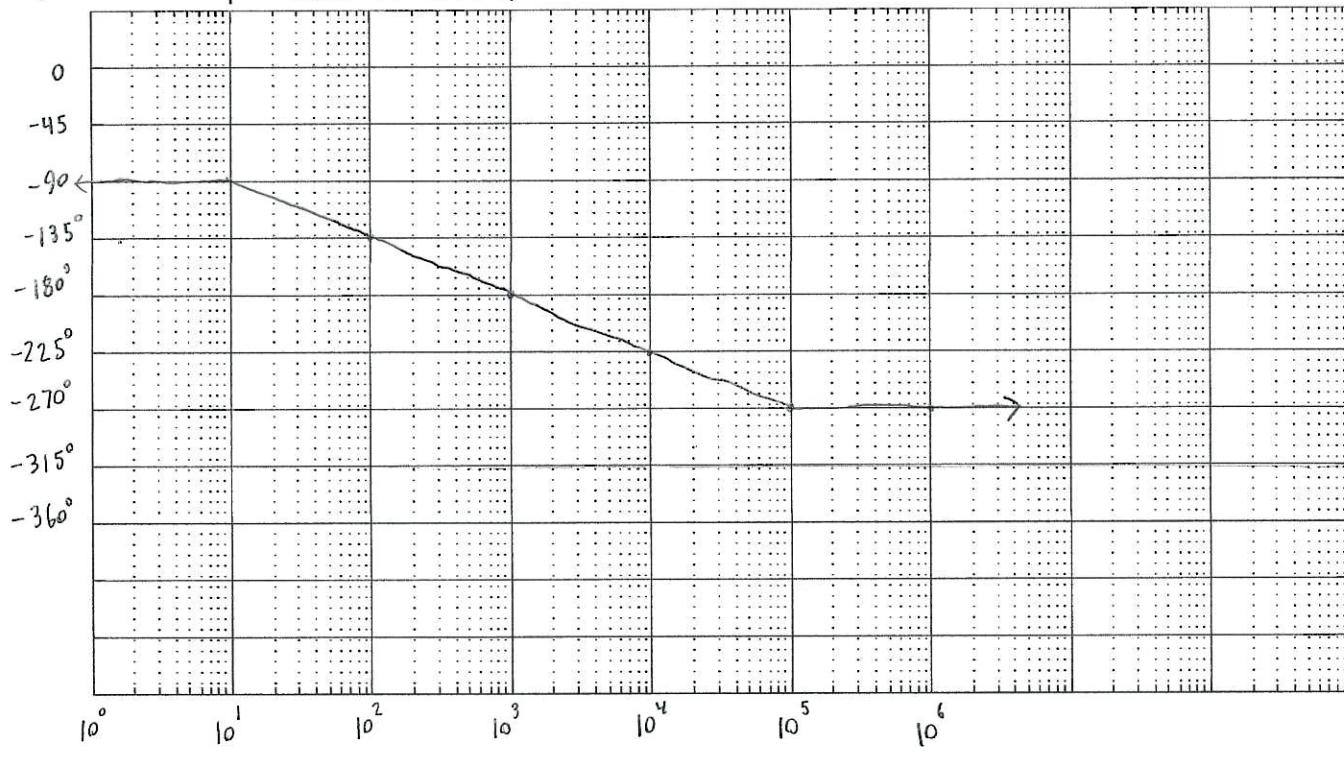

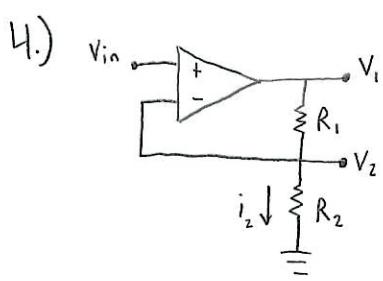


$$V_2 = V_{in}$$

$$i_2 = \frac{V_{in}}{R_2}$$

$$V_1 = V_{in} + i_2 R_1 = V_{in} + V_{in} \frac{R_1}{R_2}$$
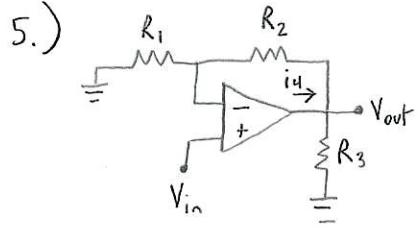
$$V_1 = V_{in} \left(1 + \frac{R_1}{R_2} \right)$$



$$KCL: \frac{-V_{in}}{R_1} = \frac{V_{in} - V_{out}}{R_2}$$

$$\frac{V_{out}}{R_2} = \frac{V_{in}}{R_1} + \frac{V_{in}}{R_2}$$

$$V_{out} = \left(1 + \frac{R_2}{R_1} \right) V_{in}$$

$$i_4 = \frac{V_{out}}{R_3} + \frac{V_{out} - V_{in}}{R_2}$$

$$= V_{out} \left(\frac{1}{R_3} + \frac{1}{R_2} \right) - \frac{V_{in}}{R_2}$$

$$= \left(1 + \frac{R_2}{R_1} \right) \left(\frac{1}{R_3} + \frac{1}{R_2} \right) V_{in} - \frac{V_{in}}{R_2}$$

$$= \left(\frac{1}{R_3} + \frac{1}{R_2} + \frac{R_2}{R_1 R_3} + \frac{1}{R_1} \right) V_{in} - \frac{V_{in}}{R_2}$$

$$i_4 = \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{R_2}{R_1 R_3} \right) V_{in}$$