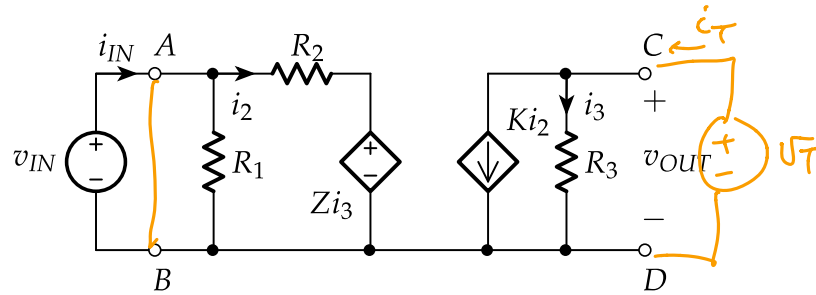


1. (15 points) For the following circuit, find the voltage gain, $\frac{v_{OUT}}{v_{IN}}$, and the input and output resistances.



$$v_{OUT} = i_3 R_3 \quad v_{IN} = i_2 R_2 + Z i_3 \quad i_3 = -K i_2$$

$$\frac{v_{OUT}}{v_{IN}} = \frac{i_3 R_3}{i_2 R_2 + Z i_3} = \frac{-K i_2 R_3}{i_2 R_2 - K i_2 Z} = \frac{-K R_3}{R_2 - K Z} = \boxed{\frac{K R_3}{K Z - R_2}}$$


$$R_{in} = \frac{v_{IN}}{i_{IN}} = \frac{v_{IN}}{\frac{v_{IN}}{R_1} + i_2} \quad v_{IN} = i_2 R_2 - K Z i_2 \Rightarrow i_2 = \frac{v_{IN}}{R_2 - K Z}$$

$$= \frac{v_{IN}}{\frac{v_{IN}}{R_1} + \frac{v_{IN}}{R_2 - K Z}} = R_1 \parallel (R_2 - K Z) = \boxed{\frac{R_1 (R_2 - K Z)}{R_1 + R_2 - K Z}}$$

$$R_{out} = \frac{v_T}{i_T} = \frac{v_T}{K i_2 + i_3} \quad -i_2 R_2 = Z i_3 \quad v_T = i_3 R_3$$

$$= \frac{i_3 R_3}{K i_2 + i_3} = \frac{i_3 R_3}{K(-\frac{Z i_3}{R_2}) + i_3} = \boxed{\frac{R_2 R_3}{R_2 - K Z}}$$

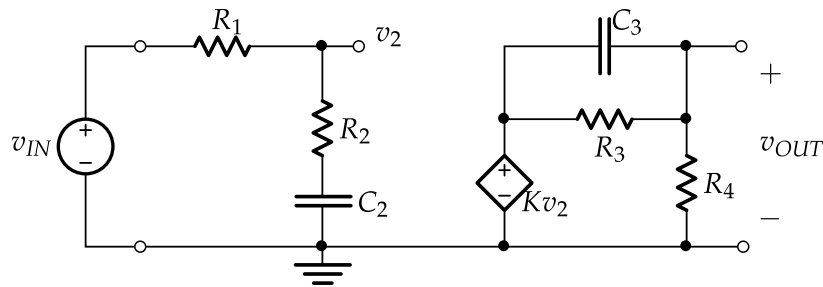2. (10 points) For the following circuit, answer the three questions below.



(a) What is the gain at low frequencies?

C_2 and C_3 are open, so $V_2 = V_{in}$ and $V_{out} = K V_2 \frac{R_4}{R_3 + R_4}$

(a) $K \frac{R_4}{R_3 + R_4}$

(b) What is the gain at high frequencies?

C_2 and C_3 are shorts, so $V_2 = \frac{R_2}{R_1 + R_2} V_{in}$ and $V_{out} = K V_2$

(b) $K \frac{R_2}{R_1 + R_2}$


(c) Sketch of the *shape* of the magnitude plot for each of the two stages of the circuit: for $\frac{\bar{V}_2}{\bar{V}_{in}}$ and for $\frac{\bar{V}_{out}}{\bar{V}_2}$ (You do not need to label the x and y axes).



3. (15 points) Bode Plots

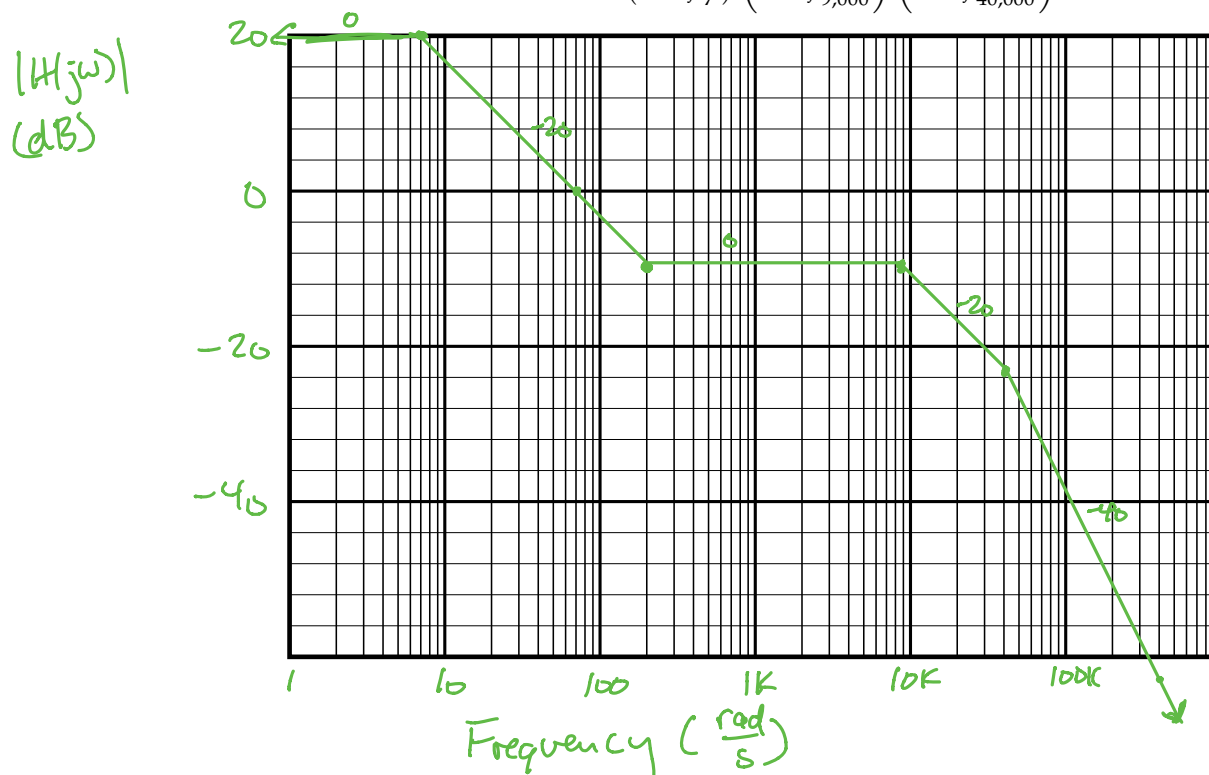- (a) Plot a straight-line approximation of the Bode plot on the graph paper provided for the *magnitude only* for the following transfer function (the unit for the values in the denominator of the imaginary terms is rad/sec).

$$H(j\omega) = -10 \frac{(1 + j\frac{\omega}{200})}{(1 + j\frac{\omega}{7}) (1 + j\frac{\omega}{9,000}) (1 + j\frac{\omega}{40,000})}$$



- (b) What is the starting phase (i.e., the phase at low frequencies)?

(b) 180° or -180°

- (c) What is the ending phase (i.e., the phase at high frequencies)?


(c) 0°
(-360° is OK)

Version B

(b) 0° (or 360°)
(c) -180° (or 180°)

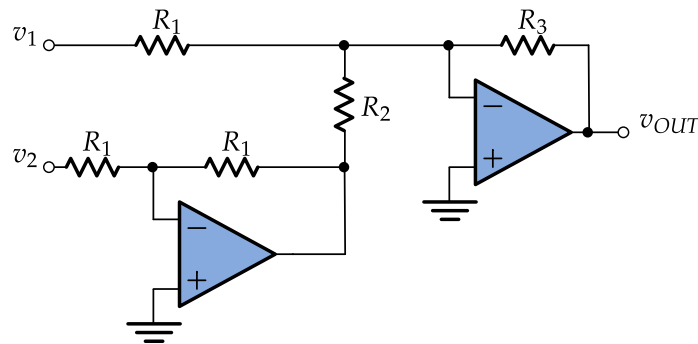
4. (15 points) Difference Amplifier

- Write an expression for the common mode gain (A_{cm}).
- Write an expression for the difference gain (A_d). (Hint: if you are using superposition, you may make an important assumption regarding R_1 and R_2 .)
- For $R_1 = 3 \text{ k}\Omega$, $R_2 = 2.99 \text{ k}\Omega$, and $R_3 = 30 \text{ k}\Omega$, approximate the CMRR? (Hint: you can use the difference gain calculated from Part (b))
- What is the input resistance seen at each of the input terminals (i.e., at v_1 and v_2)?



There are two ways to solve this problem.

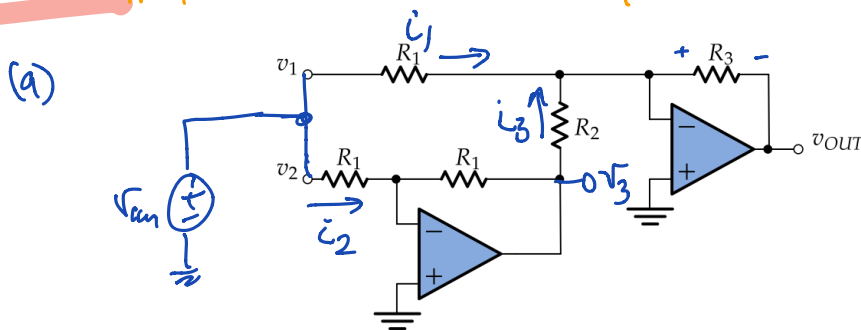Approach (1) Apply $v_d \pm v_{cm}$ directly:




$$i_2 = \frac{v_{cm}}{R_1} \quad i_1 = \frac{v_{cm}}{R_1} \quad i_3 = \frac{v_3}{R_2} \quad v_{OUT} = -(i_1 + i_3) R_3$$

$$v_3 = -i_2 R_1 = -v_{cm}$$

$$\text{so } v_{OUT} = -\left(\frac{v_{cm}}{R_1} + \frac{v_3}{R_2}\right) R_3 = -v_{cm} R_3 \left(\frac{1}{R_1} - \frac{1}{R_2}\right)$$
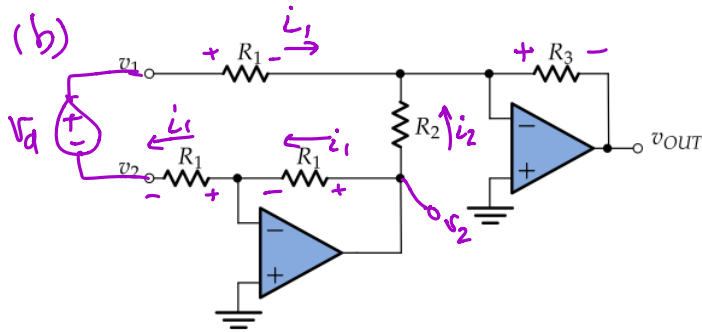
$$A_{cm} = \frac{v_{OUT}}{v_{cm}} = -R_3 \left(\frac{R_2 - R_1}{R_1 R_2}\right) = \boxed{R_3 \left(\frac{R_1 - R_2}{R_1 R_2}\right)}$$



$$v_{out} = -(i_1 + i_2)R_3$$

$$i_1 = \frac{v_d}{2R_1}$$

$$v_2 = i_1 R_1 = \frac{v_d}{2}$$

$$i_2 = \frac{v_2}{R_2} = \frac{v_d}{2R_2}$$

$$v_{out} = -\left(\frac{v_d}{2R_1} + \frac{v_d}{2R_2}\right)R_3$$


$$A_d = \frac{v_{out}}{v_d} = -\left(\frac{R_1 + R_2}{2R_1 R_2}\right)R_3$$

$$\begin{aligned} (c) \text{ CMRR} &= 20 \log_{10} \frac{|A_d|}{|A_{cm}|} = 20 \log_{10} \left| \frac{\frac{R_1 + R_2}{2R_1 R_2} \cdot R_3}{R_3 \left(\frac{R_1 - R_2}{2R_1 R_2} \right)} \right| = 20 \log_{10} \left| \frac{-(R_1 + R_2)}{2(R_1 - R_2)} \right| \\ &= 20 \log_{10} \left| \frac{3\text{k}\Omega + 299\text{k}\Omega}{2(0.01\text{k}\Omega)} \right| = 49.5\text{dB} \\ &\quad \boxed{35.8\text{dB}} \leftarrow \text{version B} \end{aligned}$$

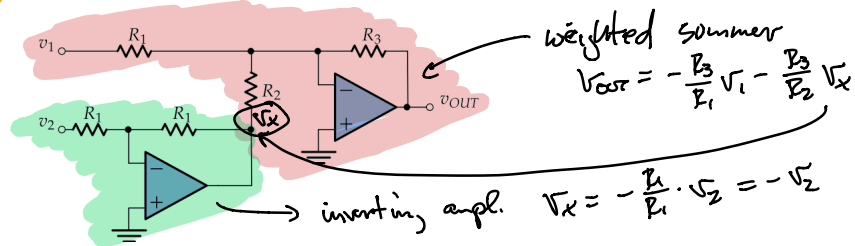(d) $R_{in} = R_1$ for both v_1 and v_2

Approach (2)

if you recognize the inverting weighted summer and the inverting amplifier,



$$(a) \quad v_{out} = -\frac{R_3}{R_1} v_1 - \frac{R_3}{R_2} (-v_2) = -\frac{R_3}{R_1} v_1 + \frac{R_3}{R_2} v_2$$

$$v_{out} = -\frac{R_3}{R_1} v_{cm} + \frac{R_3}{R_2} v_{cm} \Rightarrow \boxed{A_{cm} = \frac{v_{out}}{v_{cm}} = R_3 \left(\frac{R_1 - R_2}{R_1 R_2} \right)}$$

(b) For this to be a difference amplifier, $R_1 = R_2$

$$\text{So } v_{out} = \frac{R_3}{R_1} (v_2 - v_1) \quad \text{and} \quad \boxed{A_d = \frac{v_{out}}{(v_2 - v_1)} = \frac{R_3}{R_1}}$$

$$A_d = \frac{30k\Omega}{3k\Omega} = 10$$


$$(c) \quad CMRR = 20 \log_{10} \left| \frac{\frac{R_3}{R_1}}{R_3 \left(\frac{R_1 - R_2}{R_1 R_2} \right)} \right| = 20 \log_{10} \left| \frac{R_2}{R_1 - R_2} \right|$$

$$= 20 \log_{10} \left| \frac{2.99k\Omega}{0.01k\Omega} \right| = \boxed{49.5 \text{ dB}}$$

$$\text{version B} \quad = 20 \log_{10} \left| \frac{4.92k\Omega}{0.08k\Omega} \right| = 35.8 \text{ dB}$$

(d) $R_{in} = R_1$ for both v_1 and v_2

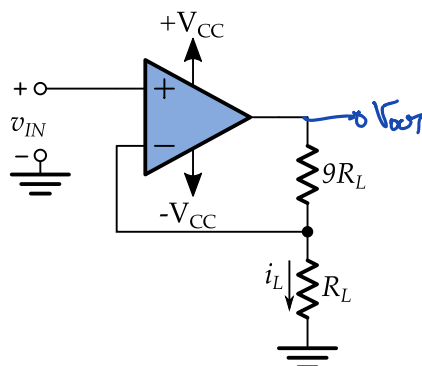5. (15 points) For the following circuit, the op-amp is powered by a pair of $\pm V_{CC} = \pm 15$ volt supplies (as shown).



- (a) Write an expression for i_L in terms of v_{IN} and R_L .
- (b) What is the range of v_{IN} that ensures the circuit does not go into voltage saturation?
- (c) What range of load resistor values (i.e., R_L) will ensure that the circuit does not go into current saturation for the full input range from above? The maximum current for the op-amp is 15 mA.

$$(a) \quad i_L = \frac{v_{IN}}{R_L}$$

$$(b) \quad v_{OUT} = \left(1 + \frac{9R_L}{R_L}\right) v_{IN} = 10 v_{IN} \Rightarrow \text{non-inverting amplifier configuration}$$

Since $-15V < v_{OUT} < 15V$

$$\boxed{-1.5V < v_{IN} < 1.5V}$$

(c) from (a) $\frac{1}{2}$ (b)


$$i_L = \frac{v_{IN}}{R_L} < 15 \text{ mA}$$

$$R_L > \frac{v_{IN}}{15 \text{ mA}} = \frac{1.5V}{15 \text{ mA}} = 100 \Omega$$

$$\boxed{R_L > 100 \Omega}$$

$R_L > 50 \Omega$ for version B

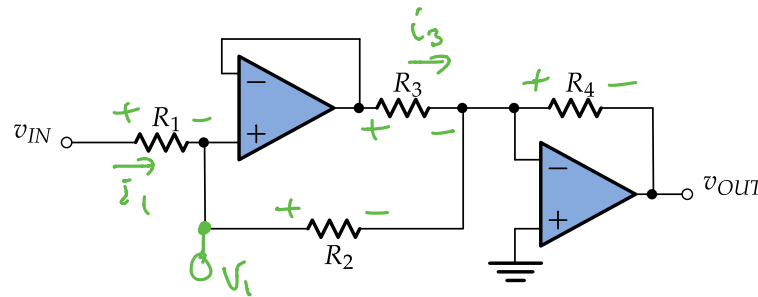6. (15 points) For the following circuit, find an expression for the voltage gain, $\frac{v_{OUT}}{v_{IN}}$.



$$v_{OUT} = -(i_1 + i_3) R_4$$



$$i_1 = \frac{v_{IN}}{R_1 + R_2} \quad v_1 = \frac{R_2}{R_1 + R_2} \cdot v_{IN} \quad i_3 = \frac{v_1}{R_3}$$

$$v_{OUT} = - \left(\frac{v_{IN}}{R_1 + R_2} + \frac{v_1}{R_3} \right) R_4$$

$$= - \left(\frac{v_{IN}}{R_1 + R_2} + \frac{R_2 v_{IN}}{R_3 (R_1 + R_2)} \right) R_4$$

$$\frac{v_{OUT}}{v_{IN}} = -R_4 \left(\frac{R_3 + R_2}{R_3 (R_1 + R_2)} \right) = -\frac{R_4}{R_3} \left(\frac{R_2 + R_3}{R_1 + R_2} \right)$$

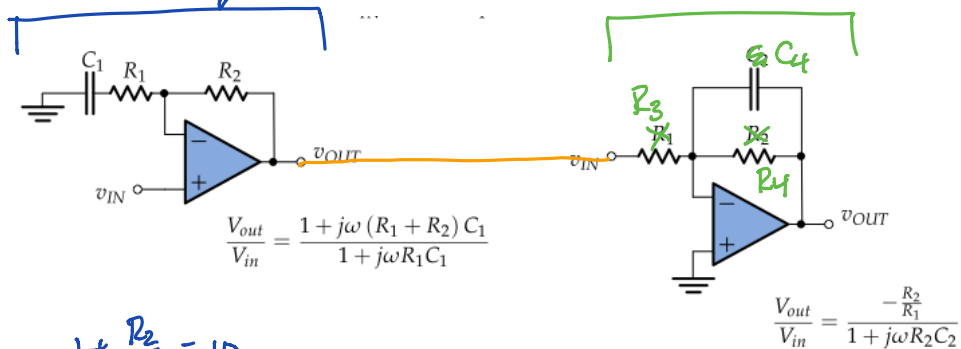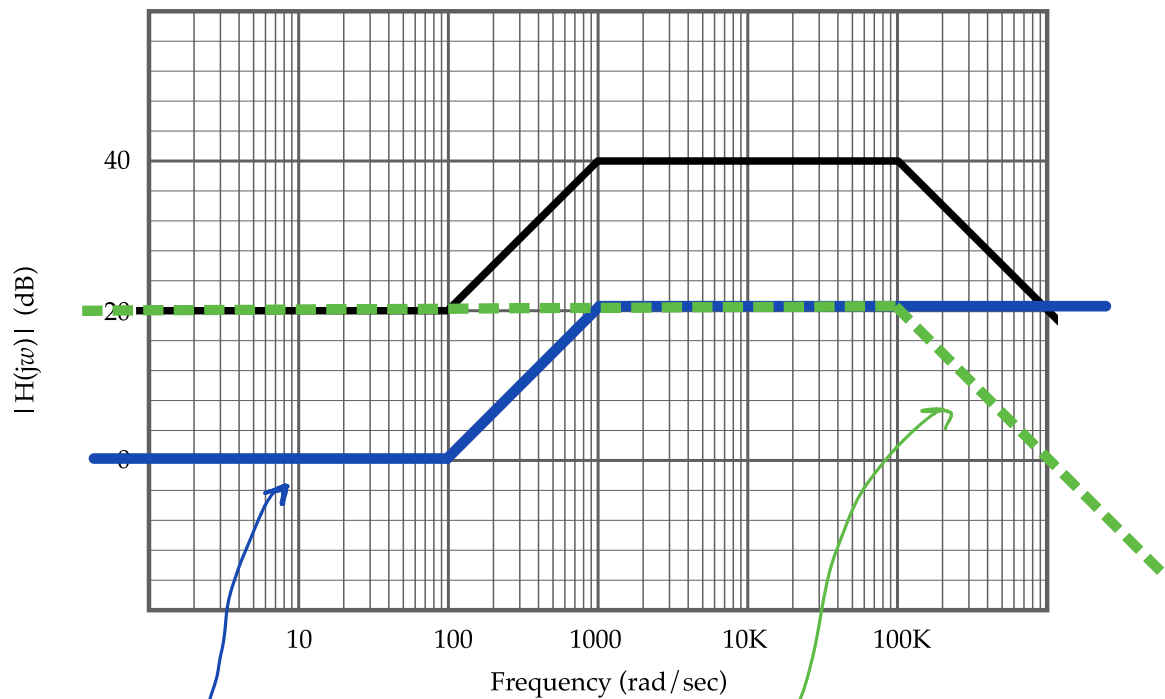7. (15 points) Design a circuit that has the following straight-line approximation to the Bode plot. Indicate which order the stages should be placed in to ensure that the input resistance does not vary with frequency.



$$1 + \frac{R_2}{R_1} = 10$$

choose $R_2 = 90 \text{ k}\Omega$
 $R_1 = 10 \text{ k}\Omega$

$$\frac{1}{R_1 C_1} = 1000 \frac{\text{rad}}{\text{s}}$$

$$C_1 = \frac{1}{10^3 \cdot 10^4} = 10^{-7} \text{ F} = 0.1 \mu\text{F} = 100 \text{ nF}$$

$$\frac{R_4}{R_3} = 10$$



choose

$$R_4 = 10 \text{ k}\Omega$$

$$R_3 = 1 \text{ k}\Omega$$

$$\frac{1}{R_4 C_3} = 10^6 \frac{\text{rad}}{\text{s}}$$
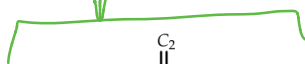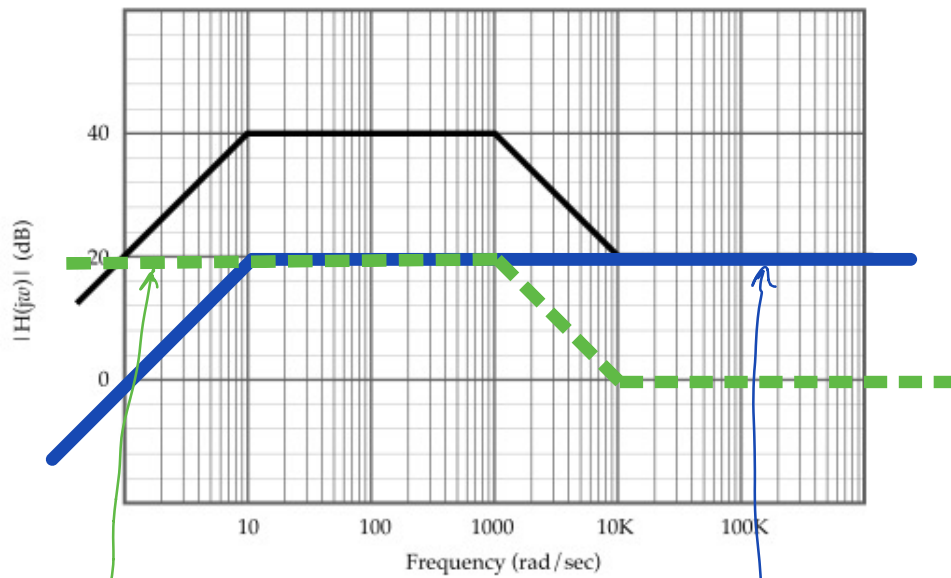
$$C_3 = \frac{1}{10^5 \cdot 10^4} = 10^{-9} \text{ F} = 1 \text{ nF}$$



$$\frac{V_{out}}{V_{in}} = \left[1 + \frac{R_2}{R_1} \right] \left[\frac{1 + j\omega (R_1 || R_2) C_2}{1 + j\omega R_2 C_2} \right]$$


$$1 + \frac{R_2}{R_1} = 10$$

choose
 $R_2 = 90 \text{ k}\Omega$
 $R_1 = 10 \text{ k}\Omega$

$$\frac{1}{R_2 C_2} = 1000 \frac{\text{rad}}{\text{sec}}$$

$$C_2 = \frac{1}{9 \times 10^4 \times 10^3} = 1.11 \times 10^{-8} \text{ F}$$

$$= 0.01 \mu\text{F} = 11.1 \text{ nF}$$

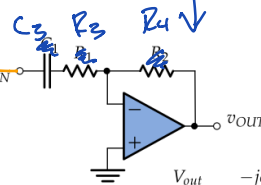

$$\frac{V_{out}}{V_{in}} = \frac{-j\omega R_2 C_1}{1 + j\omega R_1 C_1}$$

$$\frac{R_4}{R_3} = 10$$

choose
 $R_4 = 100 \text{ k}\Omega$
 $R_3 = 10 \text{ k}\Omega$

$$\frac{1}{R_3 C_3} = 10 \frac{\text{rad}}{\text{sec}}$$

$$C_3 = \frac{1}{10^4 \times 10^4} = 10^{-5} \text{ F}$$

$$= 10 \mu\text{F}$$