
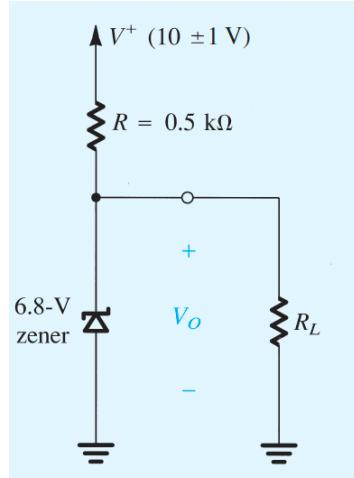


Homework 8 Topic: Diodes II + BJTs

- Consider a half-wave peak rectifier fed with a voltage v_s having a triangular waveform with 24-V peak-to-peak amplitude, zero average, and 1-kHz frequency. Assume that the diode has a 0.7-V drop when conducting. Let the load resistance $R = 100\Omega$ and the filter capacitor $C = 100 \mu F$. Find the average dc output voltage, the time interval during which the diode conducts, the average diode current during conduction, and the maximum diode current.
- Zener Diode Regulator: For this problem you will need the data sheet for a Zener Diode, which you can find your own or use the one Fairchild Semiconductor that is provided on Canvas. Note that the data sheet provides values for V_Z , which is measured at the current I_Z , as well as for the series resistance. We want to design a 12 V regulator using a reverse-bias Zener diode similar to the circuit below the load of $2.2 \text{ k}\Omega$. For this design problem, the supply voltage V^+ is 25 ± 2.5 V (not 10 ± 1 V as shown in the figure below).
 - Choose one Zener diode to regulate the load voltage to approximately 12 V. Based on the information in the data sheet, find V_{Z0} for this diode.
 - If the Zener current is 25 mA, find V_Z . Then find the current through R , and from that determine a value for R . Use the nominal voltage for the power supply (i.e., 25 V).
 - Find the line regulation.

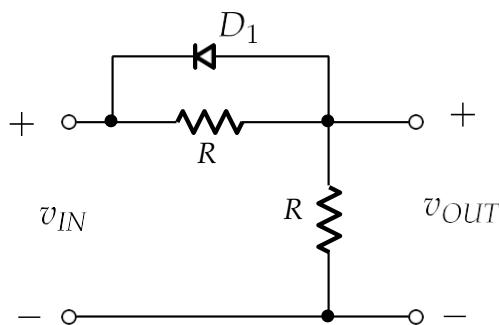

- For the circuit below using the constant voltage drop model with $V_{D0} = 0.7 \text{ V}$ and $r_D = 0$:
 - Write an expression for v_{OUT} in terms of v_{IN} .
 - Sketch a graph of v_{OUT} vs. v_{IN} .



1)

$$V_{O,pk} = V_{S,peak} - 0.7V = \frac{24}{10} - 0.7 = 11.3[V]$$

$$v_0 = 11.3 e^{-T/f_{cr}} \Rightarrow v_0 @ T = 10.22$$

$$\Delta v_o = 11.3 - 10.22 = 1.08$$

$$i_c \Delta t = C v_o$$

$$i_c = \frac{100 \times 10^{-6} \cdot 1.08}{22.5 \times 10^3} = 4.8A$$

$$i_{L,pk} = C \frac{\delta v_o}{\delta t} @ 0 = 100 \frac{1.08}{10^3} = 0.108A$$

$$i_{L,pk} = \frac{V_o}{R_L} = \frac{11.3}{100} = 0.113A$$

$$V_{AVG} = \frac{V_{max} + V_{C+T}}{2} = \frac{11.3 + 10.22}{2} = 10.76$$

$$\frac{12}{T_L} = \frac{1.08}{\Delta t} \Rightarrow \Delta t = \frac{1.08}{12} \frac{10^{-3}}{4} = 22.5 \text{ ms}$$

$$i_L = \frac{v_{avg}}{R_L} = \frac{10.76}{100} = 0.1076A$$

$$i_{avg} = i_L + i_D = 0.1076 + 0.08 = 0.1976A$$

$$i_{2,max} = i_{C,pk} + i_{D,pk} = \frac{0.108 + 0.08}{0.01} = 1.88A$$

2)

$$I_Z = MMS Z5221B \rightarrow 20mA \text{ at } 30V \quad v_{non} = 2.1V$$

$$V_{Z0} = V_Z - I_Z R_Z = 12 - 20 \cdot 20 \cdot 10^{-3} = 12 - 0.4 = 11.6V$$

$$I_Z = 20mA \quad V_Z = V_{Z0} + I_Z R_Z = 11.6 + 20 \cdot 20 \cdot 10^{-3} = 12.15V$$

$$I_R = I_Z + I_{RL} = 2.5 - 12.15 = 2.5 + \frac{12.15}{2 \cdot 10^3} \Rightarrow R_L = \frac{12.15}{30 \cdot 5 \cdot 10^3} = 421$$

$$V_S - V_Z = I_Z + \frac{V_Z}{R_L}$$

$$LR = \Delta v_S \frac{R_L}{R_1 R_2} = \frac{2.5V \cdot 30}{421 \cdot 22} = 0.166 \frac{V}{V}$$

3)

$$V_{DD} = 7V \quad r_o = 0$$


$$v_{out} = -v_{IN}$$

$$\frac{v_{out}}{R} = \frac{v_{IN} - (v_{out} + 0.7)}{R}$$

$$v_{out} = v_{out} + v_{IN}$$

$$v_{out} = 3V_{out}$$
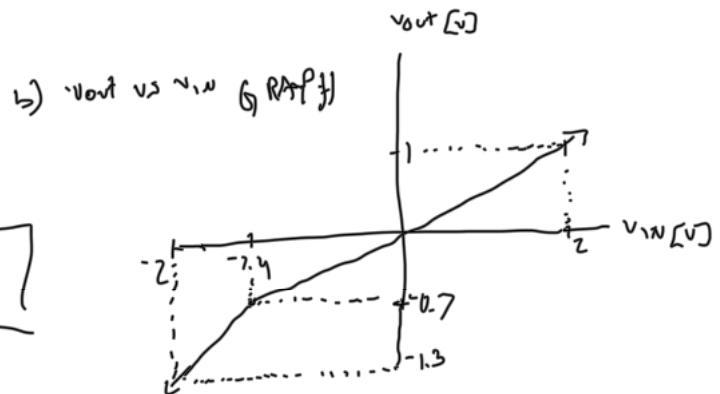
$$v_{out} = \begin{cases} V_{IN} + 0.7, & V_{IN} \leq -1.4[V] \\ V_{IN}/2, & V_{IN} > -1.4[V] \end{cases}$$




4)


$$V_{out} = \begin{cases} \frac{2v_{IN} + 0.7}{3}, & v_{IN} \leq -1.4[V] \\ \frac{v_{IN}}{2}, & v_{IN} > -1.4[V] \end{cases}$$

$$\frac{V_o}{R} = \frac{V_{IN} - V_o}{R} - \frac{V_o - 0.7}{R}$$
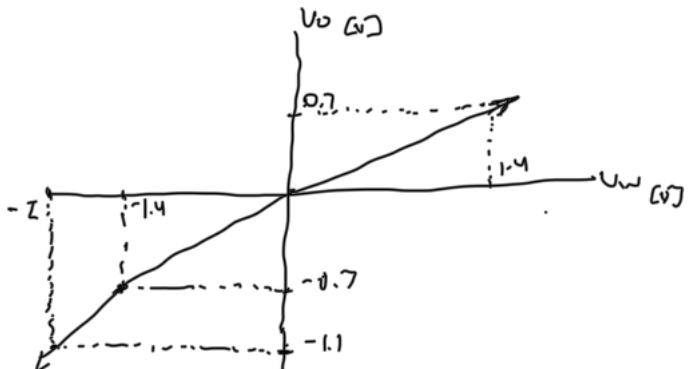
$$\frac{2V_o}{R} = \frac{(2v_{IN} + 0.7)}{3R}$$



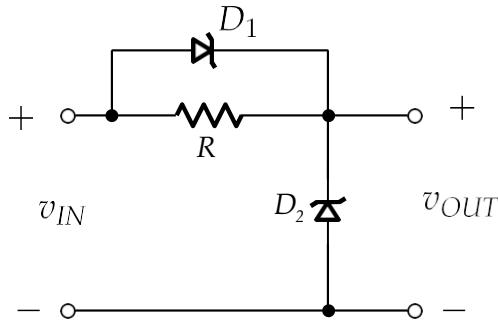
4. Repeat problem 3 with $r_D = R$.
5. For the circuit below using the constant voltage drop model with $V_{D0} = 0.7\text{ V}$, $V_{Z0} = 1.4\text{ V}$, $r_D = r_z = 0$:
- Write an expression for v_{OUT} in terms of v_{IN} .
 - Sketch a graph of v_{OUT} vs. v_{IN} .




6. Measurements of V_{BE} and two terminal currents taken on a number of npn transistors operating in the active mode are tabulated below. For each, calculate the missing current value as well as α , β , and I_S as indicated by the table.

| Transistor | a | b | c | d | e |
|-------------------------|-------|-------|-------|-------|-------|
| V_{BE} (mV) | 700 | 690 | 580 | 780 | 820 |
| I_C (mA) | 1.000 | 1.000 | | 10.10 | |
| I_B (μA) | 10 | | 5 | 120 | 1050 |
| I_E (mA) | | 1.020 | 0.235 | | 75.00 |
| α | | | | | |
| β | | | | | |
| I_S | | | | | |

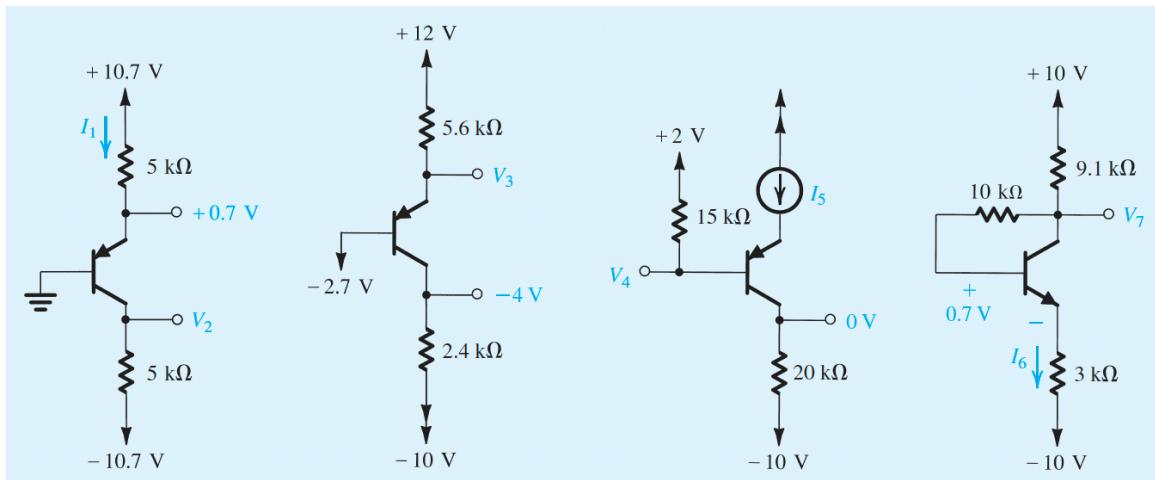
7. For the circuits below, assume that the transistors have very large β . Some measurements have been made on these circuits, with the results indicated in the figure. Find the values of the other labeled voltages and currents.



$$5) V_{DD} = 0.7 \text{ V}$$

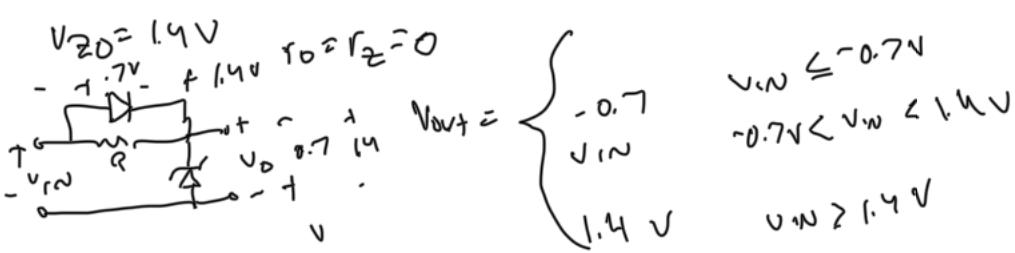
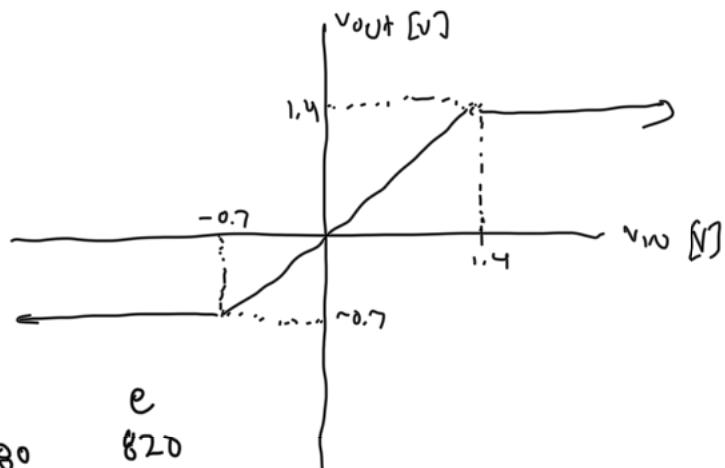
$$\begin{aligned} v_{IN} &\leq -0.7 \text{ V} \\ -0.7 \text{ V} &< v_{IN} < 1.4 \text{ V} \\ v_{IN} &> 1.4 \text{ V} \end{aligned}$$




b)

| | a | b | c | d | e |
|---------------------|------------------------|--------------------------|-------------------------|-------------------------|-------------------------|
| $V_{BE(\text{MV})}$ | 700 | 690 | 580 | 780 | 820 |
| $I_C(\text{mA})$ | 1.000 | 1.000 | 0.23 | 10.10 | 13.95 |
| $I_B(\text{mA})$ | 10 | 20 | 5 | 120 | 1050 |
| $I_E(\text{mA})$ | 1.01 | 1.020 | 0.235 | 10.22 | 15.00 |
| α | .99 | .98 | .979 | .988 | .986 |
| β | 100 | 50 | 46 | 84.167 | 70.43 |
| I_S | 6.91×10^{-16} | 1.0315×10^{-15} | 1.932×10^{-15} | 2.847×10^{-16} | 4.208×10^{-16} |

$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{1 - \alpha} \quad I_E = I_B + I_C \quad I_C = \frac{I_C}{\beta} \quad I_E = \frac{I_C}{\alpha}$$

$$T = 300 \cdot 1K \quad V_T = 25 \text{ mV}$$


7) $\beta \gg \alpha$

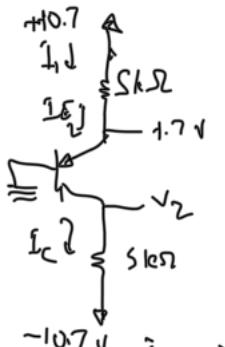


$$I_1 = \frac{10.7 - 0.7}{5 \text{ k}\Omega} = 2 \text{ mA}$$

$$I_C = I_E = I_1 = 2 \text{ mA} \quad V_2 = 0.7 \text{ V}$$
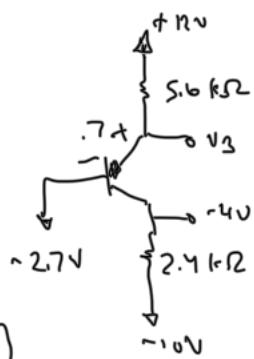
$$V_2 = 10.7 - 5 \times 0.2 \times 10^3 = 0.7 \text{ V}$$



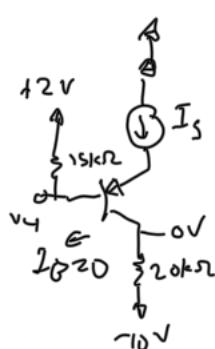
$$V_3 = 2.7 + 0.7 \quad V_3 = 2.0 \text{ V}$$



$$I_5 = I_E = I_0 = \frac{1.5}{20 \text{ k}\Omega} = 0.5 \text{ mA}$$

$$V_4 = 2 \text{ V}$$

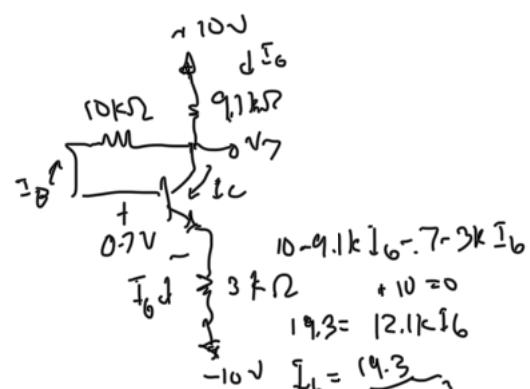

$$I_6 = 1.595 \text{ mA}$$

$$I_7 = 10 \text{ V} - 9.1 \text{ k}\Omega \cdot I_6$$

$$= 10 - 9.1 \times 10^3 \cdot 1.595 \cdot 10^{-3}$$

$$V_7 = -4.51 \text{ V}$$