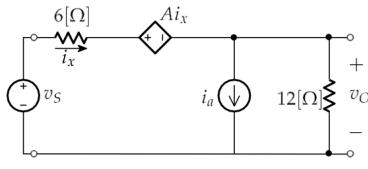


Problem 1

Use superposition to solve this problem. Choose values for i_a and A so that

$$v_o = \frac{1}{2} v_s - 3[V]$$

Hint: first find A by using only the voltage source, and then find the value of i_a by using only the current source.



Ans: $A = 6\Omega$; $i_a = 0.5A$



$$\text{KVL: } -v_s + 6i_x + A i_x + v_o = 0$$

$$v_o = v_s - i_x(6+A)$$

$$v_o' = v_s - \frac{v_o}{12}(6+A)$$

$$v_o' + \frac{v_o}{12}(6+A) = v_s$$

$$v_o'(1 + \frac{6+A}{12}) = v_s$$


$$v_o' \left(\frac{18+A}{12} \right) = v_s$$

$$v_o' = v_s \left(\frac{12}{18+A} \right)$$

$$\text{From eq.: } \frac{1}{2} v_s = v_o' \left(\frac{12}{18+A} \right)$$

$$18+A=24$$

$$A=6\Omega$$

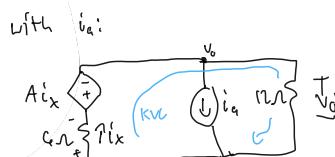

$$\text{KVL: } 6i_x + A i_x + v_o = 0 \quad \text{KVL at } V_o: -i_x + i_a + \frac{v_o''}{12} = 0$$

$$v_o'' = -6i_x - A i_x$$

$$v_o'' = -i_x(6+A)$$

$$v_o'' = -i_x(12)$$

$$v_o'' = -12(i_a + \frac{v_o''}{12})$$

$$v_o'' = -12i_a - v_o''$$

$$2v_o'' = -12i_a$$

$$v_o'' = -6i_a$$


$$\text{from eq.: } -3 = -6i_a$$

$$\frac{1}{2} = i_a$$

$$0.5[A] = i_a$$

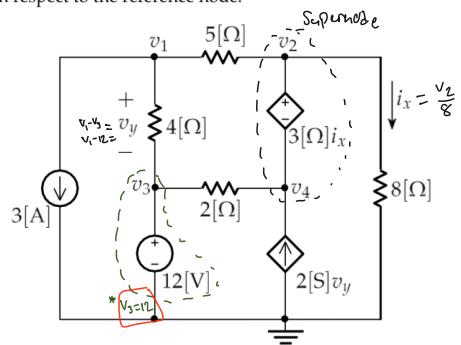Problem 2

For the following circuit, use the node voltage method to determine the values of v_1 , v_2 , v_3 , and v_4 with respect to the reference node.



Ans: $v_1=23.5V$, $v_2=52.9V$, $v_3=12V$, and $v_4=33.1V$

$$Q) V_1 : \left(3 + \frac{V_1 - V_3}{4} \right) + \frac{V_1 - V_2}{8} = 0$$

$$Q) 0 + 5V_1 - 5(V_3) + 4V_1 - 4V_2 = 0$$

$$4V_1 - 4V_2 - 5(4) + 4Q = 0$$

$$9V_1 - 4V_2 = 0$$

$$V_1 = \frac{4}{9}V_2$$

$$V_1 = \frac{1152}{49} \approx 23.5 \text{ [V]}$$

$$\text{Supernode eq., } V_2 - V_1 - 3i_x = 3\left(\frac{V_2}{8}\right)$$

$$V_2 - V_1 - \frac{3}{8}V_2 = 0$$

$$\frac{5}{8}V_2 = V_1$$

$$\frac{5}{8}\left[\frac{2592}{49}\right] = V_1$$

$$\frac{1620}{49} \approx 33.1 \text{ [V]} = V_1$$

Supernode 1 & 2:

$$\left(\frac{V_2 - V_1}{8} + \frac{V_2}{8} + \frac{V_1 - V_3}{2} - 2(V_1 - V_3) = 0 \right) 40$$

$$8V_2 - 8V_1 + 8V_2 + 20V_4 - 20V_3 - 80(V_1 - V_3) = 0$$

$$13V_2 - 8V_1 + 20V_4 - 20V_3 - 80V_1 + 80V_3 = 0$$

$$-88V_1 + 18V_2 + 20V_4 + 720 = 0$$

$$-88\left(\frac{4}{9}V_2\right) + 13V_2 + 20\left(\frac{5}{8}V_2\right) + 720 = 0$$

$$-\frac{352}{9}V_2 + 13V_2 + \frac{125}{8}V_2 + 720 = 0$$

$$V_2 \left(\frac{215}{144}\right) = -720$$

$$V_2 = \frac{2592}{49} \approx 52.9 \text{ [V]}$$


Problem 3

For the following circuit, you measure an open circuit potential $v_{oc} = 180/11 [V]$ between nodes a and b when you remove the load resistor $R_L = 40[\Omega]$, you

1

ECE 3355: Electronics

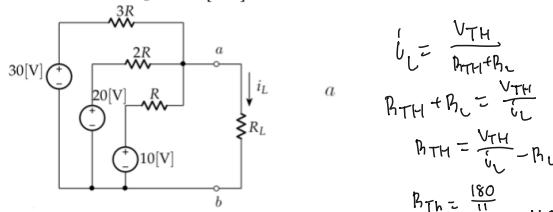measure a current $i_L = 163.6[\text{mA}]$. Find R .



Ans: 110Ω


$$i_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$R_{TH} + R_L = \frac{V_{TH}}{i_L}$$

$$R_{TH} = \frac{V_{TH}}{i_L} - R_L$$

$$R_{TH} = \frac{180}{163.6 \cdot 10^{-3}} - 40 = 110 \Omega$$

$$R_{TH} = 60.02 \approx 60$$

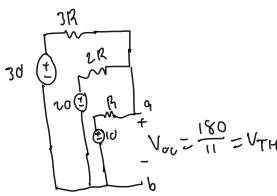


$$R_{TH}: \quad 3R || 2R || R = \frac{1}{\left(\frac{1}{3R} + \frac{1}{2R} + \frac{1}{R}\right)} \approx \frac{1}{\frac{1}{R} \left(\frac{1}{3} + \frac{1}{2} + 1 \right)} = \frac{6R}{11}$$

$$R_{TH} = \frac{6R}{11} = 60 \Omega$$


$$R = 110 \Omega$$

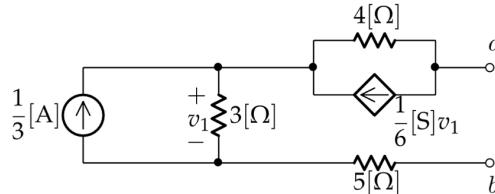Problem 4

Find the Thevenin equivalent for the following circuit between nodes *a* and *b*.



Ans: $1/3 \text{V}$; 10Ω

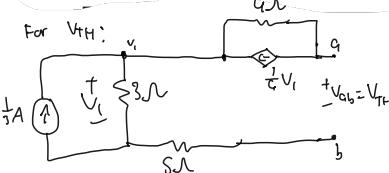

Node V_{TH} :

$$0.33 - \frac{V_1}{3} + \frac{1}{6}V_1 = 0$$

$$\frac{V_1}{4} = \frac{V_1}{12}$$

$$V_1 = \frac{1}{3}V_1$$

$$V_1 = \frac{1}{3}(1) = \frac{1}{3}$$

$$\therefore V_{ab} = V_{TH} = \frac{1}{3} \text{V}$$

KCL at V_1 :

$$-\left(\frac{1}{3} + \frac{V_1}{3} - \frac{1}{6}V_1 + \frac{V_1 - V_2}{4}\right) = 0$$

$$-V_1 + 4V_1 - 2V_1 + 3V_1 - 3V_2 = 0$$


$$5V_1 - 3V_2 = 0$$

$$5V_1 = 3V_2$$

$$V_1 = \frac{3}{5}V_2$$

$$V_1 = \frac{3}{5}(4) = \frac{12}{5}$$

$$V_2 = \frac{12}{5}$$

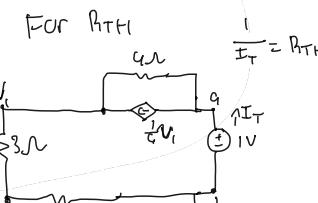

For R_{TH}

$$\frac{1}{I_T} = R_{TH}$$

$$KCL \text{ at } a: -I_T + \frac{V_1 - V_2}{4} + \frac{1}{6}V_1 = 0$$

$$I_T = \frac{V_1 - V_2}{4} + \frac{1}{6}V_1$$

$$I_T = \frac{1 - \frac{4}{3}}{4} + \frac{1}{6}\left(\frac{4}{3} - \frac{1}{2}\right)$$

$$5V_2 - 5V_1 + 3V_2 = 0$$

$$I_T = \frac{1}{20} + \frac{1}{8}\left(\frac{1}{10}\right)$$

$$I_T = \frac{1}{20} + \frac{1}{80} = \frac{2}{20}$$

$$I_T = \frac{1}{10}$$

$$\therefore R_{TH} = \frac{1}{10} = 10\Omega$$

$$KCL \text{ at } V_1: \left(\frac{V_1 - V_2}{4} + \frac{V_1 - V_2}{3} - \frac{1}{6}V_1\right) = 0$$

$$3V_1 - 3V_2 + 4V_1 - 4V_2 - 2V_1 = 0$$

$$7V_1 - 3V_2 - 2(V_1 - V_2) = 0$$

$$5V_1 - 2V_2 = 3$$

$$5V_1 = 3 + 2V_2$$

$$5V_1 = 3 + 2\left(\frac{5}{6}V_1\right)$$


$$5V_1 = 3 + \frac{5}{3}V_1$$

$$\frac{10}{3}V_1 = 3$$

$$V_1 = \frac{9}{10}$$

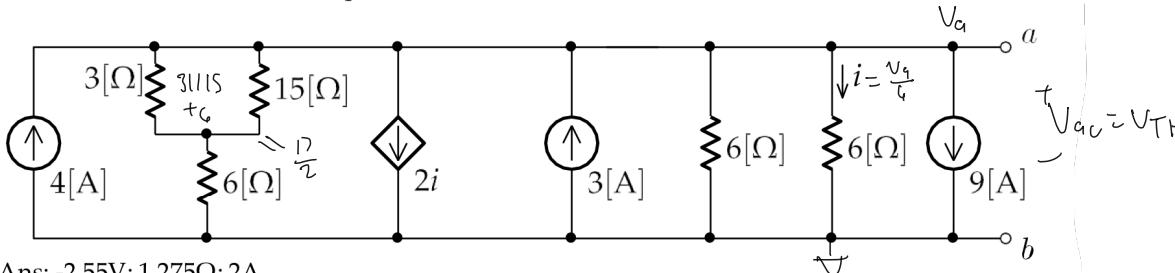Problem 5

Find the Thevenin or Norton equivalent for the circuit below between nodes a and b .



Ans: -2.55V; 1.275Ω; 2A

For V_{TH} :

$$\text{KCL at } a: -i + \frac{V_a}{8.5} + 2i - 3 + \frac{V_a}{6} + \frac{V_a}{4} + 9 = 0$$

$$2 + \frac{V_a}{8.5} + 2\left(\frac{V_a}{6}\right) + \frac{2}{4}V_a = 0$$

$$2 + \frac{V_a}{8.5} + \frac{1}{6}V_a = 0$$

$$\frac{40}{51}V_a = -2$$

$$V_a = -2.55 \text{ V}$$

$$\therefore V_{TH} = -2.55 \text{ V}$$

For R_{TH}

$$\text{KCL at } a: \frac{V_a}{8.5} + 2i + \frac{V_a}{4} + \frac{V_a}{6} - i_T = 0$$

$$\frac{V_a}{8.5} + 2\left(\frac{V_a}{6}\right) + \frac{2}{4}V_a = i_T$$

$$\frac{40}{51}V_a + \frac{V_a}{6} = i_T$$

$$\frac{40}{51}V_a = i_T$$

$$\frac{40}{51} = i_T$$

$$\therefore R_{TH} = \frac{V_T}{I_N} = \frac{1}{\frac{40}{51}} = \frac{51}{40} \Omega$$

$$R_{TH} = 1.275 \Omega$$


$$\therefore I_N = \frac{V_{TH}}{R_{TH}} = 2 \text{ A}$$

Problem 6


Find the Thévenin equivalent circuit at terminals (a,b) in the circuit below.

2

ECE 3355: Electronics

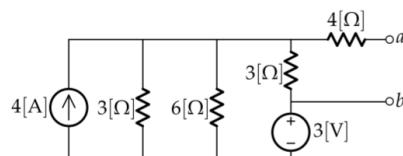

Ans: 3V; $26/5 \Omega$

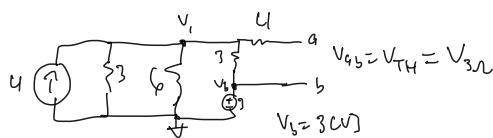

$$\text{At } V_1: -4 + \frac{V_1}{3} + \frac{V_1 - V_2}{6} + \frac{V_1 - V_3}{3} = 0$$

$$V_1 \left(\frac{1}{3} + \frac{1}{6} + \frac{1}{3} \right) - \frac{V_2}{3} = 4$$

$$V_1 \left(\frac{5}{6} \right) = 4$$

$$V_1 = 4.8 \text{ [V]} \quad \therefore \quad V_{ab} = V_{TH} = V_{3,2} = V_1 - V_2$$

$$V_{TH} = 4.8 - 3 = 1.8 \text{ [V]}$$


$$R_{TH}: \quad \begin{array}{c} 4 \\ | \\ 3 \end{array} \quad \begin{array}{c} 4 \\ | \\ 3 \end{array}$$

$$(3||6||3) + 4 = \frac{26}{5} \Omega$$

$$R_{TH} = \frac{26}{5} \Omega$$

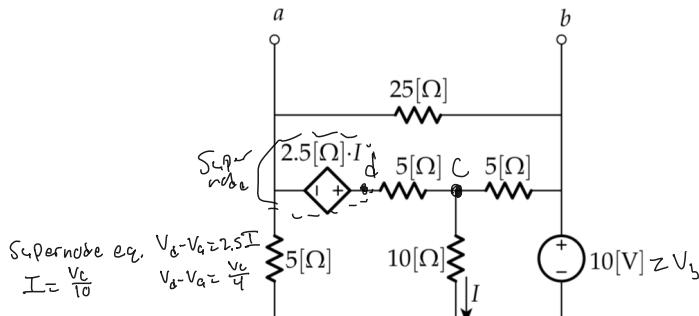Problem 7

Find the Thévenin equivalent circuit at terminals (a,b) for the circuit below



$$\text{Ans: } -50/7\text{V}; 75/28\Omega$$

V_{TH} ; Node V_0 lit

$$\text{Supernode: } \left(\frac{V_a - V_b}{2s} + \frac{V_a}{s} + \frac{V_d - V_c}{s} = 0 \right) 2s$$

$$V_a - V_b + sV_a + sV_d - sV_c = 0$$

$$sV_a - 10 + sV_d - sV_c = 0$$

$$s(V_d - \frac{V_c}{4}) + sV_d - sV_c = 10$$

$$11V_d - \frac{13}{2}V_c = 10$$

$$\text{at C: } \left(\frac{V_c - V_d}{s} + \frac{V_c}{10} + \frac{V_c - V_b}{s} = 0 \right) 10$$

$$2V_c - 2V_d + V_c + 2V_c - 2V_b = 0$$

$$5V_c - 2V_d = 20$$

$$\begin{aligned} 11V_d - \frac{13}{2}V_c &= 10 \\ + (-2)V_d + sV_c &= 20 \\ + 22V_d + 5sV_c &= 220 \end{aligned}$$

$$42V_c = 240$$

$$V_c = \frac{40}{7}$$

$$\therefore V_d = \frac{s(40)}{2} - 20$$

$$V_d = \frac{30}{7}$$


$$\therefore V_a = V_d - \frac{V_c}{4}$$

$$V_a = \frac{30}{7} - \frac{40}{28}$$

$$V_a = \frac{20}{7}$$

$$V_{TH} = V_{ab} = \frac{20}{7} - 10$$

$$V_{TH} = -\frac{50}{7}$$

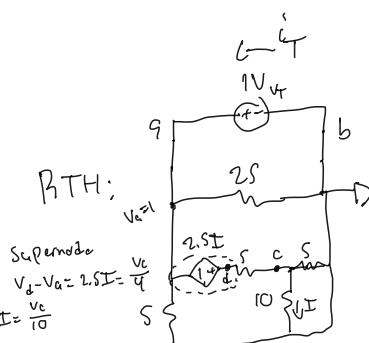

$$\text{at } V_a: \left(\frac{V_c - V_d}{s} + \frac{V_c}{10} + \frac{V_c - V_b}{s} = 0 \right) 10$$

$$2V_c - 2V_d + V_c + 2V_c = 0$$

$$5V_c = 2V_d$$

$$V_c = \frac{2}{5}V_d$$

$$\text{Supernode: } V_d = V_a + \frac{(2sV_c)}{4}$$

$$V_d = V_a + \frac{V_c}{10}$$

$$\frac{q}{10}V_d = V_a$$

$$V_d = \frac{10}{q}V_a \text{ or } \frac{5}{2}V_c = \frac{10}{q}V_a$$

$$V_c = \frac{4}{5}V_a$$

$$\text{at } V_c: \left(\frac{V_d - V_a}{2s} + \frac{V_d}{s} + \frac{V_d - V_b}{s} = 0 \right) 2s$$

$$V_a + sV_a + sV_d - sV_c = 2sI$$

$$s(V_a + s(\frac{10}{q}V_a) - s(\frac{4}{5}V_a)) = 2sI$$

$$\frac{28}{25}V_a = 2sI$$


$$\frac{28}{25}V_a = i_T$$

$$\frac{28}{25}CAj = i_T \quad \therefore R_{TH} = \frac{V_T}{i_T} = \frac{1}{\frac{28}{25}}$$



$$R_{TH} = \frac{25}{28} \text{ [CL]}$$

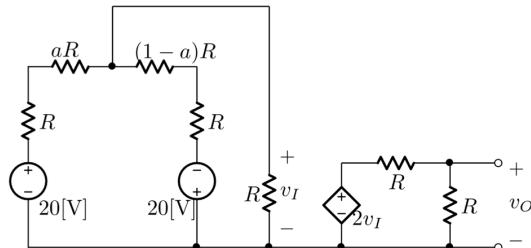Problem 8

For the following circuit determine the value of v_o for $a=1/2$ and $a=1/4$



$$a = \frac{1}{2}$$

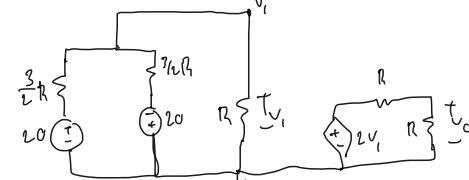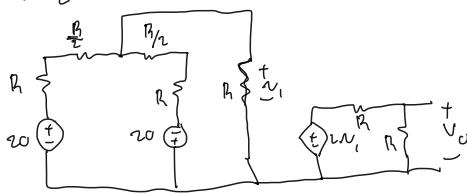

$$\text{Node } v_i: \frac{v_i - 20}{\frac{1}{2}R} + \frac{v_i + 20}{\frac{1}{2}R} + \frac{v_i}{R} = 0$$


$$v_i \left(\frac{4}{5R} + \frac{4}{7R} + \frac{1}{R} \right) - \frac{80}{5R} + \frac{80}{7R} = 0$$

$$v_i \left(\frac{83}{35R} \right) - \frac{32}{7R} = 0$$

$$v_i \left(\frac{83}{35R} \right) = \frac{32}{7R}$$

$$v_i = \frac{160}{83}$$

$$v_i = 0$$

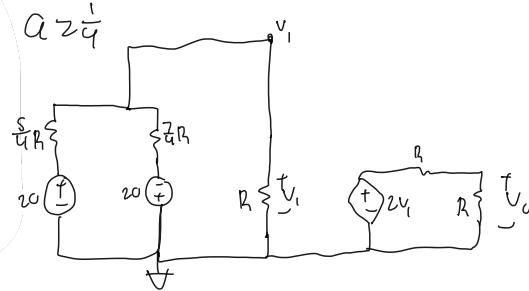

$$\text{Node } v_i: \frac{v_i - 20}{\frac{1}{2}R} + \frac{v_i + 20}{\frac{1}{2}R} + \frac{v_i}{R} = 0$$

$$v_i \left(\frac{4}{5R} + \frac{4}{7R} + \frac{1}{R} \right) - \frac{80}{5R} + \frac{80}{7R} = 0$$

$$v_i \left(\frac{83}{35R} \right) - \frac{32}{7R} = 0$$

$$v_i \left(\frac{83}{35R} \right) = \frac{32}{7R}$$

$$v_i = \frac{160}{83}$$

$$\text{At } v_o: \frac{v_o - 2v_i}{R} + \frac{v_o}{R} = 0$$

$$v_o \left(\frac{1}{R} + \frac{1}{R} \right) = 2 \left(\frac{160}{83} \right)$$

$$v_o \left(\frac{2}{R} \right) = \frac{320}{83R}$$

$$v_o = \frac{160}{83} \approx 1.93 \text{ V}$$


Problem 9

- a. Determine the output voltage (v_o) in the circuit below in terms of v_s

3

ECE 3355: Electronics

- b. Specify the linear range for v_s

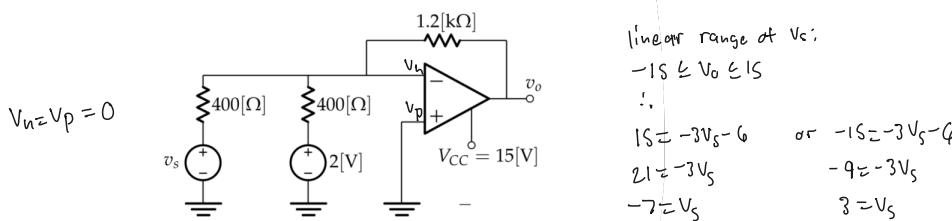

Ans: $-3v_s - 6[V]$ for $-7[V] < v_s < 3[V]$

$$\text{KCL at } v_n: \left(\frac{v_n - v_s}{400} + \frac{v_n - 2}{400} + \frac{v_n - v_o}{1.2k} = 0 \right) 1.2k$$

$$3v_n - 3v_s + 3v_n - 6 + v_n - v_o = 0$$

$$v_o = -3v_n - 3v_s - 6$$

$$v_o = -3v_s - 6$$

linear range of v_s :

$$-15 \leq v_o \leq 15$$

∴

$$15 = -3v_s - 6 \quad \text{or} \quad -15 = -3v_s - 6$$

$$21 = -3v_s \quad -9 = -3v_s$$

$$-7 = v_s \quad 3 = v_s$$

$$-7 \leq v_s \leq 3 \text{ [V]}$$