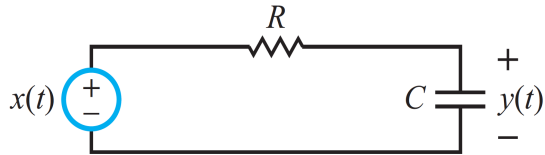


1. (40 pts) For the following RC circuit, calculate the following outputs for $x(t) = 25 \cos(3t)u(t)$ when $R = 250k\Omega$, $C = 1\mu F$, and an initial capacitor voltage of 1V.



- Zero-input response
 - Zero-state response
 - Transient response
 - Steady-state response
 - Natural response
 - Forced response
2. (40 pts) Given an LTI system with an impulse response $h(t) = 2\delta(t) + e^{-4t} \sin(2t) u(t)$, determine the following:
- $H(s)$
 - $\hat{H}(\omega)$
 - Poles and zeros of the system
 - LCCDE description of the system
 - Output response $y(t)$ to input $x(t) = 2te^{-5t}u(t)$. Assume zero initial conditions.
3. (20 pts) Rewrite the following circuit in the s -domain.
Initial conditions: Capacitor voltage = 1V. Inductor current = 0.1A

