

1. (20 points) Draw a minimal op-amp circuit that realizes the following transfer function:

$$H(s) = \frac{3s^2 + 4s + 5}{s^2 + 6s + 7}$$

2. (30 points) Write down the phasor representation for each of the following signals:

a. (5 pts) $x_1(t) = 12 \cos(2t)$

b. (5 pts) $x_2(t) = 20 \cos(3t + 45^\circ)$

c. (5 pts) $x_3(t) = 10 \sin(2t + 30^\circ)$

d. (5 pts) $x_4(t) = 35 \cos(2t) + 22 \sin(2t + 45^\circ)$

e. (10 pts) $x_5(t) = \frac{d}{dt} \{35 \cos(2t) + 22 \sin(2t + 45^\circ)\}$. Please also express the result in the time domain.

f. (10 pts) $x_6(t) = \int [35 \cos(2\tau) + 22 \sin(2\tau + 45^\circ)] d\tau$. Please also express the result in the time domain.

3. (20 points) Given two phasor voltages $\mathbf{V}_1 = 10e^{j60^\circ}$, and $\mathbf{V}_2 = 5e^{j45^\circ}$, calculate the following quantities:


a. $\mathbf{V}_1 + \mathbf{V}_2$

b. $\mathbf{V}_1 - \mathbf{V}_2$

c. $\mathbf{V}_1 \mathbf{V}_2$

d. $\frac{\mathbf{V}_1}{\mathbf{V}_2}$

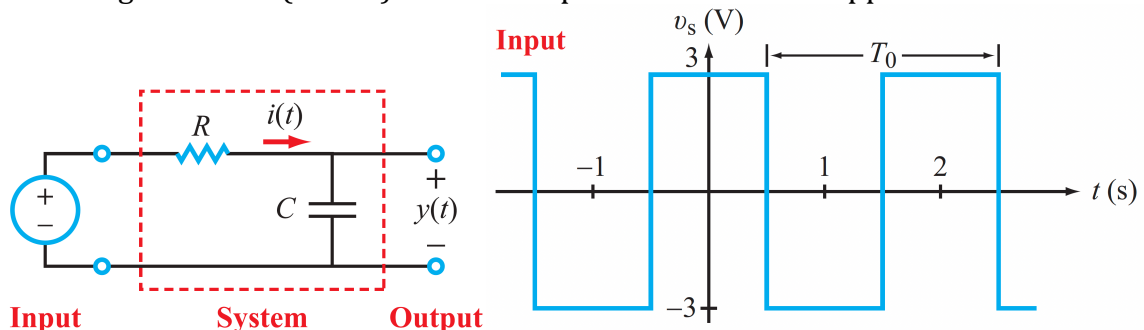4. (30 points) calculate the first 3 terms of the output voltage, at $(\omega_0, 3\omega_0, 5\omega_0)$ for the following RC circuit ($RC = 1$) when the input shown below is applied:



Use the Fourier series expansion in equation 5.13 of the textbook:

$$v_s(t) = \frac{12}{\pi} \left(\cos \omega_0 t - \frac{1}{3} \cos 3\omega_0 t + \frac{1}{5} \cos 5\omega_0 t - \dots \right), \quad (5.13)$$