

1. Given the transfer function

$$H(j\omega) = \frac{j\frac{\omega}{10} \left(1 + j\frac{\omega}{100}\right)}{(1 + j\frac{\omega}{10})(1 + j\frac{\omega}{10,000})(1 + j\frac{\omega}{1,000})}$$

sketch the Bode magnitude and phase plot using the straight-line approximations.

$$Z_1 = 100$$

$$P_1 = 10$$

$$P_2 = 1K$$

$$P_3 = 10K$$

$$H(j\cdot 10) \approx j$$

$$|H(j\omega)| \approx j\omega$$

$$\angle H(j\omega) \approx 90^\circ$$


$$+20 \frac{d\theta}{d\omega}$$

$$-20 \frac{d\theta}{d\omega}$$

$$H(j\omega) \approx j$$

$$|H(j\omega)| \approx j\omega$$

$$\angle H(j\omega) \approx 90^\circ$$

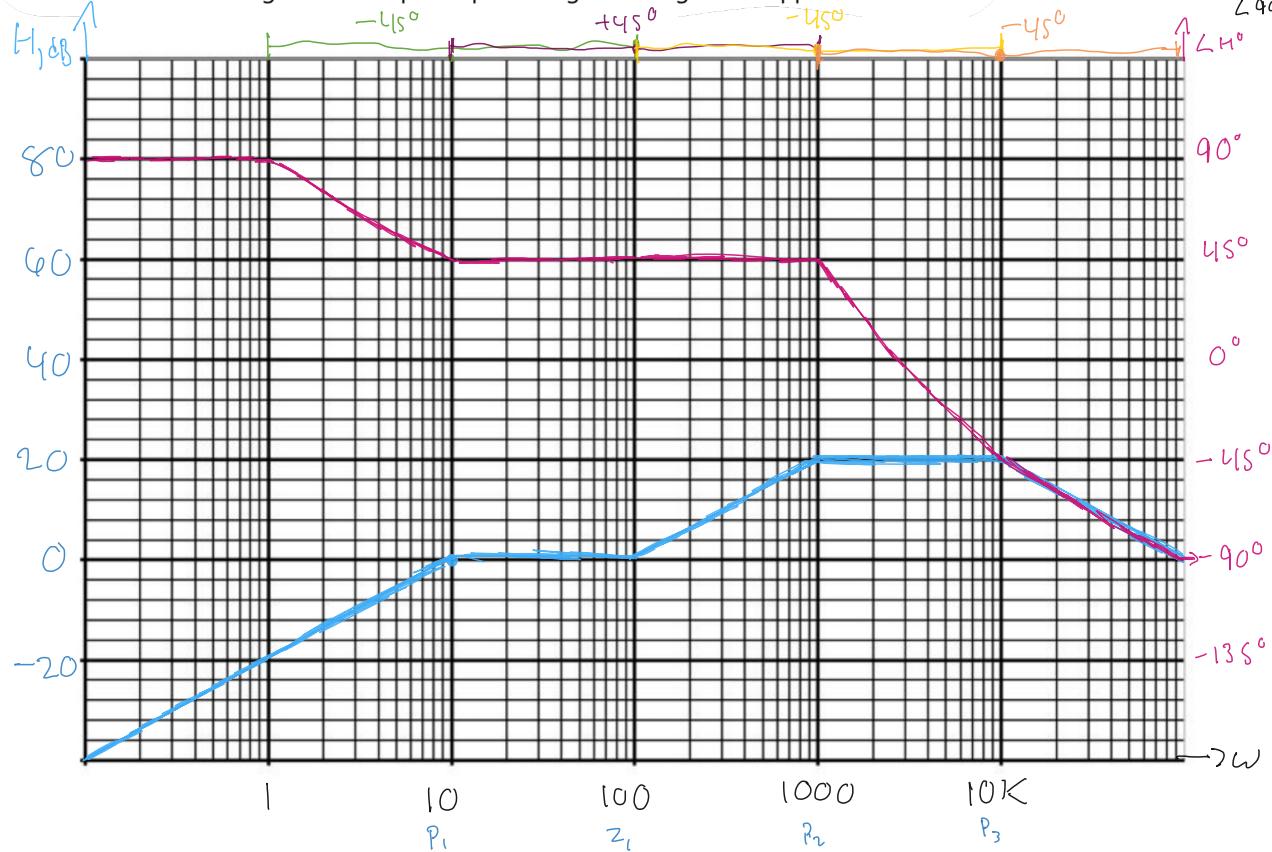

2. Given the transfer function


$$H(j\omega) = \frac{slope \frac{d\text{dB}}{d\log \omega} \text{ initial}}{60 \cdot j \frac{\omega}{30}} \quad P_1 = 30 \quad P_2 = 20K$$

$$(1 + j\frac{\omega}{30})(1 + j\frac{\omega}{20,000}) \quad -20 \frac{d\theta}{d\omega}$$

sketch the Bode magnitude and phase plots using straight-line approximations.

$$H(j\cdot 1) \approx 2j \quad |H(j\cdot 1)| \approx 2 \quad 20 \log(2) \approx 6 \text{ dB}$$

$$|H(j\omega)| = 2j\omega \quad \angle H(j\omega) \approx 90^\circ$$

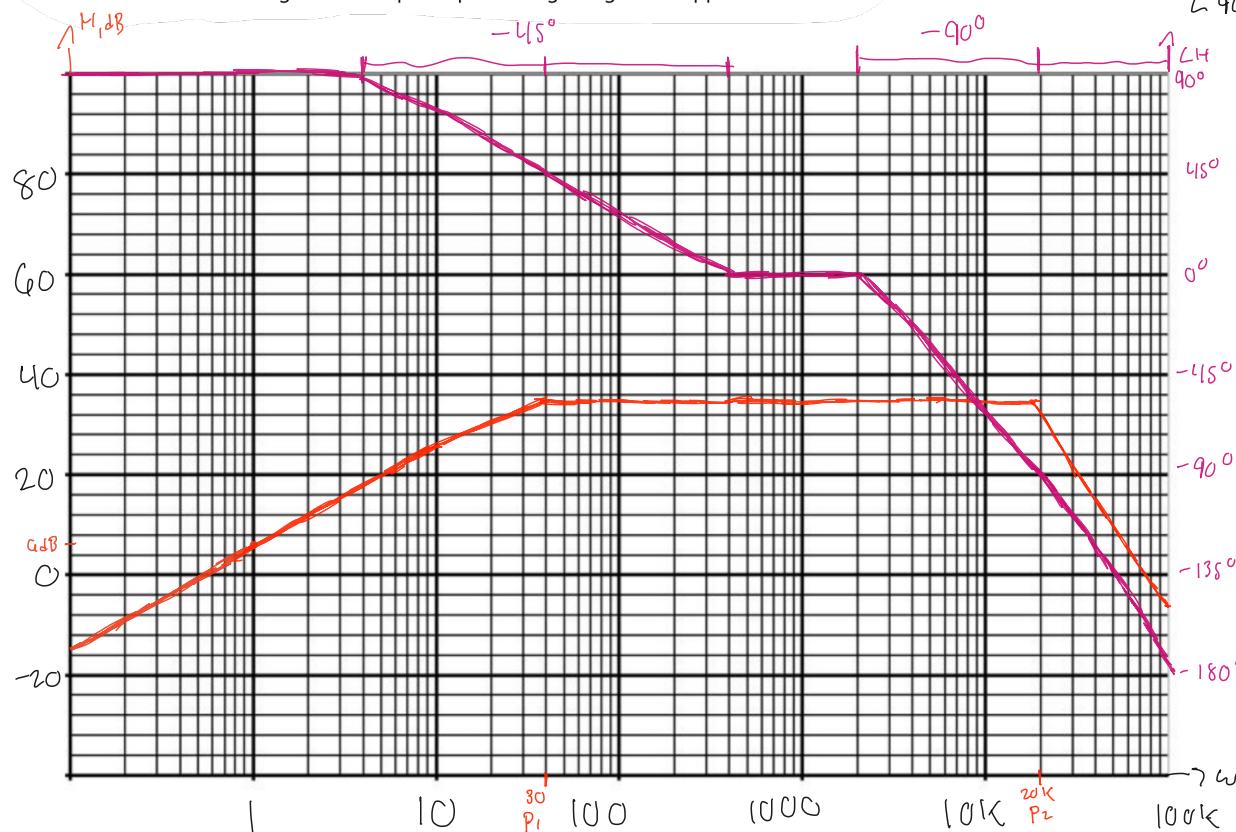


3. For the circuit below show

$$\frac{v_c}{v_b} = \frac{-\beta R_L}{r_\pi + (\beta + 1)R_E}$$

and
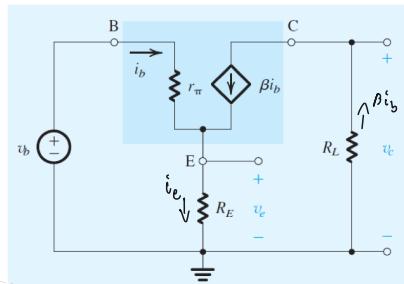
$$\frac{v_e}{v_b} = \frac{R_E}{R_E + [r_\pi/(\beta + 1)]}$$



$$V_C = -R_L \beta i_b$$

$$\frac{V_C}{V_b} = \frac{-\beta R_L \beta i_b}{r_\pi (r_\pi + R_E(1+\beta))}$$

$$\frac{V_b - V_e}{r_\pi} = i_b$$

$$\frac{V_C}{V_b} = -\frac{\beta R_L \beta}{r_\pi + R_E(1+\beta)}$$

$$V_b - V_e = i_b r_\pi$$

$$V_b = i_b r_\pi + i_b R_E(1+\beta)$$

$$V_b = i_b (r_\pi + R_E(1+\beta))$$


$$KCL \text{ at } E: i_e = i_b + \beta i_b$$

$$i_e = i_b (1 + \beta)$$

$$V_C = R_E i_e = R_E i_b (1 + \beta)$$

$$\frac{V_C}{V_b} = \frac{R_E i_b (1 + \beta)}{i_b (r_\pi + R_E(1 + \beta))} \cdot \frac{\frac{1}{(1 + \beta)}}{\frac{1}{(1 + \beta)}} = \frac{R_E}{\frac{r_\pi}{(1 + \beta)} + R_E}$$

4. For the circuit shown below, first evaluate $H_i(j\omega) = V_i(j\omega)/V_s(j\omega)$ and the corresponding cutoff (corner) frequency. Second, evaluate $H_o(j\omega) = V_o(j\omega)/V_i(j\omega)$ and the corresponding cutoff frequency. Put each of the transfer functions in the standard form discussed in class, and combine them to form the overall transfer function, $H(j\omega) = H_i(j\omega) \times H_o(j\omega)$. Provide a Bode magnitude plot for $|H(j\omega)|$. What is the bandwidth between 3-dB cutoff points?

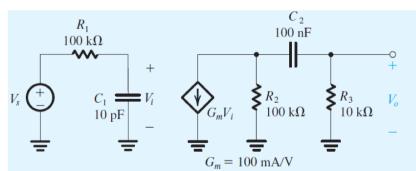

$$H_i(j\omega) = \frac{V_i(j\omega)}{V_s(j\omega)}$$

$$V_i = V_s \left(\frac{C_1}{R_1 + C_1} \right)$$

$$\frac{V_i(j\omega)}{V_s(j\omega)} = \frac{\frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} = \frac{1}{1 + j\omega R_1 C_1}$$


$$\chi_i = R_1 C_1 = 1 \mu$$

$$\omega_i = \frac{1}{\tau_i} = 1 \cdot 10^4$$

$$f_i \approx 15 \text{ kHz}$$

$$H_o(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$$

Recall:

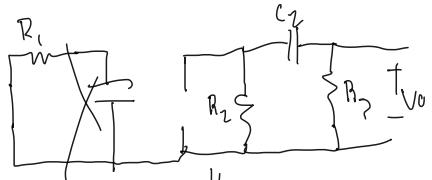

$$V_o = (-100m V_i) \left(\frac{R_2 R_3}{R_2 + R_3 + \frac{1}{j\omega C_2}} \right)$$

$$\frac{V_o}{V_i} = -100m \left(\frac{j\omega R_2 R_3 C_2}{j\omega C_2 (R_2 + R_3) + 1} \right)$$

$$\chi_2 = (R_2 + R_3) C_2 = 11 \mu$$

$$\omega_2 = \frac{1}{11 \mu} \approx 90$$

$$f_2 \approx 14.5 \text{ kHz}$$

$$H(j\omega) = H_i(j\omega) H_o(j\omega)$$

$$= \left(\frac{1}{1 + j\omega \tau_i} \right) \left(-100m \frac{R_2 R_3}{R_2 + R_3} \left(\frac{j\omega C_2 (R_2 + R_3)}{j\omega C_2 (R_2 + R_3) + 1} \right) \right) \cdot \frac{R_2 + R_3}{R_2 + R_3}$$

$$H(j\omega) = \left(\frac{1}{1 + j\omega \tau_i} \right) \left(-100m \frac{R_2 R_3}{R_2 + R_3} \left(\frac{j\omega C_2 (R_2 + R_3)}{j\omega C_2 (R_2 + R_3) + 1} \right) \right)$$


midband: $\omega_2 < \omega < \omega_1$

$$\omega_1 \ll 1: \frac{1}{1 + j\omega \tau_i} \approx 1$$

$$\omega_2 \gg 1: -100m \frac{R_2 R_3}{R_2 + R_3 + \frac{1}{j\omega C_2}} \approx -100m \frac{R_2 R_3}{R_2 + R_3} \approx -909 \therefore H(j\omega) = \left(\frac{1}{1 + j\omega \tau_i} \right) \left(-909 \left(\frac{j\omega \chi_2}{j\omega \chi_2 + 1} \right) \right)$$

$$H(j\omega) = \left(\frac{1}{1 + j\frac{\omega}{\omega_1}} \right) \left(-909 \left(\frac{j\frac{\omega}{\omega_1}}{1 + j\frac{\omega}{\omega_1}} \right) \right) = -909 \frac{j\frac{\omega}{\omega_1}}{(1 + j\frac{\omega}{\omega_1})(1 + j\frac{\omega}{\omega_1})}$$

since highpass
+ lowpass gives
band pass

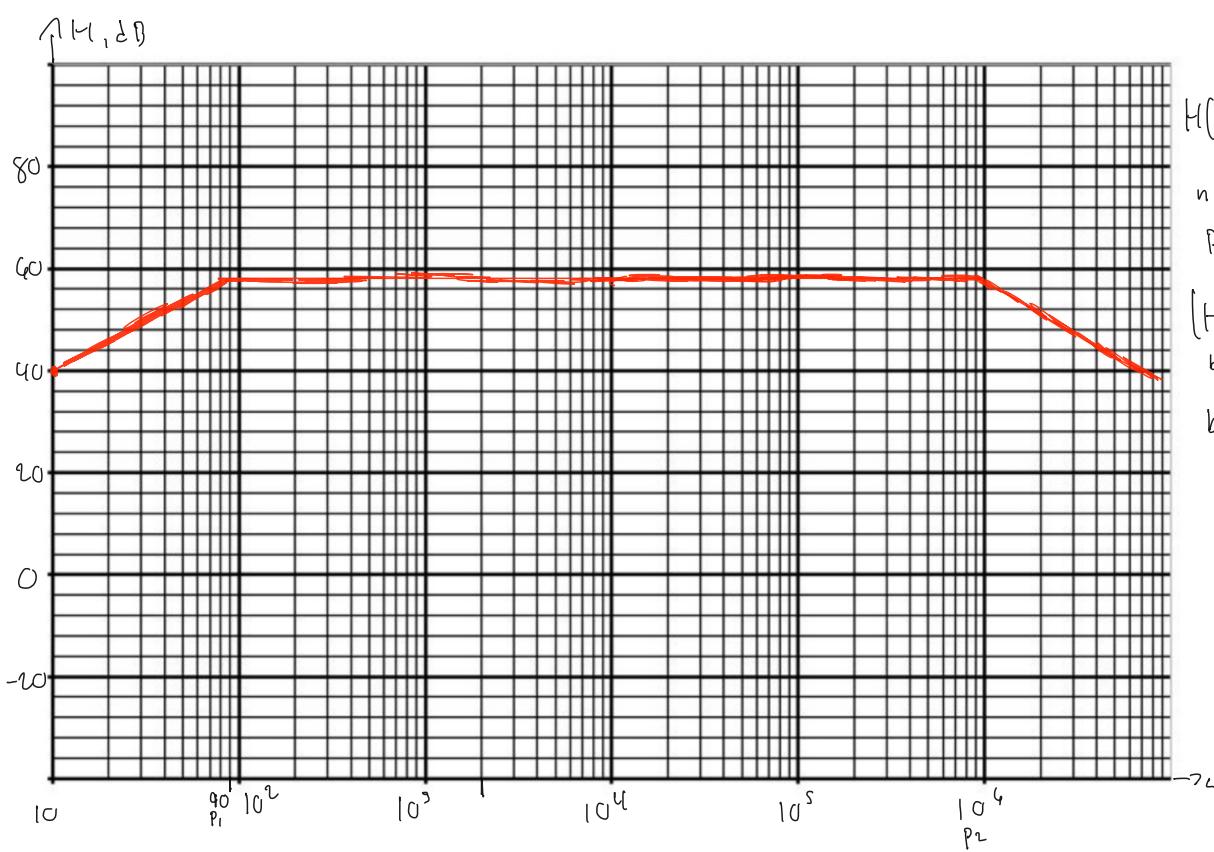

$$H(j\omega) = 40 \frac{j\omega}{(1+j\frac{\omega}{10^4})(1+j\frac{\omega}{10^4})}$$

no 0's


$$P_1 \approx 90 \quad P_2 \approx 1 \cdot 10^6$$

$$|H(j\omega)| \approx -40 \frac{10}{40} \approx 100 \approx 40 \text{ dB below midband}$$

bandwidth between 3dB cutoff points: $f_1 - f_2 \approx 159 \text{ KHz}$


$$\text{bandwidth} \approx 159.14 \text{ [kHz]}$$

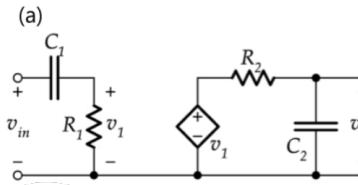5. Find the transfer function, $\frac{v_{out}}{v_{in}}$, for the following circuits. For (a) and (b), $R_1 = R_2 = 1 \text{ k}\Omega$, $C_1 = 1 \mu\text{F}$, and $C_2 = 100 \mu\text{F}$. For (c), $R_1 = 1 \text{ k}\Omega$, $R_2 = 100 \Omega$, $C_1 = C_2 = 1 \mu\text{F}$, and $K = 60$.



$$V_1 = V_{in} \left(\frac{R_1}{R_1 + \frac{1}{j\omega C_1}} \right) \quad V_{out} = V_1 \left(\frac{\frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} \right)$$
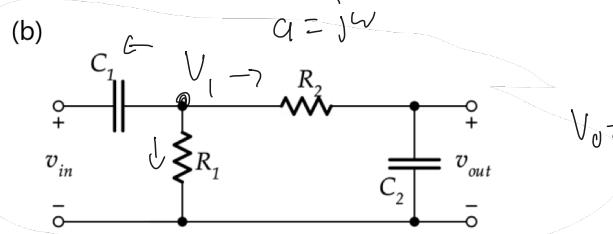
$$V_{out} = V_{in} \left(\frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1} \right) \left(\frac{1}{1 + j\omega R_2 C_2} \right)$$



$$\frac{V_1 - V_{in}}{\frac{1}{j\omega C_1}} + \frac{V_1}{R_1} + \frac{V_1 - V_o}{R_2} = 0$$

$$aC_1(V_1 - V_{in}) + \frac{V_1}{R_1} + \frac{V_1}{R_2} \left(1 - \frac{1}{1 + aR_2 C_2} \right) = 0$$

$$aC_1(V_1 - V_{in}) + \frac{V_1}{R_1} + \frac{V_1}{R_2} \left(\frac{1 + aR_2 C_2 - 1}{1 + aR_2 C_2} \right) = 0$$

$$aC_1(V_1 - V_{in}) + \frac{V_1}{R_1} + V_1 \frac{aC_2}{1 + aR_2 C_2} = 0$$

$$V_1 \left(aC_1 + \frac{1}{R_1} + \frac{aC_2}{1 + aR_2 C_2} \right) = aC_1 V_{in}$$

$$\frac{V_1}{V_{in}} = \frac{aC_1}{aC_1 + \frac{1}{R_1} + \frac{aC_2}{1 + aR_2 C_2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{j\omega R_1 C_1}{1 + j\omega R_1 C_1 + j\omega R_2 C_2 - \omega^2 R_1 R_2 C_1 C_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{j\omega R_1 C_1}{j\omega(R_1 C_1 + R_2 C_1) - \omega^2 R_1 R_2 C_1 C_2 + 1}$$

$$\frac{V_{out}}{V_{in}} = \frac{j\omega 0.001}{j\omega(0.101) - \omega^2(0.0001) + 1}$$

$$\frac{V_0}{V_{in}} = \frac{aC_1}{aC_1 + \frac{1}{R_1} + \frac{aC_2}{1 + aR_2 C_2}} \cdot V_0 = V_T \left(\frac{1}{1 + aR_2 C_2} \right)$$

$$\frac{V_0}{V_{in}} = \frac{aC_1}{(aC_1 + \frac{1}{R_1} + \frac{aC_2}{1 + aR_2 C_2})(1 + aR_2 C_2)}$$


$$\frac{V_0}{V_{in}} = \frac{aC_1}{(1 + aR_2 C_2)(aC_1 + \frac{1}{R_1}) + aC_2}$$

$$\frac{V_0}{V_{in}} = \frac{aC_1}{aC_1 + \frac{1}{R_1} + a^2 R_2 C_1 C_2 + a \frac{R_2 C_2}{R_1} + aC_2}$$

$$\frac{V_0}{V_{in}} = \frac{aR_1 C_1}{aR_1 C_1 + 1 + a^2 R_1 R_2 C_1 C_2 + aR_2 C_2 + aR_1 C_2}$$

$$\frac{V_0}{V_{in}} = \frac{a R_1 C_1}{a(R_1 C_1 + R_2 C_2 + R_1 C_2) + 1 + a^2 R_1 R_2 C_1 C_2} = \frac{j\omega 0.001}{j\omega(0.201) + 1 + (\omega)^2 0.0001}$$

(c)

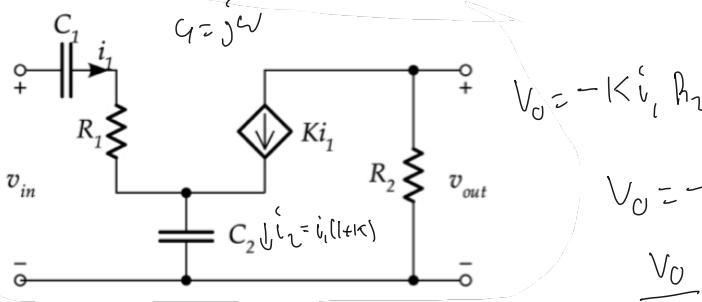

$$V_{in} = i_1 \left(\frac{1}{a C_1} + R_1 + \frac{1+K}{a C_2} \right)$$



$$V_{in} = i_1 \left(\frac{C_2 + C_1(1+K) + a C_1 C_2 R_1}{a C_1 C_2} \right)$$

$$i_1 = \frac{V_{in} a C_1 C_2}{C_2 + C_1(1+K) + a C_1 C_2 R_1}$$

$$V_0 = -K i_1 R_2$$

$$V_0 = -K \left[\frac{V_{in} a C_1 C_2 R_1}{C_2 + C_1(1+K) + a C_1 C_2 R_1} \right]$$

$$\frac{V_0}{V_{in}} = - \frac{j\omega 6 \cdot 10^{-9}}{62 \cdot 10^{-6} + j\omega 10^{-9}}$$

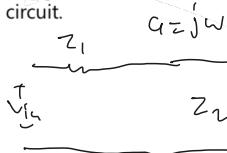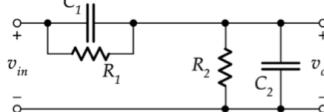6. Find the transfer function, $\frac{v_{out}}{v_{in}}$, for the following circuit.

$$z_1 = \frac{R_1}{a C_1} = \frac{R_1}{1 + a R_1 C_1}$$

$$z_2 = \frac{R_2}{a C_2} = \frac{R_2}{1 + a R_2 C_2}$$

$$= V_{in} \left[\frac{R_2}{(1+a R_2 C_2) \left(\frac{R_1}{1+a R_1 C_1} + \frac{R_2}{1+a R_2 C_2} \right)} \right]$$

$$\frac{V_0}{V_{in}} = \frac{R_2}{(1+a R_2 C_2) \left(\frac{R_1 + a R_1 R_2 C_2 + R_2 + a R_1 R_2 C_1}{(1+a R_1 C_1)(1+a R_2 C_2)} \right)}$$

$$\frac{V_0}{V_{in}} = \frac{R_2 (1 + a R_1 C_1)}{R_1 + R_2 + a R_1 R_2 C_1 + C_2}$$

$$\frac{V_0}{V_{in}} = \frac{R_2}{R_1 + R_2} \cdot \frac{1 + a R_1 C_1}{1 + \frac{a R_1 R_2 (C_1 + C_2)}{R_1 + R_2}}$$

but for frequency

$$\text{independence} \Rightarrow \frac{V_0}{V_{in}} = 0.1 = \frac{R_2}{R_1 + R_2}$$

$$(R_1 + R_2) 0.1 = R_2$$

$$0.1 R_1 + 0.1 R_2 = R_2$$

$$0.1 R_1 = 0.9 R_2$$

$$R_1 = 9 R_2$$

$$R_1 = 9(1M) = 9(M\Omega)$$

$$\therefore R_1 C_1 = R_2 C_2$$


$$C_1 = \frac{1M(30pF)}{9M}$$

$$C_1 = 3.33 [pF]$$

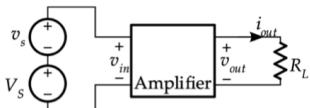7. An amplifier has a transfer characteristic that can be reasonably approximated by the expression

$$v_{out} = \begin{cases} -12V & -20V \leq v_{in} \leq 8V \\ 2v_{in} - 28V & 8V < v_{in} \leq 9V \\ 10v_{in} - 100V & 9V < v_{in} \leq 11V \\ 2v_{in} - 12V & 11V < v_{in} \leq 12V \\ 12V & 12V < v_{in} \leq 20V \end{cases}$$

- Sketch this transfer characteristic.
- Assume that $V_s = 10.5 \text{ V}$ and $v_s = A \sin(\omega t)$, where $A = 0.3 \text{ V}$ and $\omega = 60 \text{ rad/s}$, as shown in the figure below. For this signal level and DC bias value, what is the voltage gain, A_v ? Assume that $A_v = v_{out}/v_{in}$.
- Assume the above values for V_s and v_s and find an expression for $i_{out}(t)$ when $R_L = 100\Omega$.
- What are the largest values for v_s that will yield an undistorted output?




$$V_{in} = V_s + v_s = 10.5 + 0.3 \sin(\omega t)$$

$$V_{in, min} : \omega t = \frac{\pi}{2} \quad 10.5 - 0.3$$

$$max : \omega t = \frac{\pi}{2} \quad 10.5 + 0.3$$

$$10.2 \leq v_{in} \leq 10.8 \quad 9 \leq v_{in} \leq 11, \quad v_{out} = 10v_{in} - 100$$

$$\frac{v_{out}}{v_{in}} = A_v = 10$$

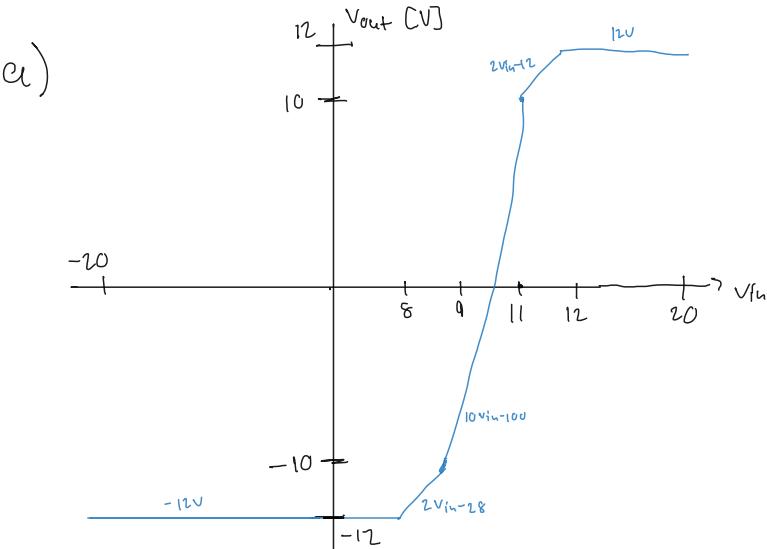

$$c) v_{out}(t) = i_{out}(t) \cdot R$$

$$10(10.5 + 0.3 \sin(60t)) - 100 = i_{out}(t) \cdot R$$

$$\frac{5 + 3 \sin(60t)}{100} = i_{out}(t)$$

$$i_{out}(t) = 50 + 30 \sin(60t) \text{ [mA]}$$

$$d) v_s = A \sin(60t)$$

$$\text{undistorted} \quad 9 \leq v_{in} \leq 11$$

$$9 \leq 10.5 + A \sin(60t) \leq 11$$

$$\text{largest } v_s \text{ value: } 10.5 + A \sin(60t) \leq 11$$

$$A \sin(60t) \leq 0.5$$

\therefore largest v_s value when $A = 0.5$ to be undistorted