

for  $R_{IN}$ :

$$KCL \text{ at } A: -i_{IN} - 6v_1 - i_1 = 0$$

$$i_{IN} = -6v_1 - \frac{v_1}{R_1}$$


$$i_{IN} = -6v_1 - \frac{(Gv_1)}{R_1}$$

$$i_{IN} = -6(Gv_1) + \frac{Gv_1}{R_1}$$

$$i_{IN} = Gv_1(G + \frac{1}{R_1})$$

$$R_{IN} = \frac{v_{IN}}{i_{IN}} = \frac{1}{(G + \frac{1}{R_1})}$$

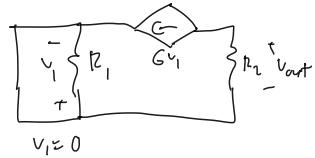for  $R_{out}$ : since  $v_{out}$  is across  $R_2$ ,  $R_{out} = R_2$



$$V_1 = -V_{IN}$$

$$KCL \text{ at } C: Gv_1 + i_2 = 0$$

$$\frac{v_{out}}{R_2} = -6v_1$$


$$v_{out} = -6v_1 \cdot R_2$$

$$v_{out} = -6(-v_{IN}) \cdot R_2$$

$$\frac{v_{out}}{v_{IN}} = GR_2 = A_v \text{ (gain)}$$

$$\therefore R_2 \leftarrow R_{out}$$

$$R_{out} = R_2$$

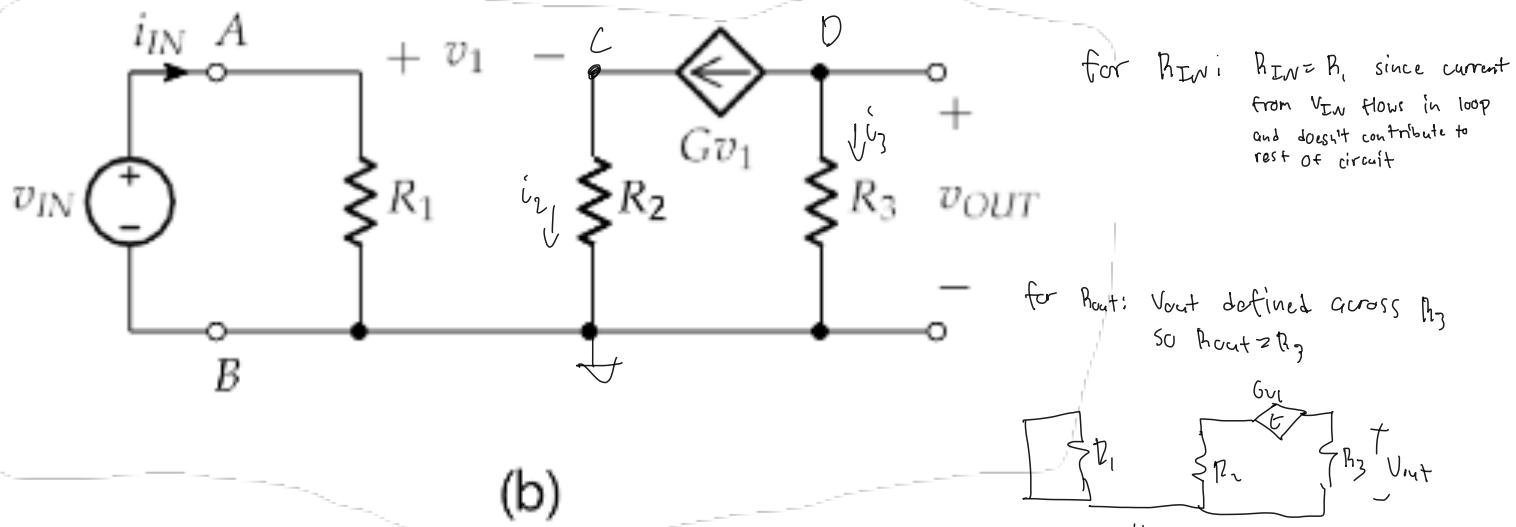

(b)

$$KCL \text{ at } C: -Gv_1 + i_2 = 0$$

$$i_2 = Gv_1$$

$$\frac{v_c}{R_2} = Gv_1$$

$$v_c = Gv_1 R_2$$

$$KCL \text{ at } D: Gv_1 + i_3 = 0$$

$$i_3 = -Gv_1$$

$$\frac{v_{out}}{R_3} = -Gv_1$$

$$v_{out} = -Gv_1 R_3$$

$$V_1 = v_{IN} - V_c$$


$$V_1 = v_{IN} - GV_1 R_2$$

$$V_1 + GV_1 R_2 = v_{IN}$$

$$v_{IN} = V_1 (1 + GR_2)$$

$$A_v = \frac{v_{out}}{v_{IN}} = \frac{-GV_1 R_3}{V_1 (1 + GR_2)}$$
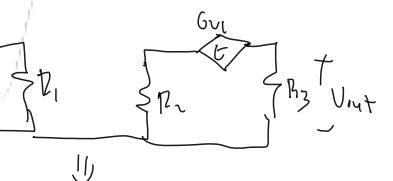
$$A_v = -\frac{GR_3}{1 + GR_2} \quad (\text{gain})$$




$$-V_1 \left\{ R_2 \left\{ Gv_1 \right\} R_3 \right\} V_{out}$$

$$V_1 = -GV_1 R_2$$

$$V_1 (GR_2) = 0$$

$$V_1 = 0 \quad \therefore \quad \left\{ R_3 \right\} V_{out}$$

$$= R_{out}$$

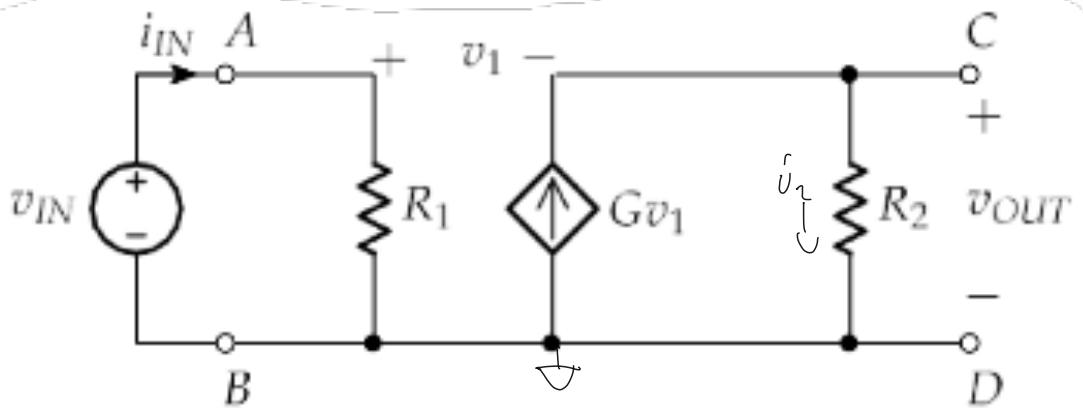


$R_1 = R_{IN}$  since  
in flows only in loop  
and  $V_{IN} = V_{IN} R_{IN}$   
 $\frac{V_{IN}}{V_{IN}} = R_{IN}$   
and  $i_{IN}$  only flows thru  
 $R_1$  i.e.  $R_1 = R_{IN}$


(c)

$$KCL \text{ at } C: -Gv_1 + \frac{v_c}{R_2} = 0 \quad * v_c = v_{out}$$

$$\frac{v_{out}}{R_2} = Gv_1$$
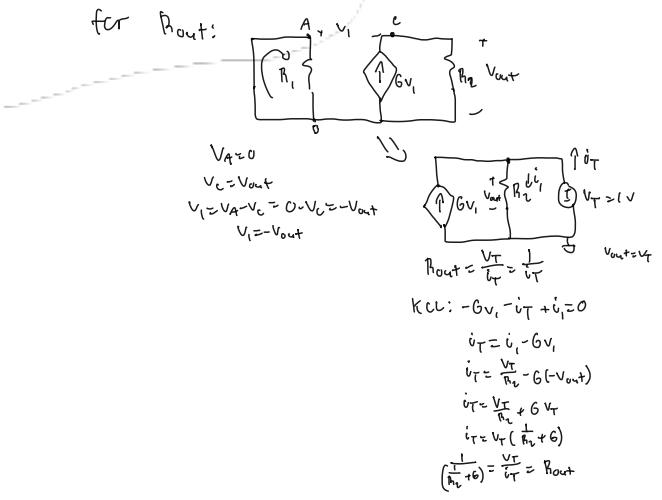
$$\begin{aligned} v_i &= v_{IN} - v_c = v_{IN} - v_{out} \\ &\frac{v_{out}}{R_2} = G(v_{IN} - v_{out}) \\ &\frac{v_{out}}{R_2} = Gv_{IN} - Gv_{out} \\ &\frac{v_{out}}{R_2} + Gv_{out} = Gv_{IN} \\ &v_{out} \left( \frac{1}{R_2} + G \right) = Gv_{IN} \\ &\frac{v_{out}}{v_{IN}} = \left( \frac{1}{R_2} + G \right) \end{aligned}$$



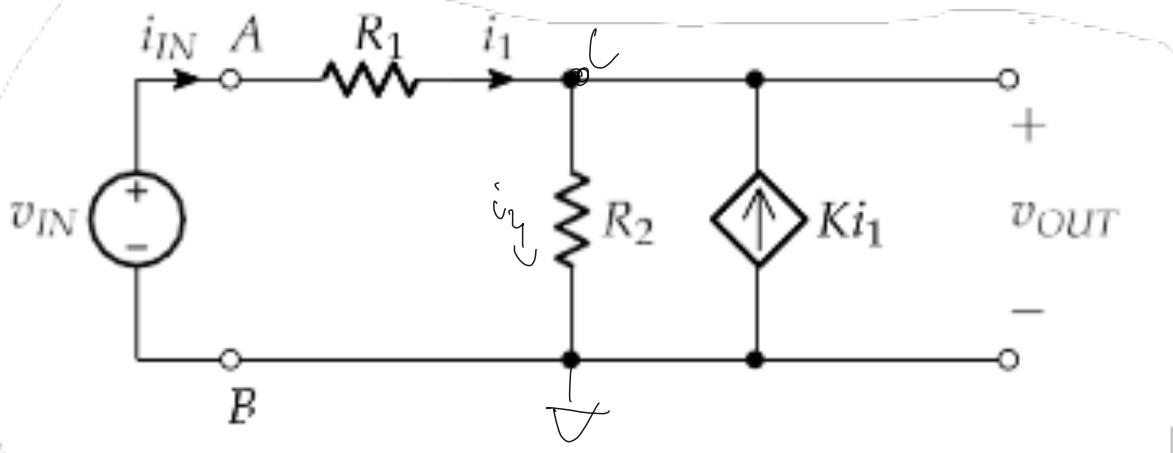

(d)

$$\begin{aligned}
 \text{KCL at } V_A: & -i_{IN} + i_1 = 0 \quad \text{KCL at } V_A: -i_1 + i_2 - Ki_1 = 0 \\
 i_1 &= i_{IN} \\
 \frac{V_A - V_L}{R_1} &= i_{IN} \\
 \frac{V_{IN} - V_{out}}{R_1} &= i_{IN} = i_1 \\
 & -\frac{V_A - V_L}{R_1} + \frac{V_L}{R_2} - K \left( \frac{V_A - V_L}{R_1} \right) = 0 \\
 & \frac{V_{out} - V_{IN}}{R_1} + \frac{V_{out}}{R_2} - K \left( \frac{V_{out} - V_{IN}}{R_1} \right) = 0 \\
 & \frac{V_{out} - V_{IN}}{R_1} + \frac{V_{out}}{R_2} + K \frac{V_{out} - V_{IN}}{R_1} = 0 \\
 & V_{out} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{K}{R_1} \right) + V_{IN} \left( -\frac{1}{R_1} - \frac{K}{R_1} \right) = 0 \\
 & V_{out} \left( \frac{1}{R_2} + \frac{1+K}{R_1} \right) = -V_{IN} \left( \frac{-1-K}{R_1} \right) \\
 & \frac{V_{out}}{V_{IN}} = \frac{\left( \frac{1+K}{R_1} \right)}{\left( \frac{1}{R_2} + \frac{1+K}{R_1} \right)} = \frac{1+K}{\left( \frac{R_1}{R_2} + 1 + K \right)} = A_V \text{ (gain)}
 \end{aligned}$$


For  $R_{IN}$ :  $R_{IN} = \frac{V_{IN}}{i_{IN}}$

$$i_{IN} = i_1 = \frac{V_{IN} - V_{out}}{R_1}$$

$$R_{IN} = \frac{V_{IN}}{\frac{V_{IN} - V_{out}}{R_1}}$$

$$R_{IN} = \frac{V_{IN} R_1}{V_{IN} - V_{out}}$$

For  $R_{out}$ :

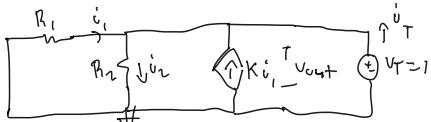

KCL at top node:  $-i_1 - Ki_1 - i_T + i_2 = 0$

$$i_T = i_2 - i_1 - Ki_1$$

$$i_T = \frac{V_T}{R_2} - \frac{V_T - V_L}{R_1} - K \left( \frac{V_T - V_L}{R_1} \right)$$


$$i_T = \frac{V_T}{R_2} + \frac{V_L}{R_1} + K \frac{V_L}{R_1}$$

$$i_T = V_T \left( \frac{1}{R_2} + \frac{1}{R_1} + \frac{K}{R_1} \right)$$

$$R_{out} = \frac{V_{out}}{i_{out}} = \frac{V_T}{i_T}$$

$$R_{out} = \frac{V_T}{V_T \left( \frac{1}{R_2} + \frac{1+K}{R_1} \right)}$$
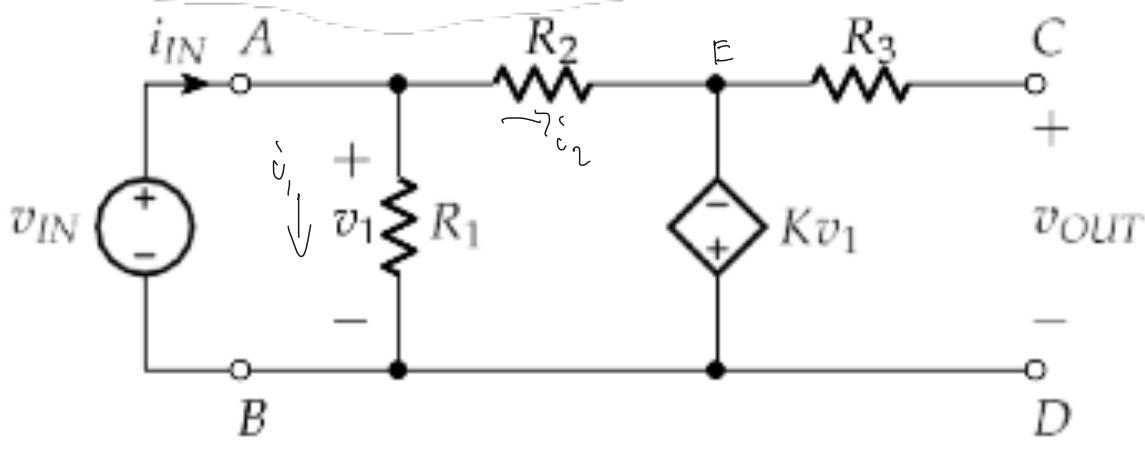
$$R_{out} = \frac{1}{\frac{1}{R_2} + \frac{1+K}{R_1}}$$



(e)

$$V_{IN} = V_i$$

$$V_{out} = -Kv_1$$

$$\text{for } R_{IN} = \frac{V_{IN}}{i_{IN}}$$

$$KCL \text{ at } A: i_{in} + i_1 + i_2 = 0$$

$$i_{IN} = i_1 + i_2$$

$$v_E = 0 - Kv_1 \\ = -Kv_{IN}$$


$$i_{IN} = \frac{V_{IN}}{R_1} + \frac{V_{IN} - v_E}{R_2}$$

$$i_{IN} = \frac{V_{IN}}{R_1} + \frac{V_{IN} - (-Kv_{IN})}{R_2}$$


$$i_{IN} = V_{IN} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{K}{R_2} \right)$$

$$\frac{V_{IN}}{i_{IN}} = R_{IN} = \frac{1}{\left( \frac{1}{R_1} + \frac{1+K}{R_2} \right)}$$

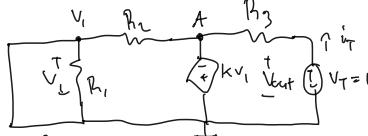
$$\text{For } R_{out} = \frac{V_{out}}{i_{out}} = \frac{V_T}{i_T} = \frac{1}{i_T}$$


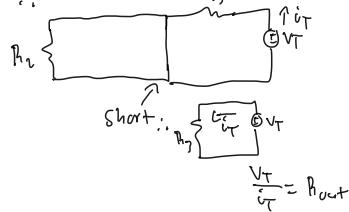
$$\text{short } ; V_i = 0 \therefore Kv_1 = 0$$



$$\frac{V_T}{i_T} = R_{out} = R_2$$

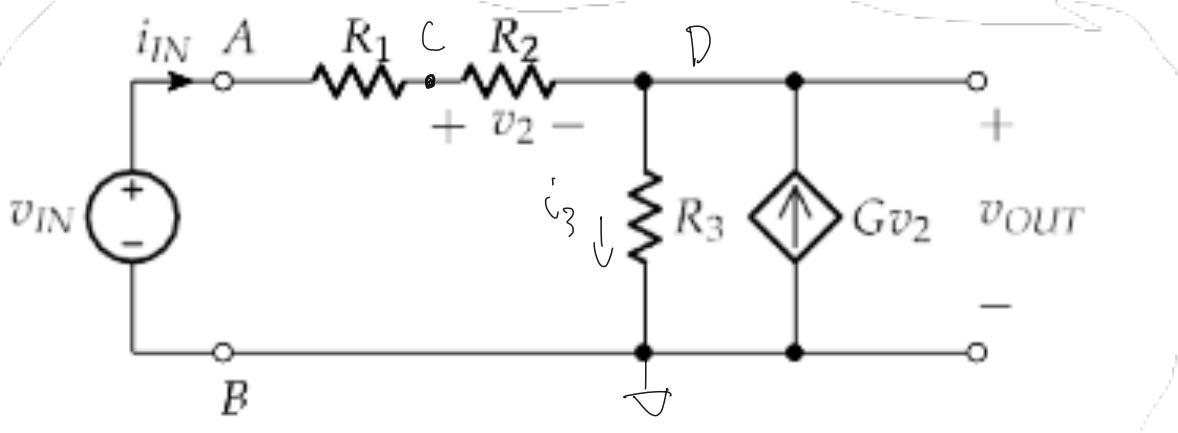

$$V_2 = i_{IN} R_2 \\ = \left( \frac{v_{IN} - v_{out}}{R_1 + R_2} \right) R_2$$

(f)

$$\text{KCL at } D: -i_N + i_3 - Gv_2 = 0$$

$$-\left( \frac{v_{IN} - V_D}{R_1 + R_2} \right) + \frac{V_D}{R_3} - Gv_2 = 0$$

$$\frac{V_{out} - V_{IN}}{R_1 + R_2} + \frac{V_{out}}{R_3} - G \left( \left( \frac{v_{IN} - v_{out}}{R_1 + R_2} \right) R_2 \right) = 0$$

$$V_{out} \left( \frac{1}{R_1 + R_2} + \frac{1}{R_3} + \frac{G R_2}{R_1 + R_2} \right) + V_{IN} \left( -\frac{1}{R_1 + R_2} - \frac{G R_2}{R_1 + R_2} \right) = 0$$

$$V_{out} \left( \frac{1}{R_1 + R_2} + \frac{1}{R_3} + \frac{G R_2}{R_1 + R_2} \right) = -V_{IN} \left( -\frac{1}{R_1 + R_2} - \frac{G R_2}{R_1 + R_2} \right)$$


$$\frac{V_{out}}{V_{IN}} = \frac{\left( \frac{1 + G R_2}{R_1 + R_2} \right)}{\frac{1 + G R_2}{R_1 + R_2} + \frac{1}{R_3}} = \frac{1 + G R_2}{1 + G R_2 + \frac{R_1 + R_2}{R_3}} = A_v \text{ (gain)}$$

$$\text{For } R_{IN} = \frac{V_{IN}}{i_{IN}}$$

$$i_{IN} = \frac{V_{IN} - V_{out}}{R_1 + R_2}$$

$$R_{IN} = \frac{V_{IN}}{\frac{V_{IN} - V_{out}}{R_1 + R_2}} = \frac{V_{IN}(R_1 + R_2)}{V_{IN} - V_{out}}$$
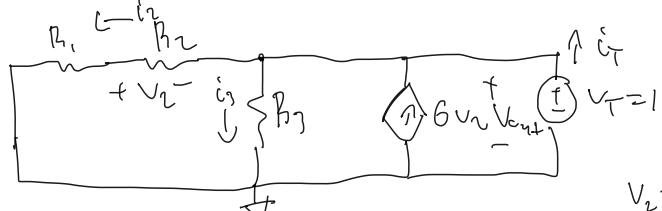
$$\text{For } R_{out} = \frac{V_{out}}{i_{out}} = \frac{V_T}{i_T}$$



$$V_2 = -i_2 R_2 \\ V_2 = -\left( \frac{V_T}{R_1 + R_2} \right) R_2$$

$$\text{KCL at top: } -i_T - Gv_2 + i_3 + i_2 = 0$$


$$-i_T - Gv_2 + \frac{V_T}{R_3} + \frac{V_T}{R_1 + R_2} = 0$$

$$-i_T - G \left( \frac{V_T}{R_1 + R_2} R_2 \right) + \frac{V_T}{R_3} + \frac{V_T}{R_1 + R_2} = 0$$

$$i_T = V_T \left( \frac{G R_2 + 1}{R_1 + R_2} + \frac{1}{R_3} + \frac{1}{R_1 + R_2} \right)$$

$$i_T = V_T \left( \frac{G R_2 + 1}{R_1 + R_2} + \frac{1}{R_3} \right)$$
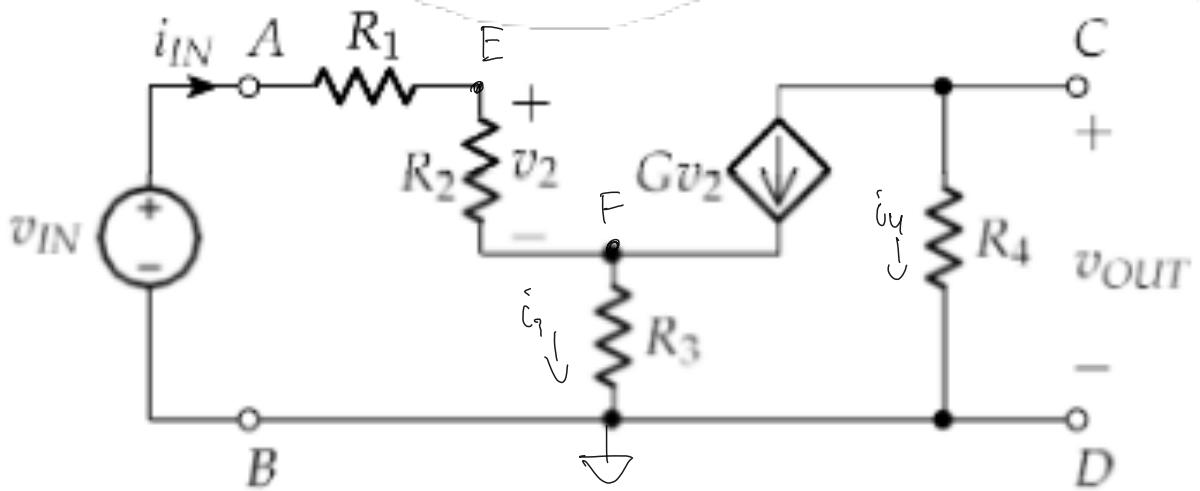
$$\frac{V_T}{i_T} = R_{out} = \frac{1}{\frac{G R_2 + 1}{R_1 + R_2} + \frac{1}{R_3}}$$



(g)

$$\text{KCL at } F: -i_{IN} + i_3 - Gv_2 = 0$$

$$-\left(\frac{V_{IN}-V_F}{R_1+R_2}\right) + \frac{V_F}{R_3} - Gv_2 = 0$$

$$\frac{V_F - V_{IN}}{R_1+R_2} + \frac{V_F}{R_3} - G\left(\frac{V_{IN}-V_F}{R_1+R_2}\right)R_2 = 0$$

$$V_F\left(\frac{1}{R_1+R_2} + \frac{1}{R_3} + \frac{GR_2}{R_1+R_2}\right) + V_{IN}\left(\frac{-1}{R_1+R_2} - \frac{GR_2}{R_1+R_2}\right) = 0$$


$$V_F = V_{IN} \frac{\left(\frac{1+GR_2}{R_1+R_2}\right)}{\frac{1+GR_2}{R_1+R_2} + \frac{1}{R_3}}$$

$$V_F = \frac{1+GR_2}{1+GR_2 + \frac{R_1+R_2}{R_3}}$$

$$V_F = \left( \frac{R_3(1+GR_2)}{R_3(1+GR_2) + R_1+R_2} \right) V_{IN} \Rightarrow$$

$$\text{For } R_{IN} = \frac{V_{IN}}{i_{IN}} = \frac{V_{IN}}{\frac{V_2}{R_2}} = \frac{V_{IN}}{\frac{V_{IN}}{D}} = D$$

$$R_{IN} = R_2(1+GR_2) + R_1 + R_2$$

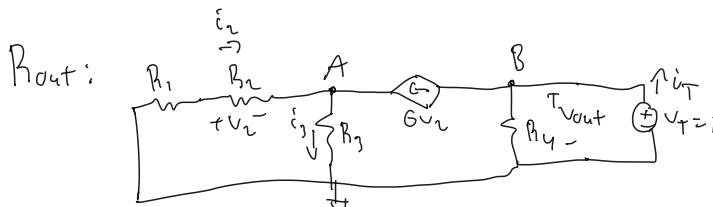

$$\text{KCL at } A: -i_2 + i_3 - Gv_2 = 0$$

$$-\left(\frac{0-V_A}{R_1+R_2}\right) + \frac{V_A}{R_3} - Gv_2 = 0$$

$$\frac{V_A}{R_1+R_2} + \frac{V_A}{R_3} - G\left(R_2\left(\frac{-V_A}{R_1+R_2}\right)\right) = 0$$

$$V_A \left(\frac{1}{R_1+R_2} + \frac{1}{R_3} + \frac{GR_2}{R_1+R_2}\right) = 0$$

$$V_A = 0 \quad \therefore V_T = 0 \quad \text{on } V_T = 0 - V_A = 0 - 0; \quad V_T = 0$$

$$\frac{V_{IN} - V_F}{R_1+R_2} = i_{IN} \quad V_T = V_E - V_F = i_N R_2 = \frac{V_{IN} - V_F}{R_1+R_2} R_2$$

$$\text{KCL at } C: i_4 + Gv_2 = 0$$

$$\frac{V_{out}}{R_4} + Gv_2 = 0$$

$$\frac{V_{out}}{R_4} = -G\left(\frac{R_2}{D} V_{IN}\right)$$

$$\frac{V_{out}}{V_{IN}} = -\frac{R_2 R_4}{D} G$$

$$A_V (\text{gain}) = G \frac{R_2 R_4}{R_3(1+GR_2) + R_1+R_2}$$


$$V_2 = \frac{R_2}{R_1+R_2} \left[ V_{IN} - \left[ V_{IN} \left( \frac{R_3(1+GR_2)}{R_3(1+GR_2) + R_1+R_2} \right) \right] \right] \quad D = R_3(1+GR_2) + R_1+R_2$$


$$V_2 = \frac{R_2}{R_1+R_2} \left[ V_{IN} \left( 1 - \frac{R_3(1+GR_2)}{D} \right) \right]$$

$$= \frac{R_2}{R_1+R_2} \left[ V_{IN} \left( \frac{D - R_3(1+GR_2)}{D} \right) \right]$$

$$V_2 = \frac{R_2}{R_1+R_2} \left[ V_{IN} \left( \frac{R_3(1+GR_2) + R_1+R_2 - R_3(1+GR_2)}{D} \right) \right]$$

$$V_2 = R_2 \frac{V_{IN}}{D}$$

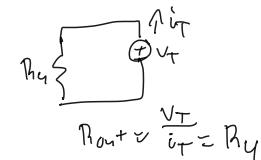

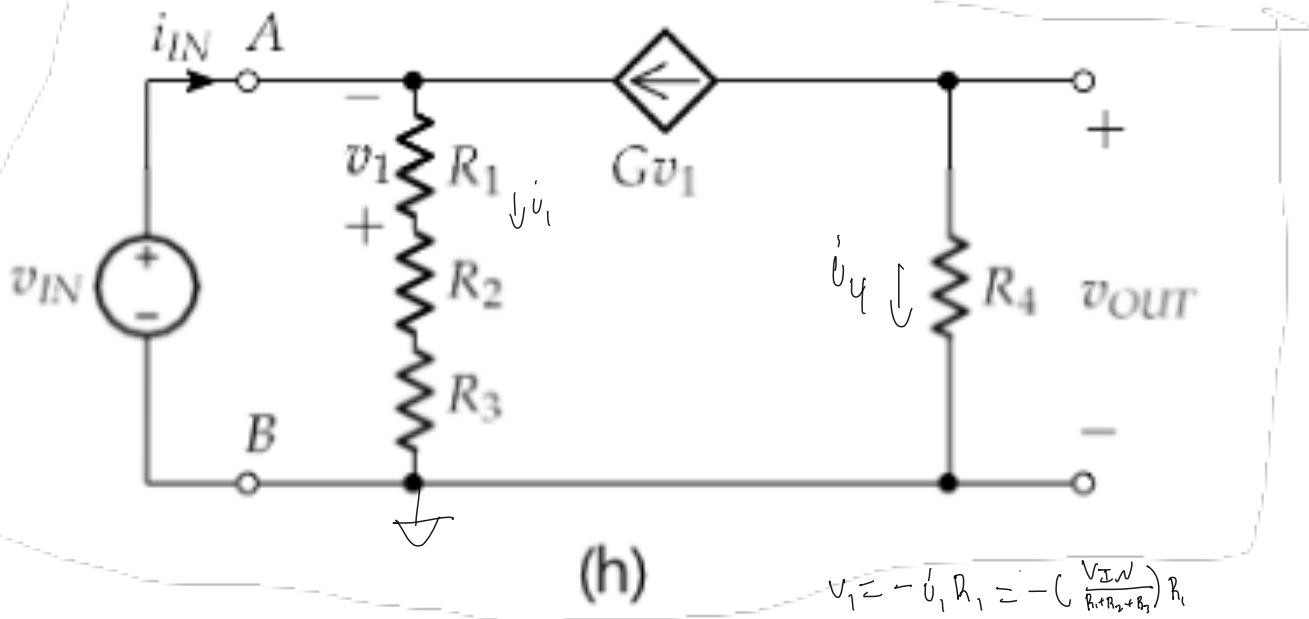

(h)

$$v_1 = -\frac{v_{IN}}{R_1} = -\left(\frac{v_{IN}}{R_1 + R_2 + R_3}\right) R_1$$

KCL @ C;  $Gv_1 + i_4 = 0$

$$G\left(-\left(\frac{v_{IN}}{R_1 + R_2 + R_3}\right) R_1\right) + \frac{v_{out}}{R_4} = 0$$

$$v_{IN} \left(-\frac{GR_1}{R_1 + R_2 + R_3}\right) = -\frac{v_{out}}{R_4}$$

$$\frac{v_{out}}{v_{IN}} = \frac{GR_1 R_4}{R_1 + R_2 + R_3} = A_v \text{ (gain)}$$

$$\text{For } R_{IN} = \frac{v_{IN}}{i_{IN}}$$

KCL @ A;  $-i_{IN} + i_1 - Gv_1 = 0$

$$\frac{v_{IN}}{R_1 + R_2 + R_3} = i_{IN} + G\left(-\left(\frac{v_{IN}}{R_1 + R_2 + R_3}\right) R_1\right)$$


$$v_{IN} \left(\frac{1}{R_1 + R_2 + R_3} + \frac{GR_1}{R_1 + R_2 + R_3}\right) = i_{IN}$$


$$i_{IN} = v_{IN} \left(\frac{1 + GR_1}{R_1 + R_2 + R_3}\right)$$

$$\text{so } R_{IN} = \frac{v_{IN}}{i_{IN} \left(\frac{1 + GR_1}{R_1 + R_2 + R_3}\right)}$$

$$R_{IN} = \frac{R_1 + R_2 + R_3}{1 + GR_1}$$

For  $R_{out}$

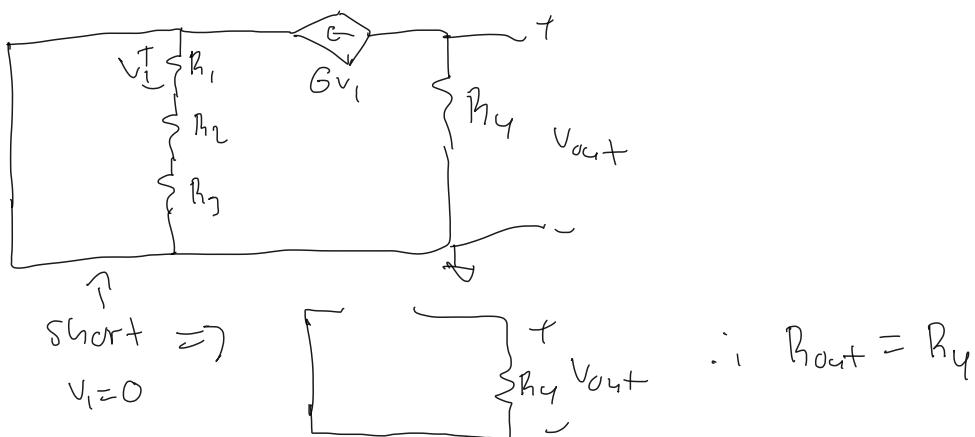

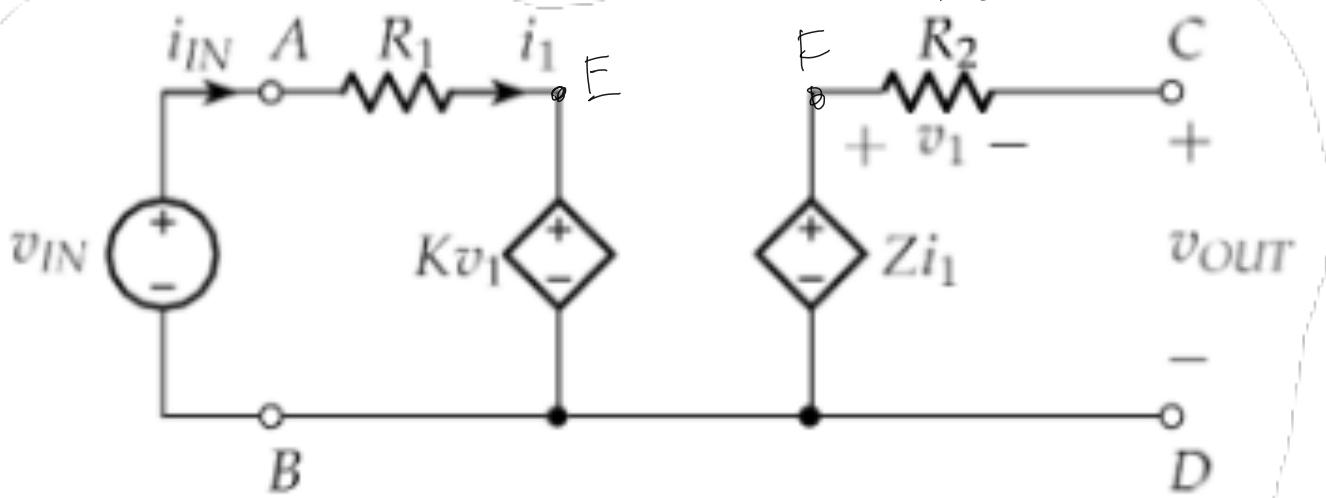

$$v_N = v_i = \frac{v_{IN} - Kv_1}{R_1}$$

$$i_1 = \frac{v_{IN} - 0}{R_1} = i_{IN}$$

(i)

$$v_1 = Z i_1 - v_{out}$$

$$i_2 = 0 = \frac{Z i_1 - v_{out}}{R_2}$$

$$Z i_1 = v_{out} \therefore v_1 = 0$$


$$Z \left( \frac{v_{IN}}{R_1} \right) = v_{out}$$

$$\frac{v_{out}}{v_{IN}} = \frac{Z}{R_1} = A_V (\text{gain})$$

$$\text{For } R_{IN} = \frac{v_{in}}{i_{in}} = \frac{v_{in}}{\frac{v_{in}}{R_1}} = R_1$$

$$R_{IN} = R_1$$
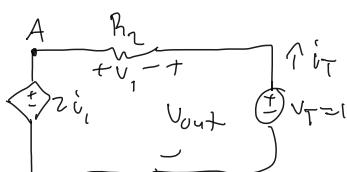
$$\text{For } R_{out} = \frac{v_T}{i_T}$$



$$\frac{v_T - V_A}{R_2} = i_T \quad i_1 = -\left( \frac{Kv_1}{R_1} \right) \quad v_1 = V_A - v_T \quad V_A = Z i_1 = -\frac{KZ}{R_1} v_1$$

$$\frac{v_T - \frac{KZ}{R_1 + KZ}}{R_2} = i_T$$

$$\frac{\frac{R_1 + KZ - KZ}{R_1 + KZ}}{R_2} = i_T$$

$$\frac{R_1}{R_2(R_1 + KZ)} = i_T$$

$$R_{out} = \frac{v_T}{i_T} = \frac{1}{R_2(R_1 + KZ)}$$

$$R_{out} = \frac{R_2(R_1 + KZ)}{R_1}$$


$$V_A = \frac{-KZ}{R_1} (V_A - v_T)$$

$$V_A \left( 1 + \frac{KZ}{R_1} \right) = V_T \frac{KZ}{R_1}$$

$$V_A = V_T \frac{\frac{KZ}{R_1}}{1 + \frac{KZ}{R_1}}$$

$$V_A = V_T \frac{KZ}{R_1 + KZ}$$

$$V_A = \frac{KZ}{R_1 + KZ}$$

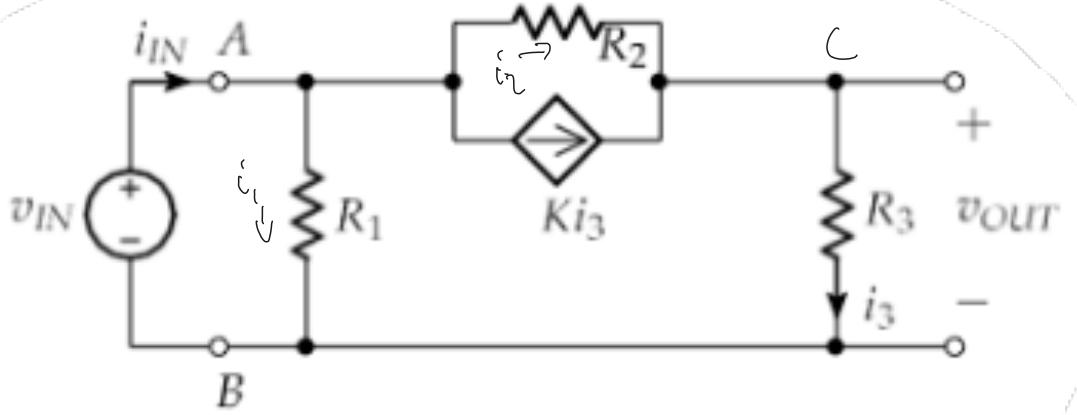

(j)

$$\text{KCL at } C: -i_2 - Ki_3 + i_3 = 0$$

$$-\left(\frac{v_{IN} - v_{out}}{R_2}\right) - K\left(\frac{v_{out}}{R_3}\right) + \frac{v_{out}}{R_3} = 0$$

$$v_{out} \left( \frac{1}{R_2} - \frac{K}{R_3} + \frac{1}{R_3} \right) + v_{IN} \left( -\frac{1}{R_2} \right) = 0$$

$$v_{out} \left( \frac{1}{R_2} + \frac{1-K}{R_3} \right) = v_{IN} \cdot \frac{1}{R_2}$$

$$\frac{v_{out}}{v_{IN}} = \frac{1}{R_2} \cdot \frac{1}{\frac{1}{R_2} + \frac{1-K}{R_3}}$$

$$= \frac{1}{1 + \frac{R_2(1-K)}{R_3}}$$

$$= \frac{R_3}{R_3 + R_2(1-K)} = A_v \text{ (gain)}$$

$$\text{For } R_{IN} = \frac{v_{IN}}{i_{IN}}$$

$$\text{from KCL at } C: \frac{v_{out}}{R_3} = \frac{v_{IN} - v_{out}}{R_2} + K\left(\frac{v_{out}}{R_3}\right)$$

$$v_{out} = A_v v_{IN}$$

$$\frac{A_v v_{IN}}{R_3} = \frac{v_{IN} - A_v v_{IN}}{R_2} + A_v v_{IN} \frac{K}{R_3}$$

$$\frac{A_v}{R_3} = \frac{1 - A_v}{R_2} + A_v \frac{K}{R_3}$$

$$\frac{1 - A_v}{R_2} = A_v \left( \frac{1 - K}{R_3} \right)$$

$$A_v \left( \frac{1}{R_2} + \frac{1-K}{R_3} \right) = \frac{1}{R_2}$$

$$A_v \left( \frac{R_3 + R_2(1-K)}{R_2 R_3} \right) = \frac{1}{R_2}$$

$$A_v = \left( \frac{R_3}{R_2 + R_2(1-K)} \right)$$

$$\text{KCL at } A: -i_{IN} + i_1 + i_2 + K i_3 = 0$$

$$i_{IN} = \frac{v_{IN}}{R_1} + \frac{v_{IN} - v_{out}}{R_2} + K \left( \frac{v_{out}}{R_3} \right)$$

$$i_{IN} = \frac{v_{IN}}{R_1} + \frac{v_{IN} - A_v v_{IN}}{R_2} + K \frac{A_v v_{IN}}{R_3}$$

$$i_{IN} = v_{IN} \left( \frac{1}{R_1} + \frac{1 - A_v}{R_2} + \frac{KA_v}{R_3} \right)$$

$$i_{IN} = v_{IN} \left( \frac{1}{R_1} + \frac{A_v(1-K) + KA_v}{R_2 R_3} \right)$$


$$i_{IN} = v_{IN} \left( \frac{1}{R_1} + \frac{A_v}{R_2 R_3} \right)$$

$$i_{IN} = v_{IN} \left( \frac{1}{R_1} + \frac{R_3}{R_2(R_3 + R_2(1-K))} \right)$$

$$i_{IN} = v_{IN} \left( \frac{1}{R_1} + \frac{1}{R_2 + R_2(1-K)} \right)$$

$$\frac{v_{IN}}{i_{IN}} = R_{IN} = \frac{1}{\left( \frac{1}{R_1} + \frac{1}{R_2 + R_2(1-K)} \right)}$$

For  $R_{out}$

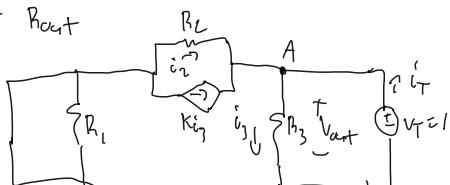

$$\text{KCL at } A: -i_T + i_3 - K i_3 - i_2 = 0$$

$$i_T = i_3(1-K) - i_2$$

$$i_T = \frac{v_T}{R_3}(1-K) - \frac{v_T}{R_2}$$

$$i_T = \frac{1-K}{R_3} + \frac{1}{R_2} = \frac{R_2(1-K) + R_3}{R_2 R_3}$$

$$R_{out} = \frac{v_T}{i_T} = \frac{1}{\frac{R_2(1-K) + R_3}{R_2 R_3}}$$

$$R_{out} = \frac{R_2 R_3}{R_2(1-K) + R_3}$$