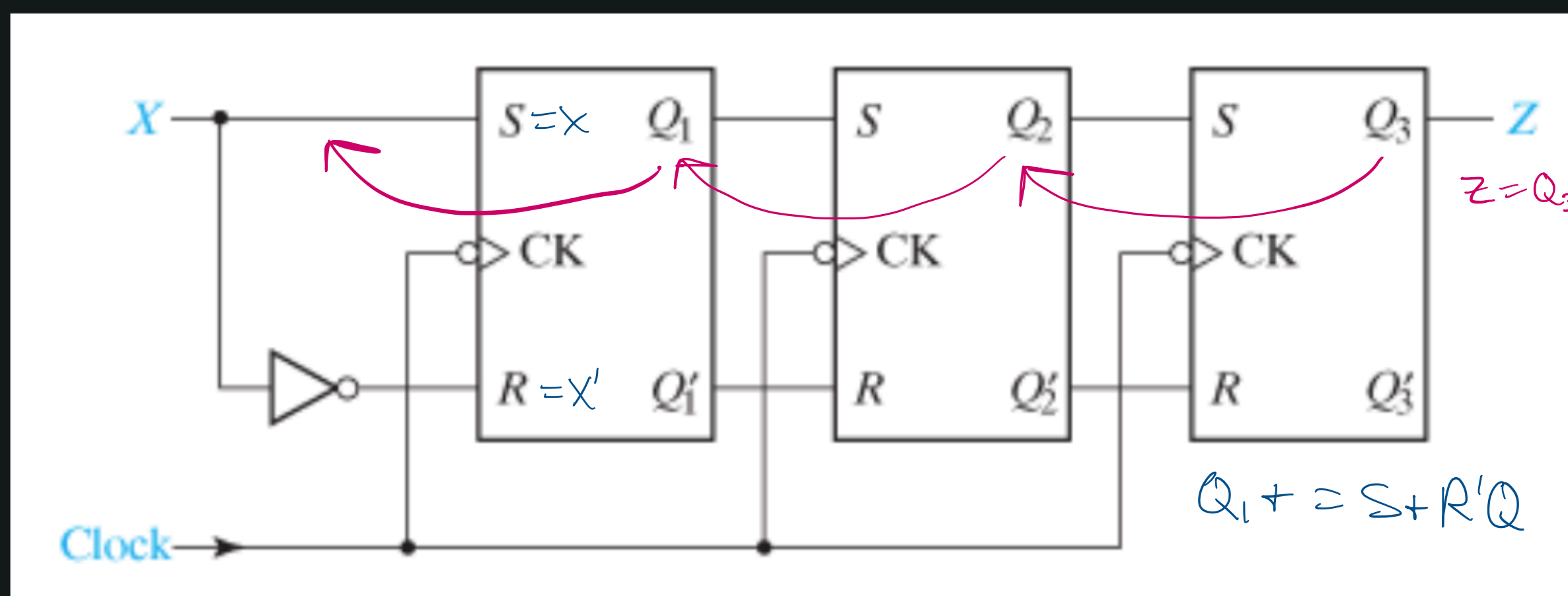


13.2 Construct a transition graph for the **shift register** shown. (X is the input, and Z is the output.) Is this a Mealy or Moore machine?



Moore machine;
 Z does not depend on current value of X

Transition table, then graph

Q_1	Q_2	Q_3	$X=0$	$X=1$	Z
0	0	0	000	100	0
0	0	1	000	100	1
0	1	0	001	101	0
0	1	1	001	101	1
1	0	0	010	110	0
1	0	1	010	110	1
1	1	0	011	111	0
1	1	1	011	111	1

$$Z = Q_3$$

Moore: output inside circle

$X = 0, 1$

Input
Output

