

11.6 a) Find I_o in the circuit in Fig. P11.6.


PSPICE
MULTISIM

b) Find V_{AN} .

c) Find V_{AB} .

d) Is the circuit a balanced or unbalanced three-phase system?

Figure P11.6

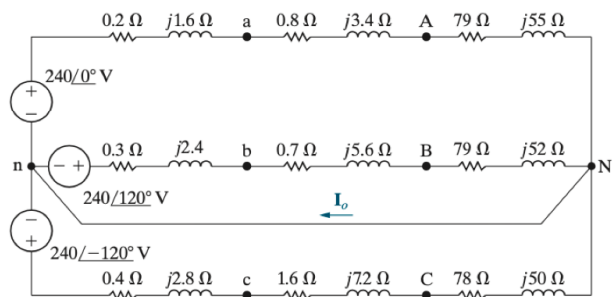

11.10 The phase voltage at the terminals of a balanced three-phase Y-connected load is 2400 V. The load has an impedance of $16 + j12 \, \Omega/\phi$ and is fed from a line having an impedance of $0.10 + j0.80 \, \Omega/\phi$. The Y-connected source at the sending end of the line has a phase sequence of acb and an internal impedance of $0.02 + j0.16 \, \Omega/\phi$. Use the a-phase voltage at the load as the reference and calculate (a) the line currents $\mathbf{I}_{aA}$, $\mathbf{I}_{bB}$, and $\mathbf{I}_{cC}$; (b) the line voltages at the source, $\mathbf{V}_{ab}$, $\mathbf{V}_{bc}$ and $\mathbf{V}_{ca}$; and (c) the internal phase-to-neutral voltages at the source, $\mathbf{V}_{a'n}$, $\mathbf{V}_{b'n}$, and $\mathbf{V}_{c'n}$.

11.15 A balanced Y-connected load having an impedance of $96 - j28 \, \Omega/\phi$ is connected in parallel with a balanced Δ -connected load having an impedance of $144 + j42 \, \Omega/\phi$. The parallel loads are fed from a line having an impedance of $j1.5 \, \Omega/\phi$. The magnitude of the phase voltage of the Y-load is 7500 V.

- a) Calculate the magnitude of the phase current in the Y-connected load.
- b) Calculate the magnitude of the phase current in the Δ -connected load.
- c) Calculate the magnitude of the current in the line feeding the loads.
- d) Calculate the magnitude of the line voltage at the sending end of the line.

11.19 A three-phase Δ -connected generator has an internal impedance of $0.6 + j4.8 \, \Omega/\phi$. When the load is removed from the generator, the magnitude of the terminal voltage is 34,500 V. The generator feeds a Δ -connected load through a transmission line with an impedance of $0.8 + j6.4 \, \Omega/\phi$. The per-phase impedance of the load is $2877 - j864 \, \Omega$.

- a) Construct a single-phase equivalent circuit.
- b) Calculate the magnitude of the line current.
- c) Calculate the magnitude of the line voltage at the terminals of the load.
- d) Calculate the magnitude of the line voltage at the terminals of the source.
- e) Calculate the magnitude of the phase current in the load.
- f) Calculate the magnitude of the phase current in the source.

11.24 In a balanced three-phase system, the source has an abc sequence, is Y-connected, and $\mathbf{V}_{an} = 250 \angle -60^\circ$ V. The source feeds two loads, both of which are Y-connected. The impedance of load 1 is $15 + j20 \ \Omega/\phi$. The complex power for the a-phase of load 2 is $500 \angle 45^\circ$ VA. Find the total complex power supplied by the source.

11.26 A three-phase positive sequence Y-connected source supplies 24 kVA with a power factor of 0.6 lagging to a parallel combination of a Y-connected load and a Δ -connected load. The Y-connected load uses 12 kVA at a power factor of 0.8 lagging and has an a-phase current of $40\angle 60^\circ$ A.

- a) Find the complex power per phase of the Δ -connected load.
- b) Find the magnitude of the line voltage.