

Name: Solutions (please print)

Signature: _____

ECE 2202 – Quiz 2

February 18, 2025 ⁶

1. Show all work necessary to complete the problem. Use additional sheets of paper as needed.
2. Show all units in solutions and figures. Units in the quiz will be included between square brackets.
3. You will have 40 minutes to work on the quiz.
4. Write your ID number on every page that you show your work.

_____/20

Problem 1/1 (20 pts)

A Device can be modeled as an independent current source in parallel with a resistance. The Device is shown in Figure 1. The relationship between the voltage and current for the Device is given in the plot in Figure 2. Two identical versions of this Device are inserted in the circuit shown in Figure 3. The polarities of the Devices are indicated with the terminal labels 1 and 2.

- Find a Norton equivalent circuit model for the Device. Draw the model, labeling the components with numerical values.
- Find the Thevenin equivalent of the circuit in Figure 3 as seen by the dependent voltage source. Draw the Thevenin equivalent circuit with clear labels.


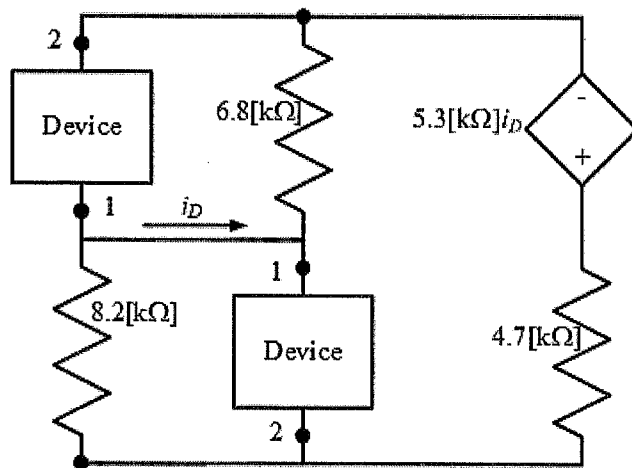
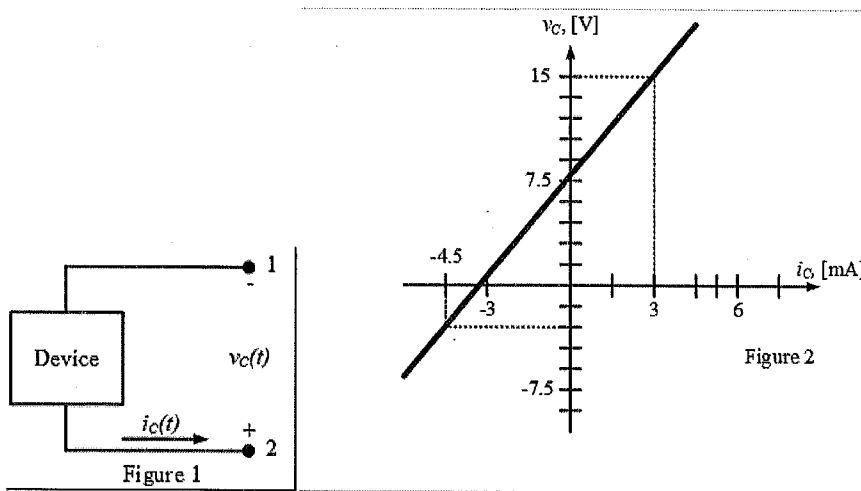


Figure 3

ID number: _____

Room for extra work

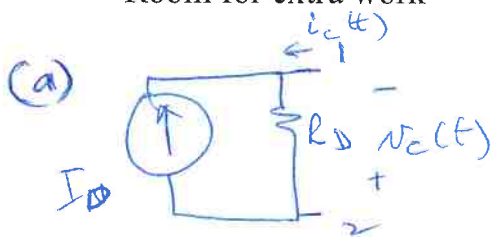

KCL at Node 1

$$-I_D + \frac{v_c}{R_D} = i_c$$

① $(-4.5 \text{ [mA]}, -3 \text{ [V]})$

$$-I_D + \frac{3 \text{ [V]}}{R_D} = -4.5 \text{ [mA]}$$

② $(3 \text{ [mA]}, 15 \text{ [V]})$


$$-I_D - \frac{15 \text{ [V]}}{R_D} = 3 \text{ [mA]}$$

Solve:


$$\frac{3}{R_D} + 0.0045 = \frac{-15}{R_D} - 0.003 = I_D$$

$$\frac{3 + 15}{R_D} = -0.0075$$


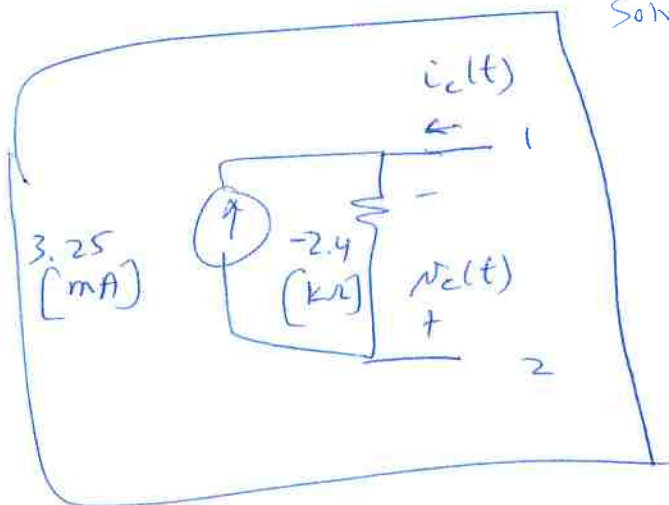
$$\begin{aligned} R_D &= -2.4 \text{ [k}\Omega\text{]} \\ I_D &= 3.25 \text{ [mA]} \end{aligned}$$



(b)

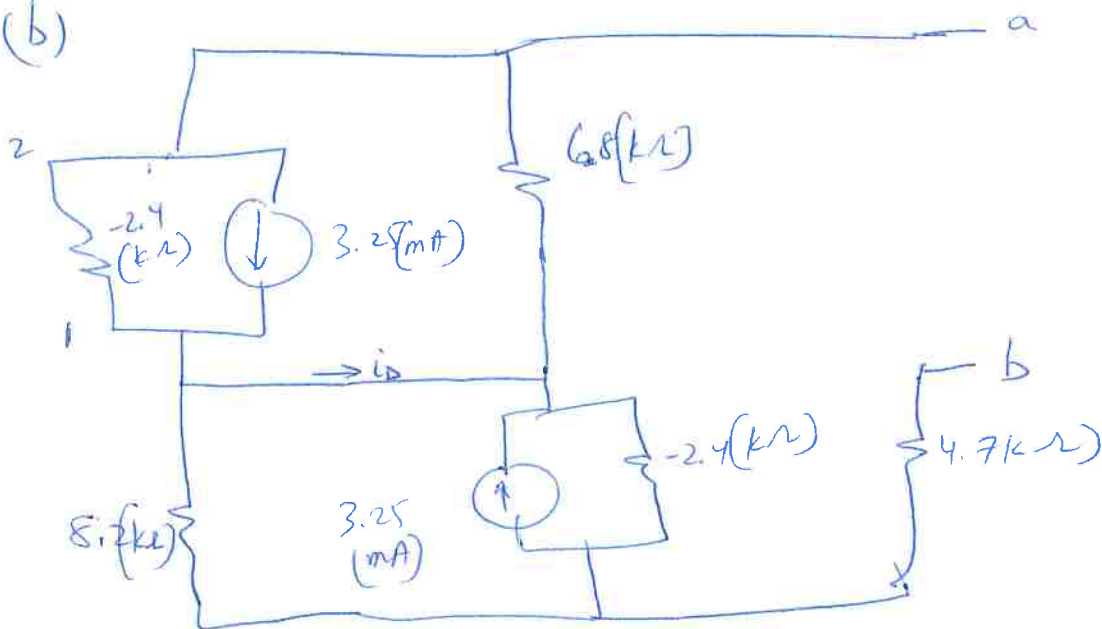


Req:

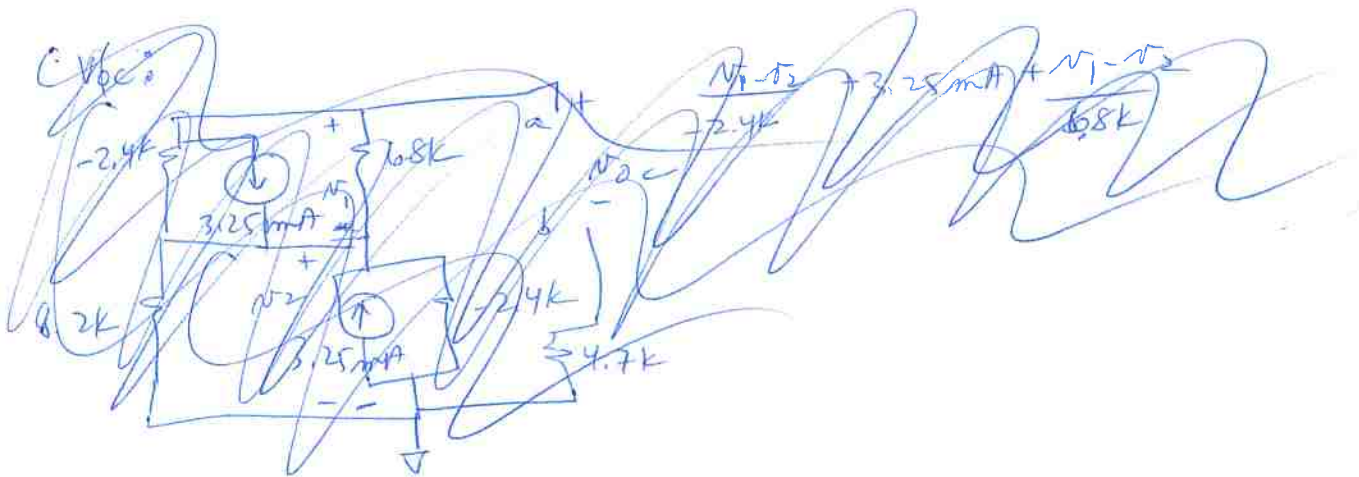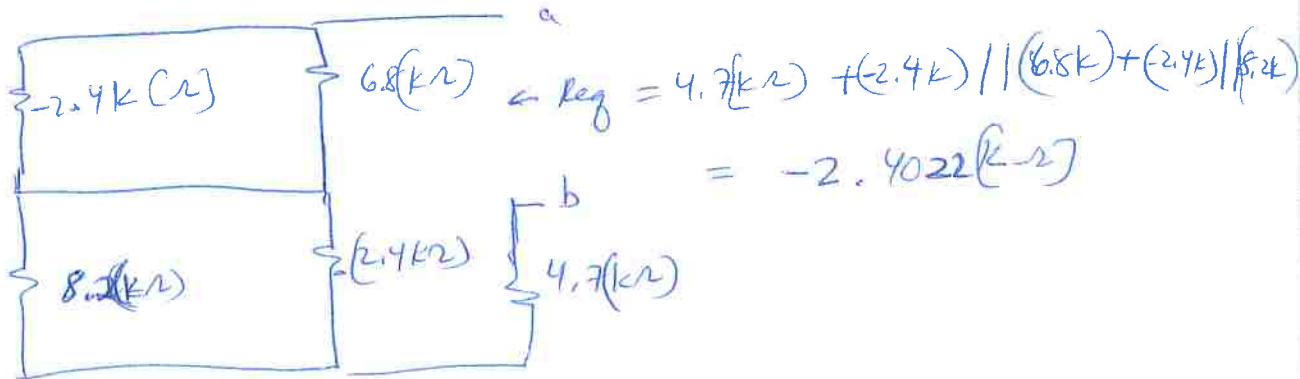


ID number: _____



V_{oc} :

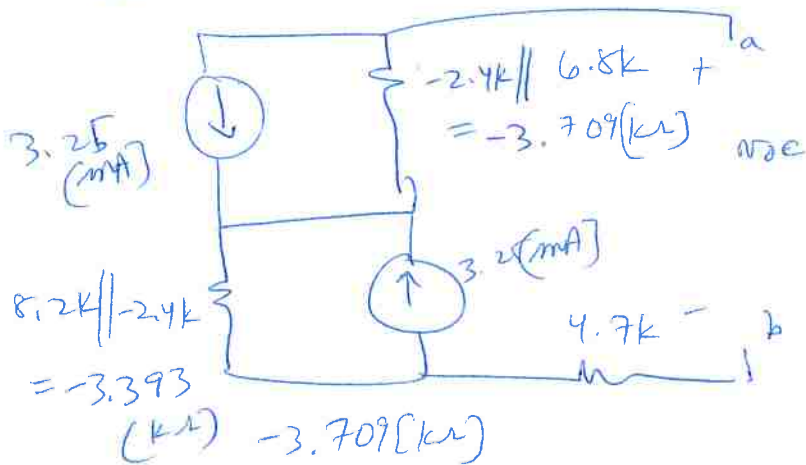

Source transformation $\rightarrow$

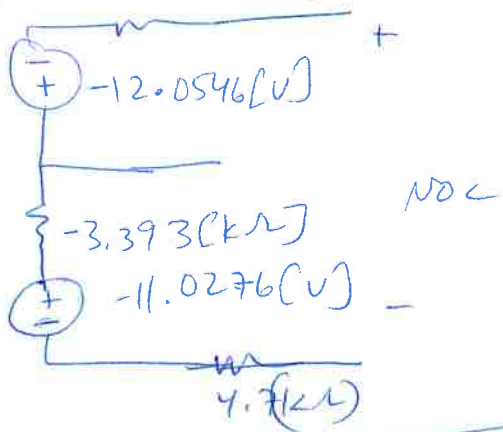

=

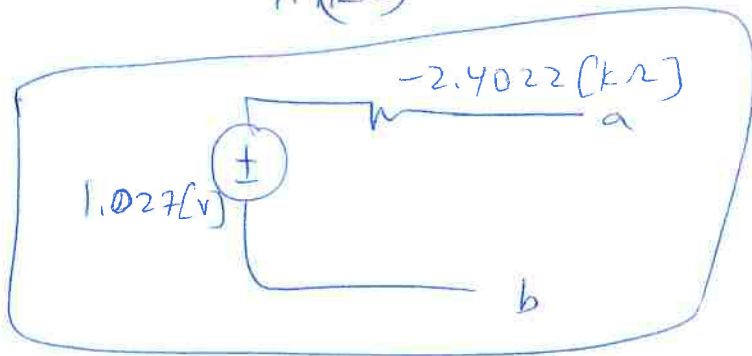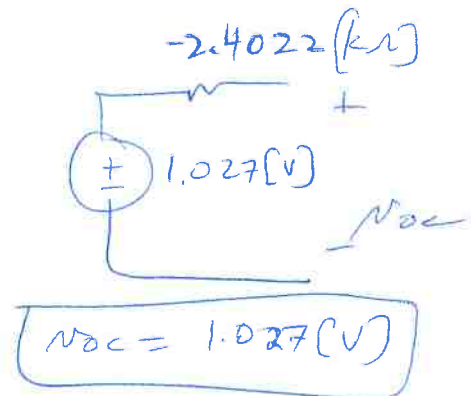

ID number: _____

$$i = \frac{dq}{dt} \quad v = \frac{dw}{dq} \quad p = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} = iv$$

$$i = C \frac{dv}{dt} \quad v = L \frac{di}{dt}$$

$$v = iR \quad R_1 || R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

$$p = Cv \frac{dv}{dt} \quad p = Li \frac{di}{dt}$$

$$p = iv = i^2 R = \frac{v^2}{R}$$


$$w = \frac{1}{2} Li^2 \quad w = \frac{1}{2} Cv^2$$

$$R = \frac{v}{i}$$

$$v_C(t) = v_C(\infty) + [v_C(T_0) - v_C(\infty)] e^{-(t-T_0)/\tau}$$

$$i_L(t) = i_L(\infty) + [i_L(T_0) - i_L(\infty)] e^{-(t-T_0)/\tau}$$


(Switch action at $t = T_0$)

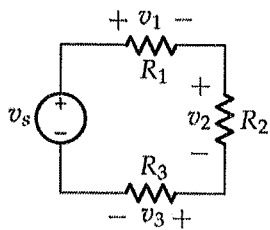

$$v_1 = \frac{R_1}{R_1 + R_2 + R_3} v_s$$

$$v_2 = \frac{R_2}{R_1 + R_2 + R_3} v_s$$
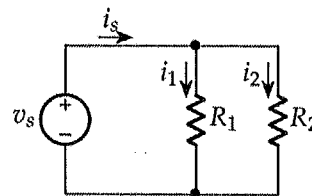
$$v_3 = \frac{R_3}{R_1 + R_2 + R_3} v_s$$






$$i_1 = \frac{R_2}{R_1 + R_2} i_s$$

$$i_2 = \frac{R_1}{R_1 + R_2} i_s$$

$$v_B = \underbrace{V_B}_{\text{DC}} + \underbrace{v_b}_{\text{AC}}$$

$\bar{V}_b \rightarrow$ Phasor notation

$$\text{CMRR} = 20 \log_{10} \frac{|A_d|}{|A_{cm}|}$$

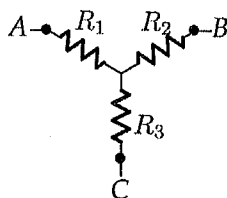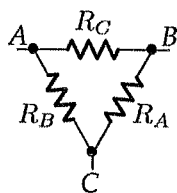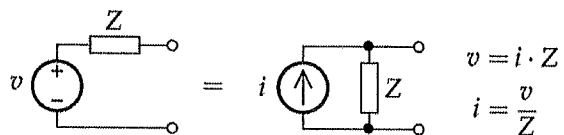

$$R_1 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_A R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

