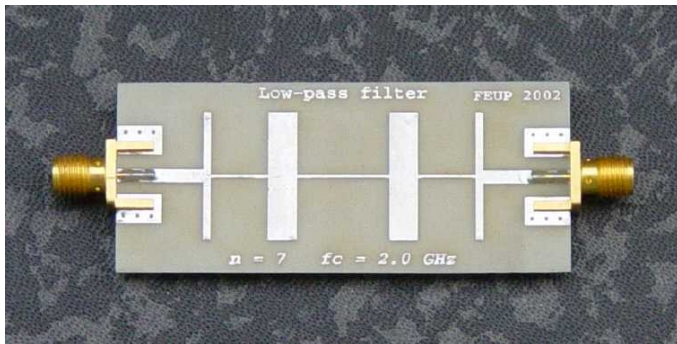


ECE 3317

Dr. Jiefu Chen

Notes 10


Transmission Lines (Reflection and Impedance)



Adapted from notes by Prof. Stuart A. Long

Reflection

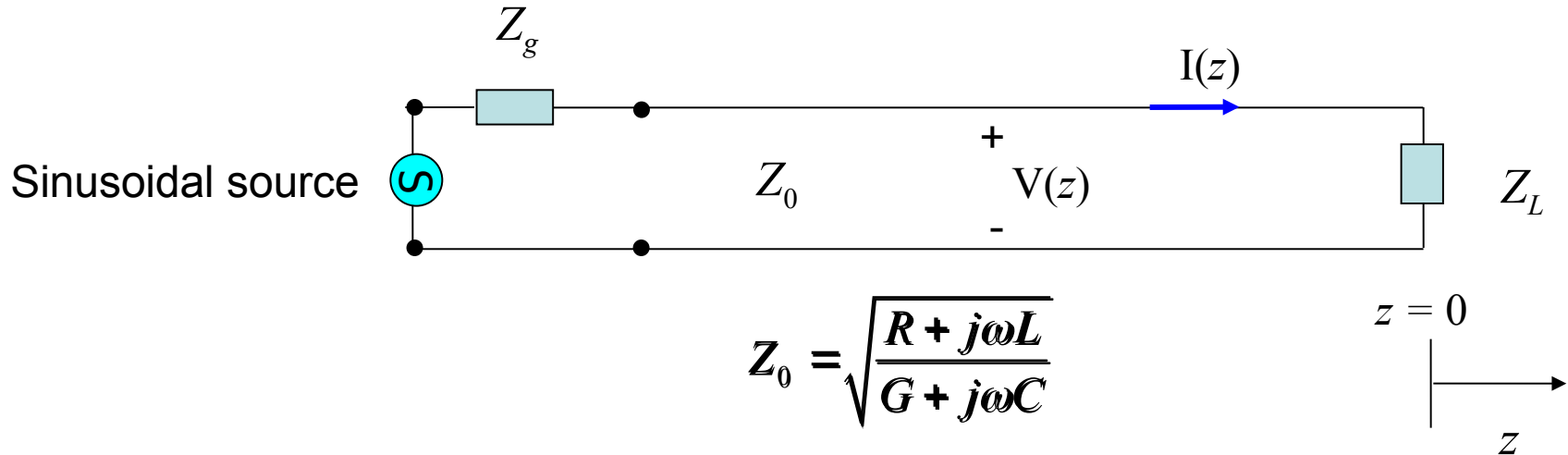Consider a transmission line that is terminated with a load:



$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Voltage and current on the line:


$$V(z) = \underbrace{Ae^{-\gamma z}}_{V^+(z)} + \underbrace{Be^{+\gamma z}}_{V^-(z)}$$

$$I(z) = \underbrace{\left(\frac{A}{Z_0}\right)e^{-\gamma z}}_{I^+(z)} - \underbrace{\left(\frac{B}{Z_0}\right)e^{+\gamma z}}_{I^-(z)}$$

A = amplitude of **net** forward-traveling wave
 B = amplitude of **net** backward-traveling wave

(sinusoidal steady-state)

Reflection (cont.)

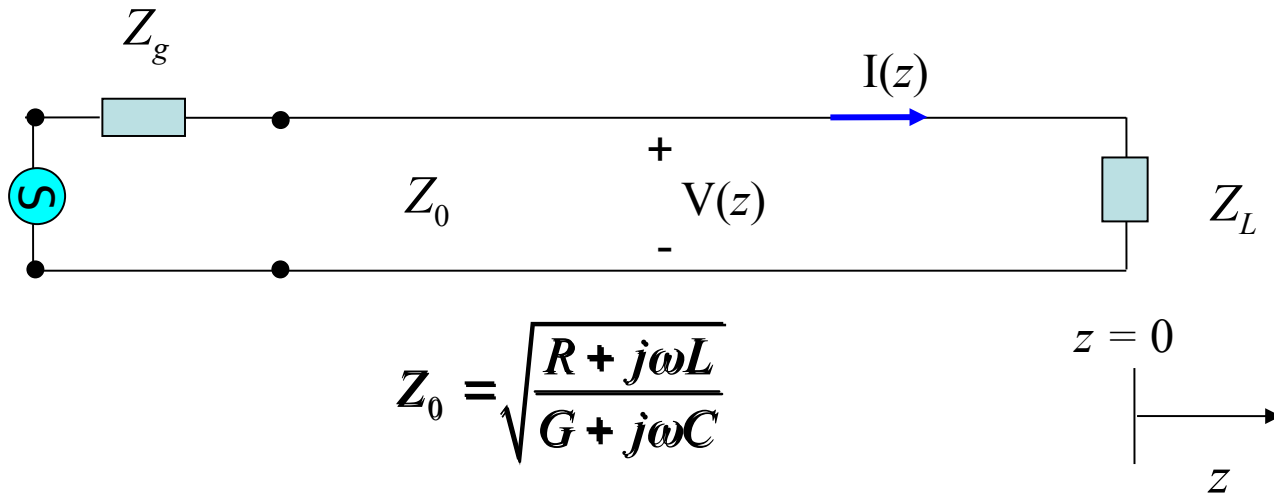

At the load ($z = 0$): $V(0) = Z_L I(0)$

Hence we have $A + B = \frac{Z_L}{Z_0} (A - B)$

or $B \left(1 + \frac{Z_L}{Z_0} \right) = A \left(\frac{Z_L}{Z_0} - 1 \right)$

Reflection Coefficient

We define the load reflection coefficient:

$$\Gamma_L \equiv \frac{V^-(0)}{V^+(0)}$$

Hence $\Gamma_L = \frac{B}{A}$

$$V(z) = Ae^{-\gamma z} + Be^{+\gamma z}$$

$$V^+(z) = Ae^{-\gamma z}$$

$$V^-(z) = Be^{+\gamma z}$$

We then have
$$\Gamma_L = \frac{\left(\frac{Z_L}{Z_0} - 1\right)}{\left(1 + \frac{Z_L}{Z_0}\right)}$$

or

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Voltage and Current

We can then write


$$V(z) = A(e^{-\gamma z} + \Gamma_L e^{+\gamma z})$$

$$I(z) = \frac{1}{Z_0} A(e^{-\gamma z} - \Gamma_L e^{+\gamma z})$$

Note: The generator (source) will determine the unknown (complex) constant A .

Impedance

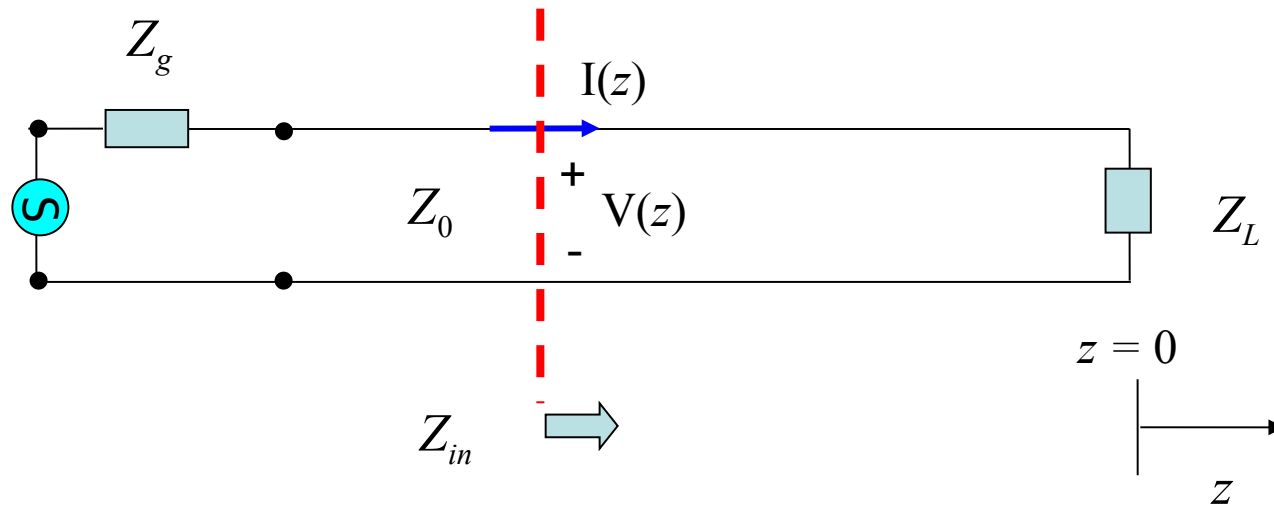We define the **input impedance** at any point on the line



$$Z_{in}(z) = \frac{V(z)}{I(z)}$$

Impedance (cont.)

We then have

$$Z_{in}(z) = \frac{A(e^{-\gamma z} + \Gamma_L e^{+\gamma z})}{\frac{1}{Z_0} A(e^{-\gamma z} - \Gamma_L e^{+\gamma z})}$$

Canceling the constant A , we have

$$Z_{in}(z) = Z_0 \left(\frac{e^{-\gamma z} + \Gamma_L e^{+\gamma z}}{e^{-\gamma z} - \Gamma_L e^{+\gamma z}} \right)$$

or

$$Z_{in}(z) = Z_0 \left(\frac{1 + \Gamma_L e^{+2\gamma z}}{1 - \Gamma_L e^{+2\gamma z}} \right)$$

Impedance (cont.)


$$\begin{aligned}
 Z_{in}(z) &= Z_0 \left(\frac{e^{-\gamma z} + \Gamma_L e^{+\gamma z}}{e^{-\gamma z} - \Gamma_L e^{+\gamma z}} \right) = Z_0 \left(\frac{e^{-\gamma z} + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{+\gamma z}}{e^{-\gamma z} - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{+\gamma z}} \right) \\
 &= Z_0 \left(\frac{(Z_L + Z_0)e^{-\gamma z} + (Z_L - Z_0)e^{+\gamma z}}{(Z_L + Z_0)e^{-\gamma z} - (Z_L - Z_0)e^{+\gamma z}} \right) \\
 &= Z_0 \left(\frac{Z_L (e^{+\gamma z} + e^{-\gamma z}) - Z_0 (e^{+\gamma z} - e^{-\gamma z})}{-Z_L (e^{+\gamma z} - e^{-\gamma z}) + Z_0 (e^{+\gamma z} + e^{-\gamma z})} \right) \\
 &= Z_0 \left(\frac{Z_L (2 \cosh(\gamma z)) - Z_0 (2 \sinh(\gamma z))}{-Z_L (2 \sinh(\gamma z)) + Z_0 (2 \cosh(\gamma z))} \right) \\
 &= Z_0 \left(\frac{Z_L - Z_0 \tanh(\gamma z)}{Z_0 - Z_L \tanh(\gamma z)} \right)
 \end{aligned}$$

Now let $z = -l$ $\tanh(\gamma z) = \tanh(-\gamma l) = -\tanh(\gamma l)$

Impedance (cont.)

We then have
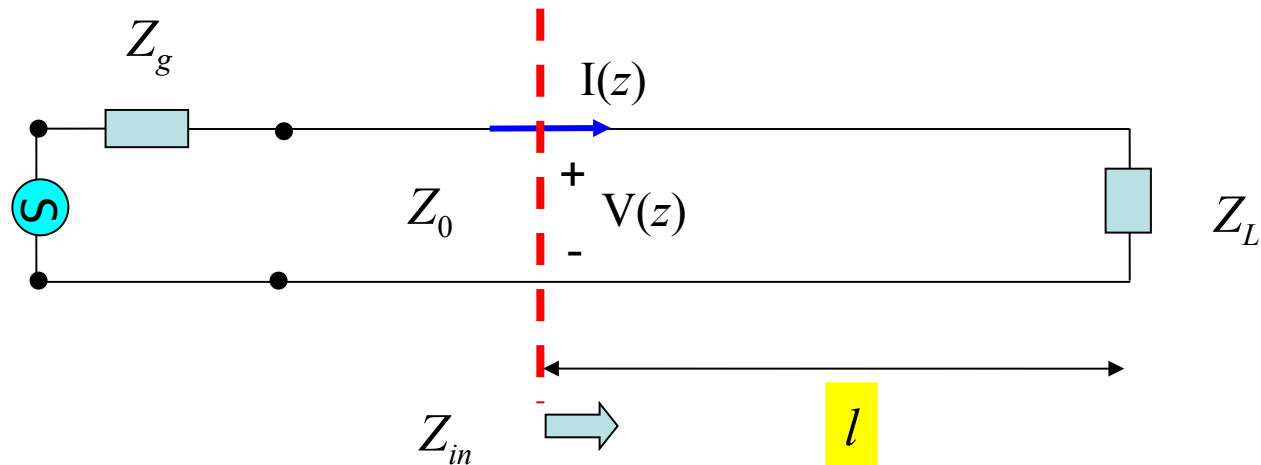
$$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)} \right)$$



Impedance (cont.)

Limiting cases

1) no transmission line:

$$l = 0 \rightarrow \tanh(\gamma l) = 0$$

$$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)} \right) = Z_L$$

2) infinitely long transmission line:

$$l \rightarrow \infty \rightarrow \tanh(\gamma l) \rightarrow 1$$

$$Z_{in} = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)} \right) = Z_0$$

Impedance (cont.)

Lossless Case

$$\gamma = \alpha + j\beta = \sqrt{\cancel{(R + j\omega L)}\cancel{(G + j\omega C)}} = j\omega\sqrt{LC}$$


Use $\tanh(jx) = j \tan(x)$

We then have
$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right)$$

where
$$\beta = \omega\sqrt{LC} = \omega\sqrt{\mu\epsilon} = \frac{2\pi}{\lambda} \quad \lambda = \frac{\lambda_0}{\sqrt{\epsilon_r}}$$

Impedance (cont.)

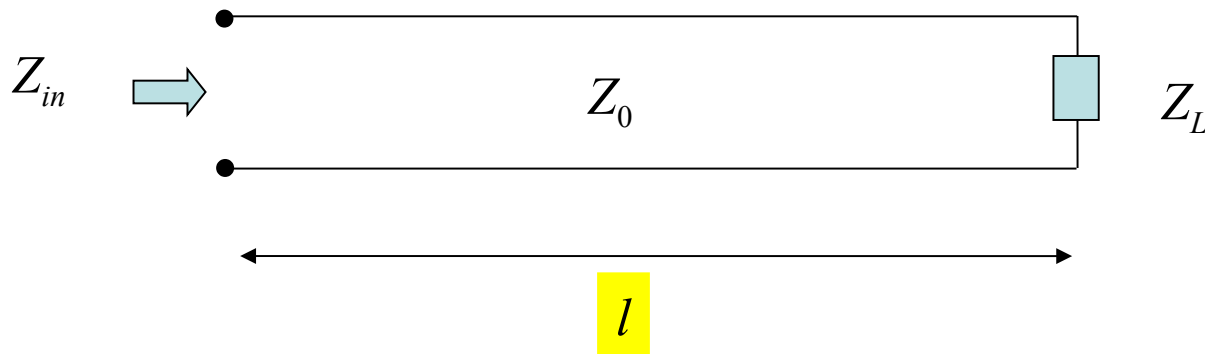Summary of final formula for a **lossless line**




$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right)$$

$$\beta = \omega \sqrt{LC} = \omega \sqrt{\mu \epsilon} = \frac{2\pi}{\lambda}$$

$$\lambda = \lambda_0 / \sqrt{\epsilon_r}$$

Impedance (cont.)

Special Cases of Lossless Line

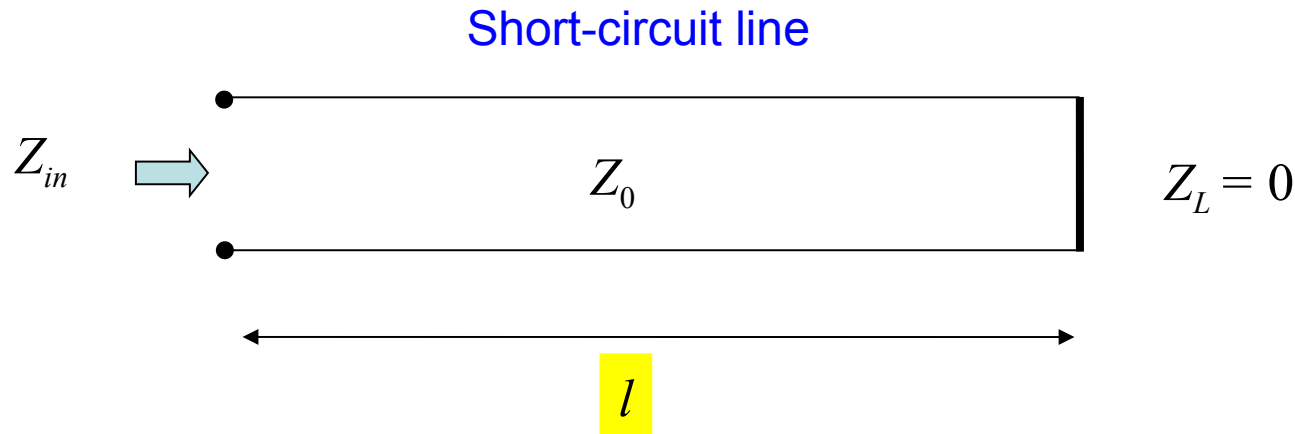

$$Z_{in} = Z_0 \left(\frac{\cancel{Z_L} + jZ_0 \tan(\beta l)}{Z_0 + j\cancel{Z_L} \tan(\beta l)} \right)$$

$$Z_{in} = jZ_0 \tan(\beta l)$$

$$\text{or } Z_{in} = jZ_0 \tan(2\pi l / \lambda)$$



Impedance (cont.)

Short-circuit line

$$X_{in} = Z_0 \tan(\beta l)$$


or

$$X_{in} = Z_0 \tan(2\pi l / \lambda)$$

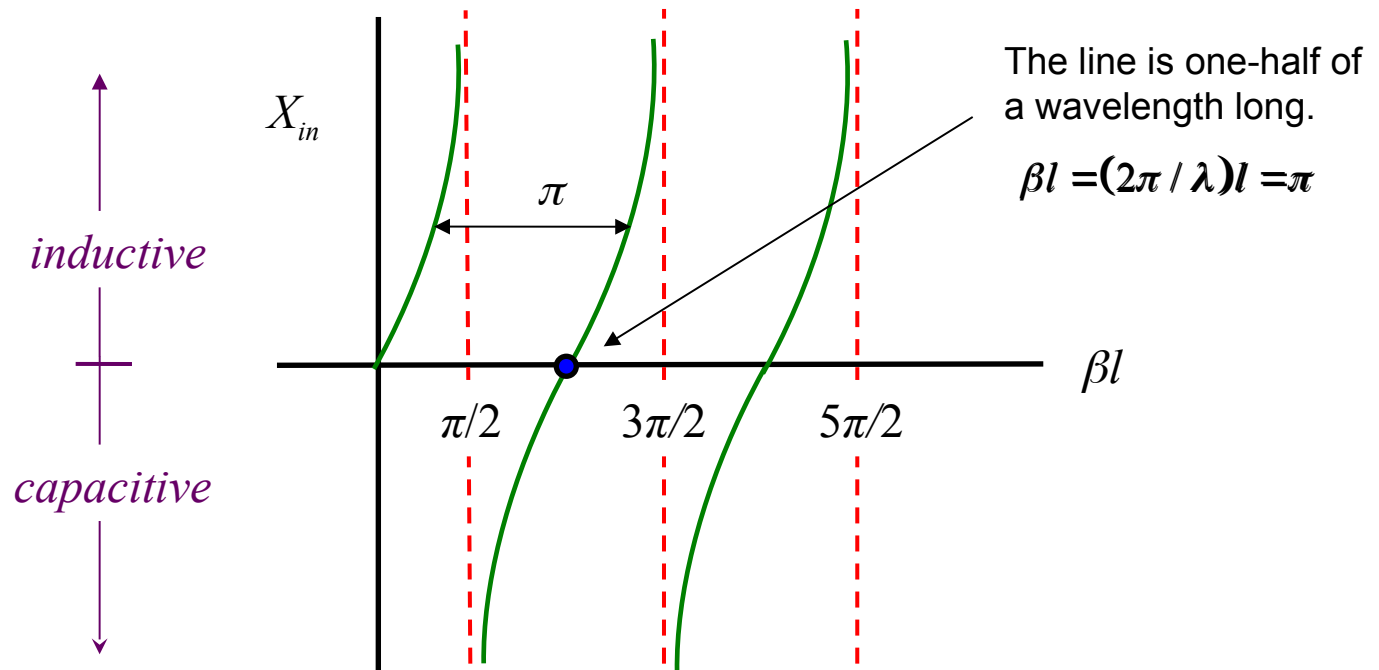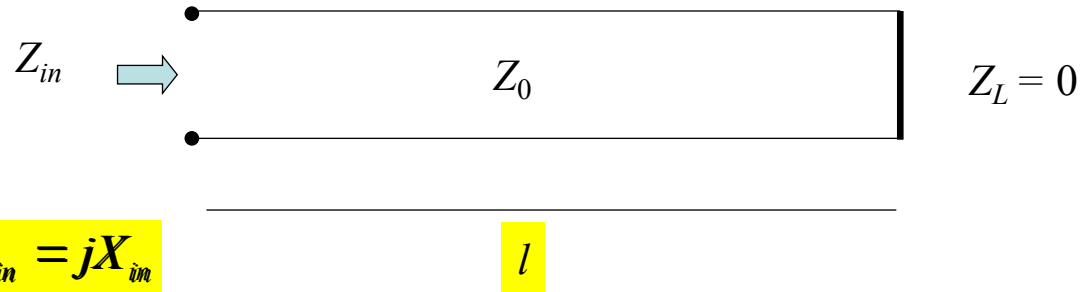

Impedance (cont.)

Special cases of Lossless Line (cont.)

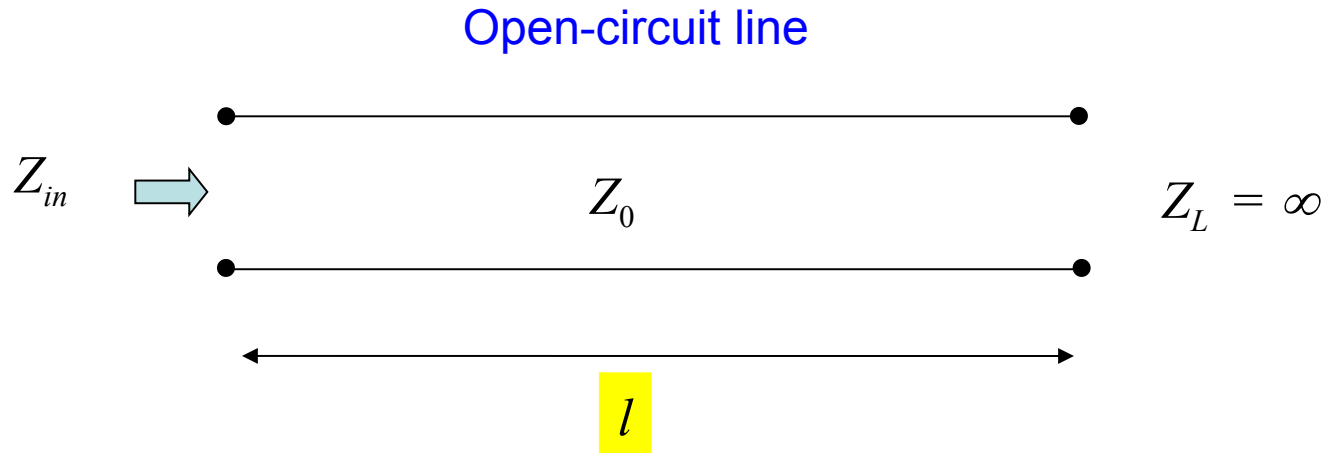

$$Z_{in} = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)} \right) \rightarrow Z_{in} = Z_0 \left(\frac{1 + j(Z_0 / Z_L) \tan(\beta l)}{(Z_0 / Z_L) + j \tan(\beta l)} \right)$$

$$Z_{in} = -jZ_0 \cot(\beta l)$$

or

$$Z_{in} = -jZ_0 \cot(2\pi l / \lambda)$$


Impedance (cont.)

Open-circuit line


$$X_{in} = -Z_0 \cot(\beta l)$$

or

$$X_{in} = -Z_0 \cot(2\pi l / \lambda)$$

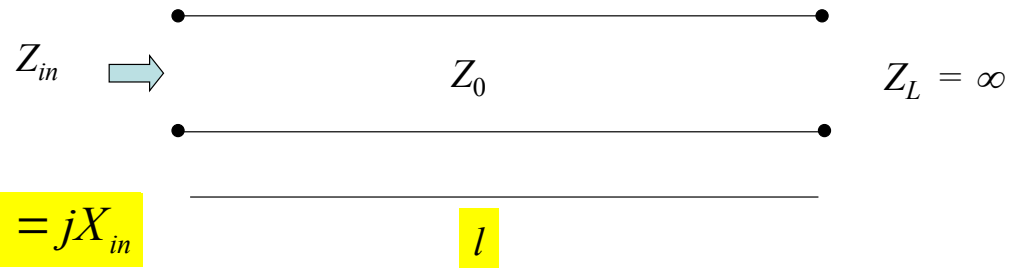

$$Z_{in} = jX_{in}$$

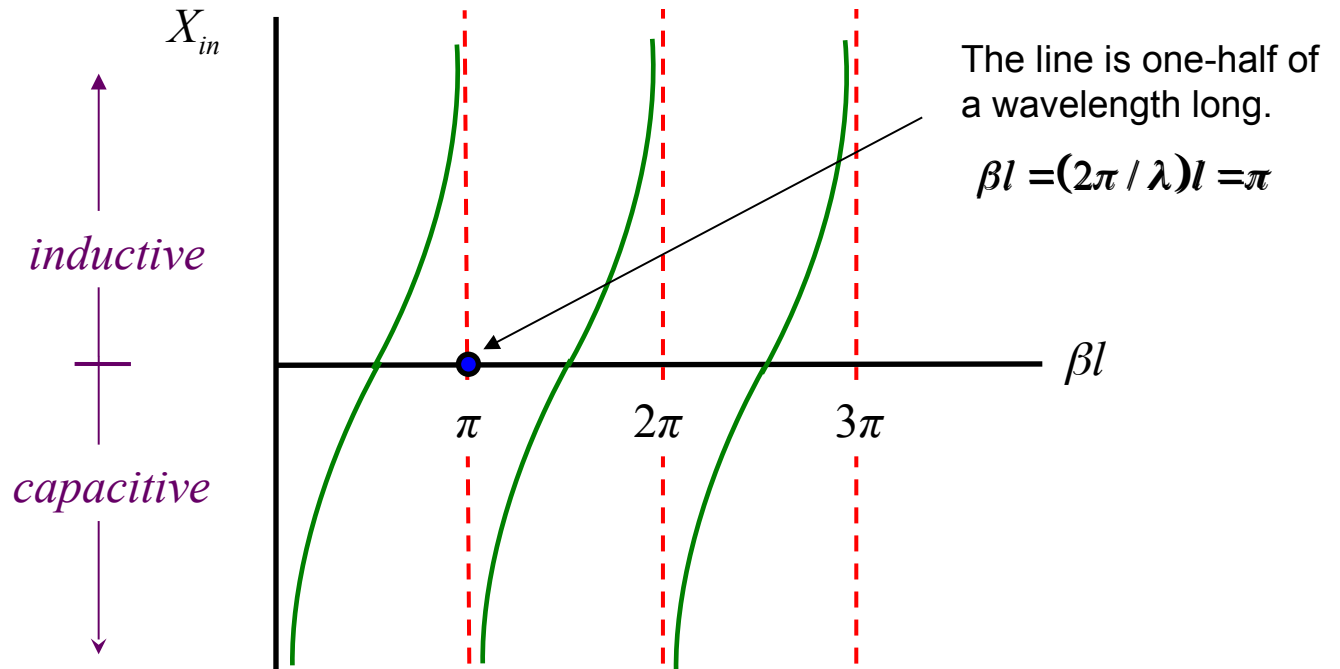

Filter Application

Microstrip filter (application of open-circuited “stubs”)

