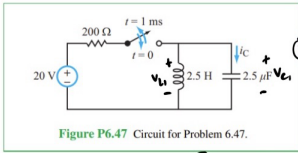


*6.47 After closing the switch in the circuit of Fig. P6.47 at $t = 0$, it was reopened at $t = 1$ ms. Determine $i_C(t)$ and plot its waveform for $t \geq 0$. Assume no energy was stored in either L or C prior to $t = 0$.



Quiz 5:
grading
rubric

3) $0 < t < 1$ [ms]

4) source transformation

$$\frac{0 \text{ [V]}}{200 \text{ [}\Omega\text{]}} = 0.1 \text{ [A]}$$



5) damping parameters:

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 200 \times 2.5 \times 10^{-6}} = 1000 \text{ [s}^{-1}\text{]}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2.5 \times 2.5 \times 10^{-6}}} = 400 \text{ [rad/s]}$$

$\alpha > \omega_0 \Rightarrow$ overdamped
go to table 6-2

+2 parameters

6) get general solution: $i_{L1}(t) = i_{L1}(\infty) + A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -93 \text{ [s}^{-1}\text{]}, \quad i_{L1}(\infty) = 0.1 \text{ [A]}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -1917 \text{ [s}^{-1}\text{]}$$

$$A_1 = \frac{i'_{L1}(0) - s_2 [i_{L1}(0) - i_{L1}(\infty)]}{s_1 - s_2} = -0.1045 \text{ [A]}$$

$$A_2 = \frac{i'_{L1}(0) - s_1 [i_{L1}(0) - i_{L1}(\infty)]}{s_1 - s_2} = 0.0045 \text{ [A]}$$

+4 for s_1, s_2, A_1, A_2

7) $i_{L1}(t) = [0.1 - 0.1045 e^{-93t} + 0.0045 e^{-1917t}] \text{ [A]}$

8) $i_{C1}(t) = LC i''_{L1}(t) \leftarrow \left[I = C \frac{dv}{dt}, v_L = L \frac{di_L}{dt} \right] \rightarrow I = C \frac{d}{dt} \left(L \frac{di_L}{dt} \right)$


$$i_{C1}(t) = 25 \text{ [H]} \cdot 2.5 \text{ [}\mu\text{F]} \cdot \frac{d}{dt} \left[\frac{d}{dt} (0.1 - 0.1045 e^{-93t} + 0.0045 e^{-1917t}) \right]$$

$$i_{C1}(t) = (-0.0045 e^{-93t} + 0.1045 e^{-1917t}) \text{ [A]}$$

+2 final $i_{C1}(t)$ eq.

10 pts so far.

⑨ $t > 1 \text{ [ms]}$ time segment 2

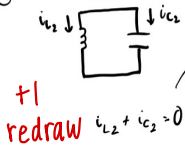

$$v_{L2} = v_{L2}$$

$$i_{L2} = -i_{C2}$$

$$i_{C2} = C \cdot \frac{dv_{L2}}{dt} = C \cdot \frac{d}{dt} v_{L2} = LC \frac{d^2 i_{L2}}{dt^2} = -LC \frac{d^2 i_{C2}}{dt^2}$$

$$i_{C2} = -LC \frac{d^2 i_{C2}}{dt^2} = -LC i_{C2}''$$

$$i_{C2}'' + \frac{1}{LC} i_{C2} = 0$$

⑩ general form is similar to underdamped: $[i_{C2}(t) = A_1 \cos \omega_0 t + B_1 \sin \omega_0 t]$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 400 \text{ [rad/s]} \quad +1 \text{ for } \omega_0$$

⑪ get $i_L(t)$ and $v_C(t)$ for both time segments

$$i_{L1}(1 \text{ [ms]}) = 0.0045 \text{ [A]} \quad (\text{plug into } ⑦)$$

$$i_{L2}(1 \text{ [ms]}) = -i_{C2}(1 \text{ [ms]}) = -0.92 A_1 - 0.39 B_1 \quad ① \quad (\text{plug into } ⑩)$$

two time segments

$$v_{C1}(t) = v_{L1}(t) = L \cdot i_{L1}'(t)$$

$$v_{C1}(t) = L \cdot [0.1045 \cdot 83 e^{-83t} - 0.0045 \cdot 1917 e^{-1917t}]$$

$$v_{C1}(1 \text{ [ms]}) = 16.36 \text{ [V]} \quad +2 \text{ for correct } v_{C1}$$

$$v_{C2}(t) = v_{L2}(t) = L \cdot i_{L2}'(t) = -L \cdot i_{C2}'(t)$$

$$v_{C2}(t) = -L \cdot \frac{d}{dt} (A_1 \cos 400t + B_1 \sin 400t) = 1000 (A_1 \sin 400t - B_1 \cos 400t)$$

$$⑫ \quad v_{C2}(1 \text{ [ms]}) = 389 A_1 - 921 B_1 \quad ②$$

① solve system: $A_1 = 2.43 \times 10^{-3} \text{ [A]}$
 $B_1 = -0.017 \text{ [A]}$

$$i_{C2}(t) = (2.43 \times 10^{-3} \cdot \cos 400t - 0.017 \sin 400t) \text{ [A]}$$

+2
final equation

+2 correct system of eq's.

+1 correct value A_1
+1 correct value B_1