

Chapter 6: Problems 6.14, 6.17, 6.22, 6.25, 6.29, 6.32, 6.35, 6.40, 6.46

*6.14 In the circuit of Fig. P6.12, $V_0 = 12\text{ V}$, $R_1 = 0.4\ \Omega$, $R_2 = 1.2\ \Omega$, and $L = 0.1\text{ H}$. What should the value of C be in order for $i_L(t)$ to exhibit a critically damped response? Provide an expression for $i_L(t)$ and plot its waveform for $t \geq 0$.


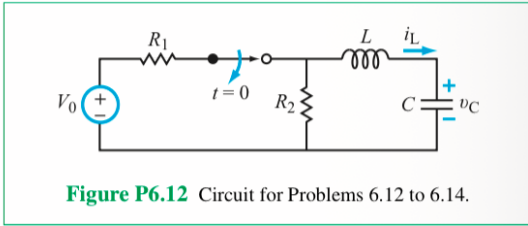


Figure P6.12 Circuit for Problems 6.12 to 6.14.

critical $\rightarrow \alpha = \omega_0$

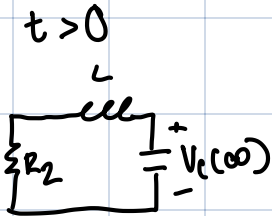$\alpha = \frac{R_2}{2L}$ $\omega_0 = \frac{1}{\sqrt{LC}}$



$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Solve for C

$$\left(\frac{R_2}{2L}\right)^2 = \left(\frac{1}{\sqrt{LC}}\right)^2$$

$$\frac{R_2^2}{4L^2} = \frac{1}{LC}$$

$\downarrow$

Inverse

$$\frac{4L^2}{R_2^2} = LC \rightarrow C = \frac{4L^2}{R_2^2} \rightarrow \frac{4L}{R_2^2} = \frac{4(0.1[H])}{(1.2)^2[\Omega]}$$

$$= 0.28[C]$$

$$\alpha = \frac{R_2}{2L} = \frac{1.2[\Omega]}{2(0.1[H])} = 6$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.1)(0.28[C])}} = 6$$

Product Rule

$$r' = 54[V] + 54[V]t$$

$$g' = -6e^{-6t} \quad g = e^{-6t}$$

$$i_L(t) = 0.28[F] \frac{dv_C}{dt} (9 + 54t)e^{-6t}$$

$$i_C = C \frac{di_L(t)}{dt}$$

$$0.28[C] [-54[V]e^{-6t} + (54[V]e^{-6t} - 6t \cdot 54[V]t)]$$

$$0.28[C] (-60[V] + 54[V]t)e^{-6t}$$

$$= -90.72te^{-6t}$$

$$i_L(t) = C \frac{dv_C(t)}{dt}$$

Solve for B_1 B_2

$$B_1 = v_C(0) - v_C(\infty)$$

$$B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$$

$t < 0_s$

$$v_C(\infty) = 0[V]$$

$$v_C(0) = 12[V] \cdot \frac{1.2[\Omega]}{1.6[\Omega]} = 9[V]$$

$$i_C(0) = 0[A]$$

$$B_1 = 9[V] - 0[V]$$

$$B_2 = \frac{1}{C} \cdot 0[A] + 6[9 - 0] = 54[V]$$

$$v_C(t) = (B_1 + B_2 t)e^{-\alpha t} + v_C(\infty) = 0$$

$$9[V] + 54[V]e^{-6t} + 0[V]$$

$$v_C(t)[V]$$



Table 6-1: Step response of RLC circuits for $t \geq 0$.

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{1}{C} \frac{i_C(0) - s_2 [v_C(0) - v_C(\infty)]}{s_1 - s_2}$ $A_2 = \frac{1}{C} \frac{i_C(0) - s_1 [v_C(0) - v_C(\infty)]}{s_2 - s_1}$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{1}{L} \frac{v_L(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2}$ $A_2 = \frac{1}{L} \frac{v_L(0) - s_1 [i_L(0) - i_L(\infty)]}{s_2 - s_1}$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t)e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t)e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{1}{C} \frac{i_C(0) + \alpha [v_C(0) - v_C(\infty)]}{\omega_d}$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{1}{L} \frac{v_L(0) + \alpha [i_L(0) - i_L(\infty)]}{\omega_d}$
Auxiliary Relations $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	Auxiliary Relations $\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_{1,2} = -\alpha \pm j\omega_d$

6.17 A series RLC circuit exhibits the following voltage and current responses:

$$v_C(t) = (6 \cos 4t - 3 \sin 4t) e^{-2t} \text{ V},$$

$$i_C(t) = -(0.24 \cos 4t + 0.18 \sin 4t) e^{-2t} \text{ A}.$$

Determine α , ω_0 , R , L , and C .

Note: Don't use Ohm's Law on a capacitor

$$a = 2$$

$$\omega_0 = 2\sqrt{5}$$

$$R = 10[\Omega]$$

$$L = 2.5[H]$$

$$C = .02[F]$$

$$(\omega_d)^2 = (\omega_0^2 - a^2) \rightarrow$$

$$\omega_d^2 = \omega_0^2 - a^2$$

$$\rightarrow \omega_0 = \sqrt{\omega_d^2 + a^2}$$

$$\sqrt{4^2 + 2^2} = 2\sqrt{5}$$

3 unknowns, 3 eq.

$$a = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_d = \sqrt{\omega_0^2 - a^2}$$



$$\frac{1}{\sqrt{LC}} = \omega_0 \rightarrow \frac{1}{2(\sqrt{LC(.02)})} = (2\sqrt{5})^2$$

$$\frac{1}{LC(.02) \cdot .02} = 10 : .02 \rightarrow .2$$

$$\frac{1}{L} = .2$$

$$L = 2.5$$

Table 6-1: Step response of RLC circuits for $t \geq 0$.

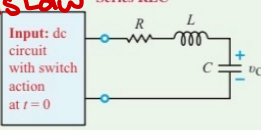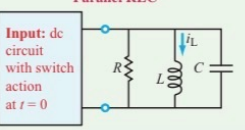Series RLC	Parallel RLC
	
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{1}{s_1 - s_2} [i_C(0) - s_2 [v_C(0) - v_C(\infty)]]$ $A_2 = \frac{1}{s_2 - s_1} [i_C(0) - s_1 [v_C(0) - v_C(\infty)]]$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{1}{s_1 - s_2} [v_L(0) - s_2 [i_L(0) - i_L(\infty)]]$ $A_2 = \frac{1}{s_2 - s_1} [v_L(0) - s_1 [i_L(0) - i_L(\infty)]]$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{L} [i_C(0) + \alpha [v_C(0) - v_C(\infty)]]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{1}{\omega_d} [i_C(0) + \alpha [v_C(0) - v_C(\infty)]]$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{1}{\omega_d} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]$
Auxiliary Relations $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$	
$\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$	

$$D_1 = 6[V] - 0[V]$$

$$D_2 = \frac{1}{C} i_C(0) + 2[6[V] - 0[V]]$$

$$4$$

$$i_C(0) = -.24$$

$$\frac{\frac{1}{C} (-.24) + 12[V]}{4}$$

$$C = .02[C]$$

$$R = 4L$$

$$4(2.5) = 10[\Omega]$$

Table 6-1: Step response of RLC circuits for $t \geq 0$.

6.22 Determine $i_C(t)$ in the circuit of Fig. P6.22 and plot its waveform for $t \geq 0$.

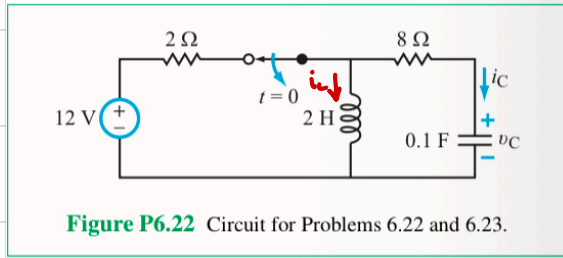


Figure P6.22 Circuit for Problems 6.22 and 6.23.

$$\alpha < \omega_0$$

Find $V_C(t)$ $t > 0$

$$\alpha = \frac{R}{2L} \rightarrow \frac{8}{2 \cdot 2} \rightarrow 2 [s^{-1}]$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \frac{1}{\sqrt{2 \cdot 0.1}} = 2.236 [rad/s]$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \rightarrow \sqrt{2.236^2 - 2^2} = 1$$

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{1}{s_1 - s_2} [\frac{1}{C} i_C(0) - s_2 [v_C(0) - v_C(\infty)]]$ $A_2 = \frac{1}{s_2 - s_1} [\frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]]$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{1}{s_1 - s_2} [v_L(0) - s_2 [i_L(0) - i_L(\infty)]]$ $A_2 = \frac{1}{s_2 - s_1} [v_L(0) - s_1 [i_L(0) - i_L(\infty)]]$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{1}{\omega_d} [\frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]]$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{1}{\omega_d} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]$
Auxiliary Relations $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$	
$\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$	

$$i_C(t) = C \frac{dV_C(t)}{dt}$$


$$V_C(t) = e^{-\alpha t} (D_1 \cos(\omega_d t) + D_2 \sin(\omega_d t)) + V_C(\infty)$$

$$V_C(\infty) = 0 [V] = V_C(0)$$

$$D_1 = 0 [V]$$

$$D_2 = \frac{1}{C} \cdot i_C(0) + \alpha [V_C(0) - V_C(\infty)] \rightarrow \frac{6 [A]}{0.1 [F]} + \alpha [V_C(0) - V_C(\infty)]$$

$t = 0$

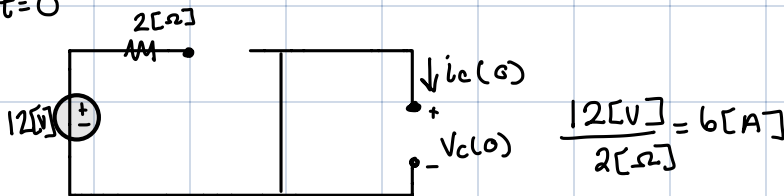

$$\frac{12 [V]}{2 [\Omega]} = 6 [A]$$

$$V_C(t) = e^{-2t} (0 [V] \cos(1)t + 60 [V] \sin(1)t) + 0 [V] \rightarrow V_C'(t) = (60 [V] \cos t) e^{-2t} - (120 [V] \sin t) e^{-2t}$$

$$i_C(t) = C \cdot V_C'(t)$$

$$0.1 [F] [V_C'(t) = (60 [V] \cos t) e^{-2t} - (120 [V] \sin t) e^{-2t}]$$

$$i_C(t) = (6 [V] \cos t + 12 [V] \sin t) e^{-2t}$$

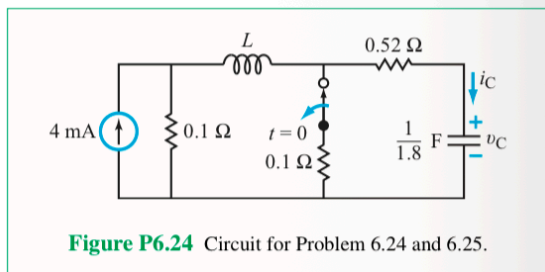


Figure P6.24 Circuit for Problem 6.24 and 6.25.

*6.25 Choose the value of the inductor in the circuit of Fig. P6.24 so that v_C exhibits a critically damped response and determine $v_C(t)$ for $t \geq 0$.

?

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}} \rightarrow \left(\frac{2L}{R}\right) = \left(\frac{\sqrt{LC}}{1}\right)^2$$

$$\frac{4L^2}{R^2} = \frac{LC}{1} \rightarrow \frac{R^2}{4} \frac{4L}{R^2} = C \cdot \frac{R^2}{4}$$


$$L = \frac{(R^2)}{4} \rightarrow \frac{(0.62 \Omega)^2}{4} (0.556 \text{ F}) = 0.0634 \text{ H}$$

$$\alpha = \frac{0.62 \Omega}{2(0.0634 \text{ H})} = 5.805 \text{ s}^{-1} \quad \omega_0 = \frac{1}{\sqrt{LC}} = \cancel{4.24 \text{ rad/s}}$$

Since α is equal to ω_0 , the value of ω_0 will be the same as α .

$$B_1 = (v_C(0) - v_C(\infty)) \text{ [V]} = (0.248 - 0.4) \text{ [mV]} = -0.15 \text{ [mV]}$$

$t < 0$ $t > 0$

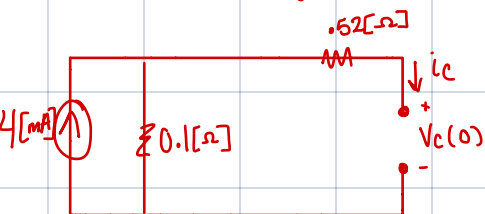


$$B_2 = \frac{1}{C} i_C(0) + \alpha [(0.248 - 0.4) \text{ [mV]}]$$

$$1.8(2.48 \text{ [mA]}) + 5.805 \text{ [s}^{-1} \text{]} (-0.15 \text{ [mV]}) = 3.593 \text{ [mV]}$$

$$4 \text{ [mA]} \times 0.62 \Omega = 0.00248 \text{ [V]} \quad \text{Req} = 0.1 \Omega + 0.62 \Omega = 0.72 \Omega \rightarrow i_C(0) = \frac{V_C(t)}{0.1 \Omega} \rightarrow \frac{0.248 \text{ [mV]}}{0.1 \Omega} = 2.48 \text{ [mA]}$$

$t > 0$

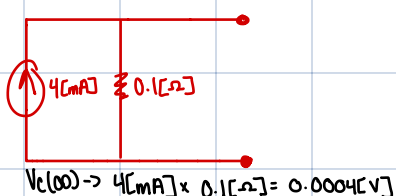

$$v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$$

$$v_C(t) = ((-0.248 \text{ [mV]} + 3.593 \text{ [mV]} t) e^{-5.805 t} + 0.4 \text{ [mV]})$$

Table 6-1: Step response of RLC circuits for $t \geq 0$.

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{1}{C} \frac{i_C(0) - s_2 [v_C(0) - v_C(\infty)]}{s_1 - s_2}$ $A_2 = \frac{1}{C} \frac{i_C(0) - s_1 [v_C(0) - v_C(\infty)]}{s_2 - s_1}$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{1}{L} \frac{v_L(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2}$ $A_2 = \frac{1}{L} \frac{v_L(0) - s_1 [i_L(0) - i_L(\infty)]}{s_2 - s_1}$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{1}{C} \frac{i_C(0) + \alpha [v_C(0) - v_C(\infty)]}{\omega_d}$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{1}{L} \frac{v_L(0) + \alpha [i_L(0) - i_L(\infty)]}{\omega_d}$
Auxiliary Relations $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_{1,2} = -\alpha \pm j\sqrt{\alpha^2 - \omega_0^2}$	

Table 6-1: Step response of RLC circuits for $t \geq 0$.

* 6.29 Choose the value of C in the circuit of Fig. P6.29 so that $v_C(t)$ has a critically damped response for $t \geq 0$. Plot the waveform of $v_C(t)$.


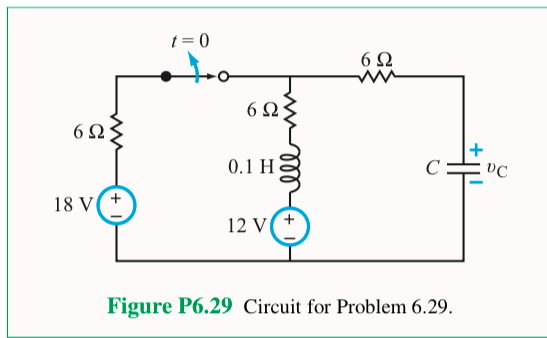


Figure P6.29 Circuit for Problem 6.29.

Part a) Find C


C from critically damp

In series

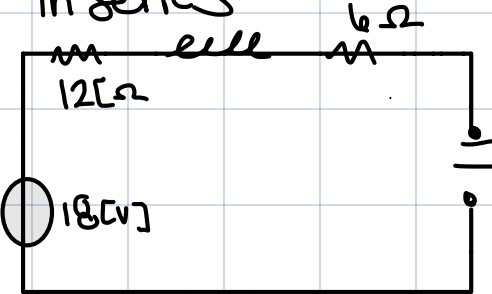


$$\frac{R}{2L} = \frac{1}{\sqrt{LC}} \rightarrow \text{Solving for } C = \frac{4L}{R^2} = \frac{4(.1)}{(12)^2} = 2.778 \text{ mF}$$

Part b) $t < 0$

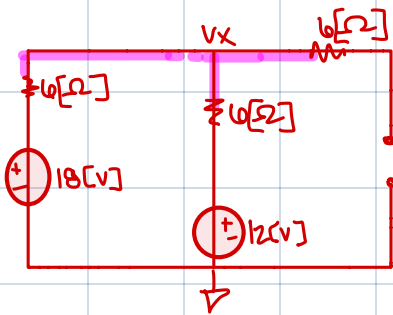

$t > 0$

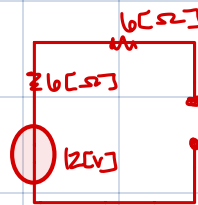

$$\begin{aligned} v_C(\infty) &= 12 \text{ V} \\ i_C(0) &= \frac{12 \text{ V}}{6 \Omega} = -0.5 \text{ A} \\ i_C(0) + 0.5 \text{ A} &= 0 \end{aligned}$$

$$v_C(0) = 15 \text{ V} \leftarrow v_C(0) = 15 \text{ V}$$

$$\frac{v_x - 18 \text{ V}}{6 \Omega} - \frac{v_x - 12 \text{ V}}{6 \Omega} + \frac{v_x}{6 \Omega} = 0$$

$$\alpha = \frac{R}{2L} \rightarrow \frac{12 \Omega}{2(0.1 \text{ H})} = 60 \text{ s}^{-1} = \omega_0 = 60 \text{ rad/s}$$

$$v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$$

$$B_1 = 15 \text{ V} - 12 \text{ V} = 3 \text{ V}$$

$$B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$$

$$B_2 \frac{-0.5 \text{ A}}{2.778 \text{ mF}} + 60 [3 \text{ V}] = 0$$

$$B_2 = 14.399 \text{ mV}$$

$$v_C(t) = (3 \text{ V} + 14.39 \text{ mV} t) e^{-60t} + 12 \text{ V}$$

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{\frac{1}{C} i_C(0) - s_2 [v_C(0) - v_C(\infty)]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{C} i_C(0) - s_1 [v_C(0) - v_C(\infty)]}{s_2 - s_1}$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{\frac{1}{L} v_L(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{L} v_L(0) - s_1 [i_L(0) - i_L(\infty)]}{s_2 - s_1}$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{\frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]}{\omega_d}$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{\frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]}{\omega_d}$
Auxiliary Relations	
$\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	$\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_{1,2} = -\alpha \pm j\omega_d$

* 6.32 For the circuit in Fig. P6.32, assume that before $t = 0$, the circuit had been in that state for a long time. Find $v_C(t)$ and $i_L(t)$ for $t \geq 0$.

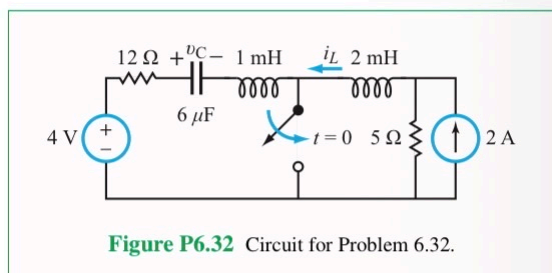


Figure P6.32 Circuit for Problem 6.32.

Step 2:


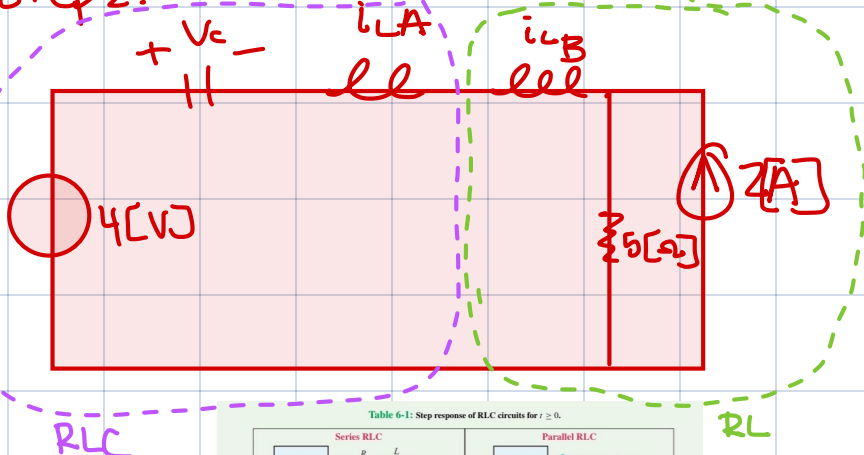


Table 6-1: Step response of RLC circuits for $t \geq 0$.

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{1}{s_1 - s_2} [s_2 (v_C(0) - v_C(\infty)) - v_C'(0)]$ $A_2 = \frac{1}{s_1 - s_2} [s_1 (v_C(0) - v_C(\infty)) - v_C'(0)]$	Total Response Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{1}{s_1 - s_2} [s_2 (i_L(0) - i_L(\infty)) - i_L'(0)]$ $A_2 = \frac{1}{s_1 - s_2} [s_1 (i_L(0) - i_L(\infty)) - i_L'(0)]$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{\alpha} [v_C'(0) + \alpha (v_C(0) - v_C(\infty))]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{\alpha} [i_L'(0) + \alpha (i_L(0) - i_L(\infty))]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{1}{\omega_d} [v_C'(0) + \alpha (v_C(0) - v_C(\infty))]$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{1}{\omega_d} [i_L'(0) + \alpha (i_L(0) - i_L(\infty))]$
Auxiliary Relations Series RLC: $\alpha = \frac{R}{2L}$, $\omega_0 = \frac{1}{\sqrt{LC}}$ Parallel RLC: $\alpha = \frac{1}{2RC}$, $\omega_0 = \sqrt{\frac{C}{L}}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	

Step 1:

$$+ < 0 [V]$$

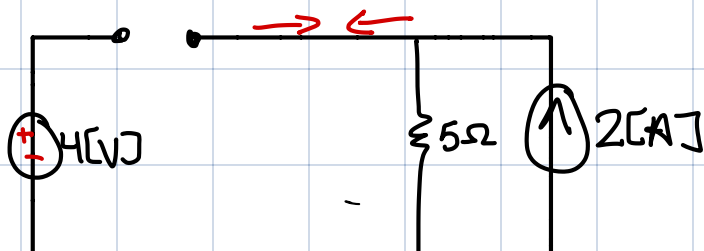

$$v_C(0^-) = -4[V] + v_C(0^-) + 10[V] = 0$$

$$v_C(0^-) = -6[V]$$

$$i_{L A}(0^-) = 0[A] = i_{L B}(0^-)$$

Step 3: RLC

Underdamp formula

$$v_C(t) = e^{-12909.9t} (-10 \cos(11430.9t) - 5.249 \sin(11430.9t)) + 4[V]$$

Step 6:

$$D_1 = (-6[V] - 4[V]) = -10[V]$$

Step 7:


$$D_2 = \frac{6000[-10]}{11430.95} = -5.249[V]$$

Steps:

$$v_C(\infty) = 4[V]$$

Step 4:
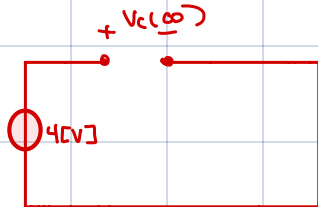
$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \Rightarrow \sqrt{6000^2 - 12909.9^2} = 11430.95 [rad/s]$$



$$v_C(\infty) = 4[V]$$

Because the cap. is in series with the inductor.
 $\hookrightarrow i_C(0) = 0[A]$

$$\alpha = \frac{R}{2L} < \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{12[\Omega]}{2(1[mH])} = 6000[s^{-1}]$$


$$\sqrt{(1[mH])(6[\mu F])} = 12909.9 [rad/s]$$

RL

$$i_L(t)$$

$$i_L(0^-) = 0[A]$$

$$i_L(\infty) = 2[A]$$

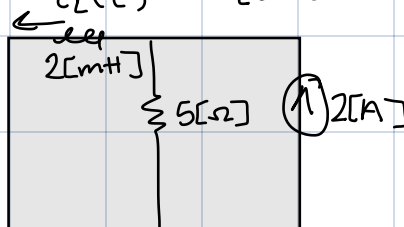

$$Z = \frac{2[mH]}{5[\Omega]} = 0.4[mA]$$

$$2[A] - 2[A] e^{-\frac{t}{0.4[mA]}} \text{ for } t \geq 0$$

*6.35 For the circuit in Fig. P6.35, find $v_C(t)$ for $t \geq 0$.

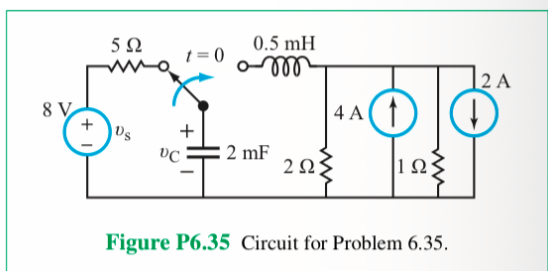


Figure P6.35 Circuit for Problem 6.35.

Step 1. Solve for α & ω_0
this will help you know where the circuit is in the formulas.

$$\alpha = \frac{R}{2L} = \frac{5\Omega}{2(0.5\text{mH})} = 5000\text{ [s}^{-1}\text{]}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.5\text{mH})(2\text{mF})}} = 1000\text{ [s}^{-1}\text{]}$$

$\alpha < \omega_0 = \text{Underdamp.}$


Table 6-1: Step response of RLC circuits for $t \geq 0$.

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{\frac{1}{C} i_C(0) - s_2 [v_C(0) - v_C(\infty)]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{C} i_C(0) - s_1 [v_C(0) - v_C(\infty)]}{s_2 - s_1}$	Total Response Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{\frac{1}{L} v_L(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{L} v_L(0) - s_1 [i_L(0) - i_L(\infty)]}{s_2 - s_1}$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{\frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]}{\omega_d}$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{\frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]}{\omega_d}$
Auxiliary Relations $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	

Step 2: $t < 0$

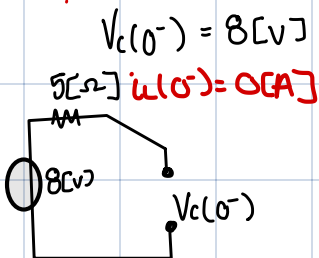

Step 3: $t = 0$

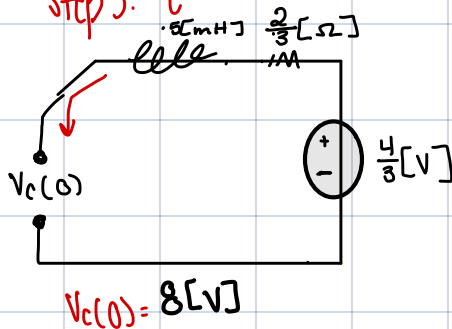

Step 4: $t \geq 0$

$$v_C(\infty) = \frac{4}{3}\text{ [V]}$$

$$v_C(t) = e^{-6666.67t} (6.6667\text{ [V]} \cos(745.35t) + 5.963 \sin(745.35t) + 1.33\text{ [V]})$$

$$D_1 = 8 - \frac{4}{3} = 6.6667\text{ [V]}$$

$$D_2 = \frac{\alpha [v_C(0) - v_C(\infty)]}{\omega_d} \rightarrow \sqrt{\omega_0^2 - \alpha^2} = 745.35$$

$$\frac{6.6667(6.6667)}{745.35} = 5.963\text{ [V]}$$

$$v_C'(0) = \frac{i_C(0)}{C}$$

$$i_C(0) = i_L(0) = 0$$

* 6.40 Determine $i_L(t)$ in the circuit of Fig. P6.40 and plot its waveform for $t \geq 0$.

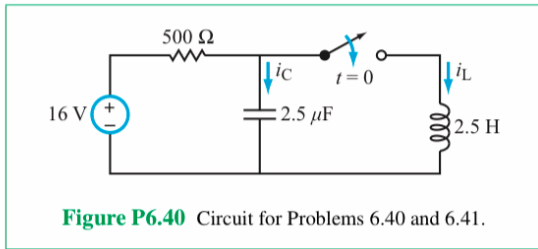


Figure P6.40 Circuit for Problems 6.40 and 6.41.

$\alpha = \omega_0$
critically damp.

$$\alpha = \frac{1}{2RC} \rightarrow \frac{1}{2(500\Omega)(2.5\mu F)} = 400[s^{-1}]$$


$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow \frac{1}{\sqrt{2.5\mu F}(2.5H)} \rightarrow 400[rad/s]$$



$$i_L(0) = \frac{16[V]}{500[\Omega]} = 32[mA]$$

$$B_1 = 0[A] - 32[mA] = -32[mA]$$
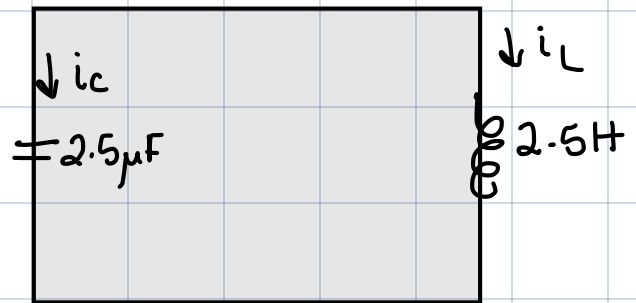
$$B_2 = \frac{16[V]}{2.5} + 400[s^{-1}](-32[mA]) = -6.4[A]$$



$$i_L(t) = [(-32[mA] - 6.4(t)[A])e^{-400t} + 32[mA]]$$

Table 6-1: Step response of RLC circuits for $t \geq 0$.

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{\frac{1}{C} i_C(0) - s_2 [v_C(0) - v_C(\infty)]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{C} i_C(0) - s_1 [v_C(0) - v_C(\infty)]}{s_2 - s_1}$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{\frac{1}{L} v_L(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{L} v_L(0) - s_1 [i_L(0) - i_L(\infty)]}{s_2 - s_1}$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{\frac{1}{C} i_C(0) + \alpha [v_C(0) - v_C(\infty)]}{\omega_d}$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{\frac{1}{L} v_L(0) + \alpha [i_L(0) - i_L(\infty)]}{\omega_d}$
Auxiliary Relations	
$\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	$\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

$$i_C(0) = \frac{16[V]}{2.5\mu F} = 6.4[A]$$

$$v_L(0) = 16[V]$$

$$i_L(0) = 0[A]$$

*6.46 In the circuit in Fig. P6.46, $v_s = 20$ V.

- (a) Determine $i_L(t)$ for $t \geq 0$.
 (b) If the source is changed to $v_s(t) = e^{-2t} u(t)$, can you still use the solution method in part (a) to find $i_L(t)$? If not, why not?


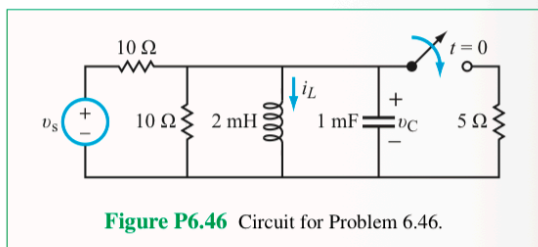


Figure P6.46 Circuit for Problem 6.46.

$$Q = \frac{1}{2RC} \rightarrow \frac{1}{2(20\Omega)(10^{-3})} = 25 [s^{-1}]$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow \frac{1}{\sqrt{2mH \cdot 1mF}} = 707.107 [rad/s]$$

$Q < \omega_0 \leftarrow$ under damped.

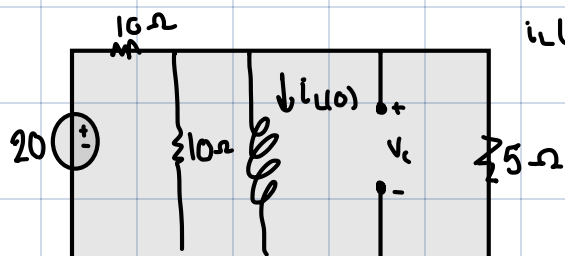

$$i_L(0) = \frac{V_s}{R_{eq}} \rightarrow \frac{20[V]}{10[\Omega]} \rightarrow 2[A]$$

$$v_L(0) = 20[V]$$

a)

$$i_L(t) = 2[A]$$

b) N/A, only works for dc sources.

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{1}{s_1 - s_2} [i_C(0) - s_2 [v_C(0) - v_C(\infty)]]$ $A_2 = \frac{1}{s_2 - s_1} [i_C(0) - s_1 [v_C(0) - v_C(\infty)]]$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{1}{s_1 - s_2} [v_L(0) - s_2 [i_L(0) - i_L(\infty)]]$ $A_2 = \frac{1}{s_2 - s_1} [v_L(0) - s_1 [i_L(0) - i_L(\infty)]]$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} [i_C(0) + \alpha [v_C(0) - v_C(\infty)]]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{1}{\omega_d} [i_C(0) + \alpha [v_C(0) - v_C(\infty)]]$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{1}{\omega_d} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]$
Auxiliary Relations $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$	
$\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$	