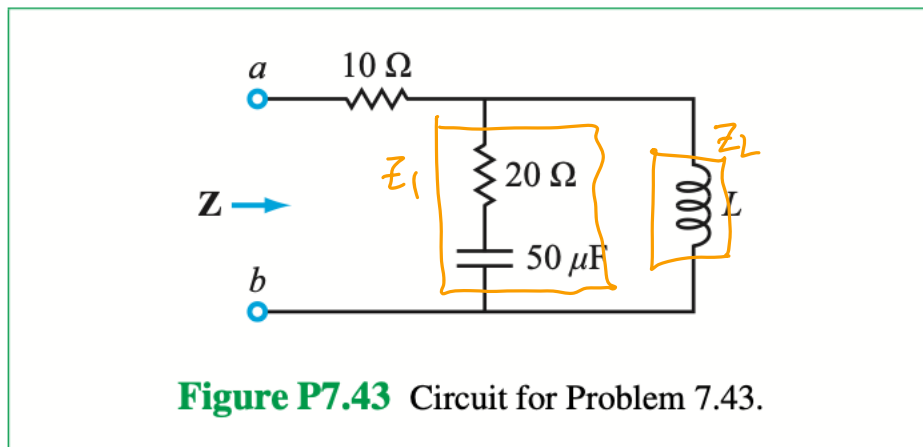


10 ~~9~~ Quiz / In-class Assignment

Name: _____ PSID: _____

Problem 1

7.43 At $\omega = 400$ rad/s, the input impedance of the circuit in **Fig. P7.43** is $\mathbf{Z} = (74 + j72) \Omega$. What is the value of L ?



$$Z_1 = 20[\Omega] - \frac{j}{400[\frac{\text{rad}}{\text{s}}] \cdot 50[\mu\text{F}]} = (20 - j50)[\Omega]$$

$$Z = 10[\Omega] + Z_1 \parallel Z_L = (74 + j72)[\Omega]$$

$$Z_1 \parallel Z_L = \frac{Z_1 Z_L}{Z_1 + Z_L} = (64 + j72)[\Omega]$$

$$Z_1 Z_L = (64 + j72)[\Omega] (Z_1 + Z_L)$$

$$Z_L (Z_1 - (64 + j72)[\Omega]) = (64 + j72)[\Omega] \cdot Z_1$$

$$Z_L = \frac{(64 + j72)(20 - j50)}{20 - j50 - (64 + j72)} [\Omega]$$

$$Z_L = j40[\Omega]$$

$$Z_L = j\omega L$$

$$L = \frac{Z_L}{j\omega} = \frac{j40[\Omega]}{j400[\frac{\text{rad}}{\text{s}}]}$$


$$Z_L = \underline{j40[\Omega]}$$

$$L = \underline{100[\text{mH}]}$$

$$L = 0.1[\text{H}]$$

Problem 2

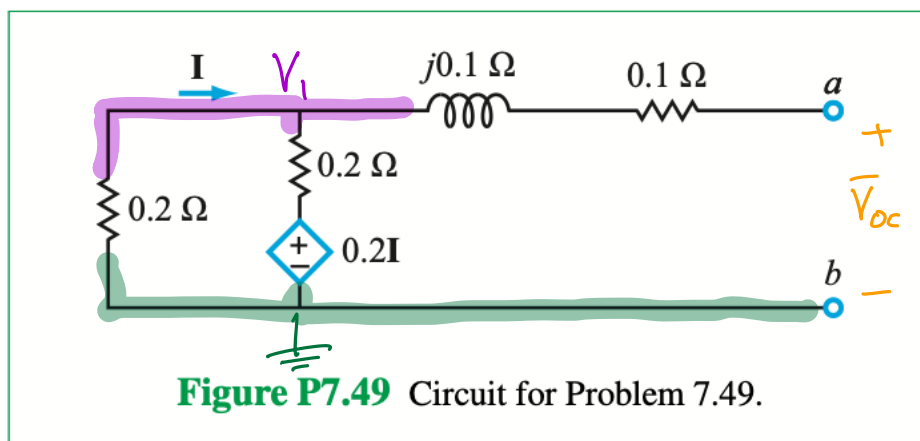7.49 The circuit in **Fig. P7.49** is in the phasor domain. Determine its Thévenin equivalent at terminals (a, b) .




$$\left[\frac{V_1 - 0.2[\Omega]I}{0.2[\Omega]} + \frac{V_1}{0.2[\Omega]} = 0 \right] \times 0.2[\Omega] \quad I = -\frac{V_1}{0.2[\Omega]}$$

$$2V_1 + V_1 = 0$$

$$V_1 = 0$$

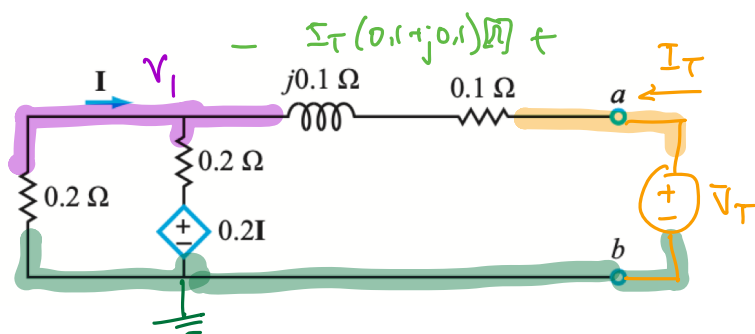this makes sense -
no independent source
to activate the dependent
source



$$\left[\frac{V_1}{0.2[\Omega]} + \frac{V_1 - 0.2[\Omega]I}{0.2[\Omega]} - I_T = 0 \right] \times 0.2[\Omega]$$

$$\underbrace{V_1 + V_1 - 0.2[\Omega]\left(-\frac{V_1}{0.2[\Omega]}\right)}_{3V_1} - 0.2[\Omega]I_T = 0 \Rightarrow 3V_T - I_T(0.3 + j0.3)[\Omega] - 0.2[\Omega]I_T = 0$$


$$V_T = V_1 + I_T(0.1 + j0.1)[\Omega]$$

$$V_1 = V_T - I_T(0.1 + j0.1)[\Omega]$$


$$3V_T = (0.5 + j0.3)[\Omega] I_T$$

$$Z_{Th} = \frac{V_T}{I_T} = \frac{(0.5 + j0.3)[\Omega]}{3}$$

Thévenin Equiv.:

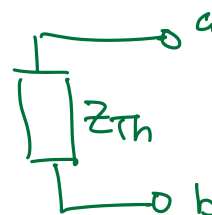

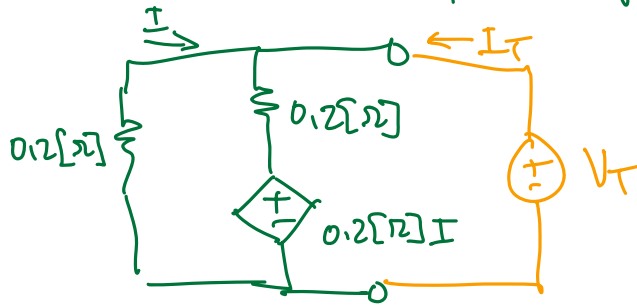you can get to the answer faster by first finding the equiv. resistance of the left hand side of the circuit:



$$V_T = -I \cdot 0.2[\Omega] \Rightarrow I = -\frac{V_T}{0.2[\Omega]}$$

$$(I + I_T) 0.2[\Omega] + 0.2[\Omega] I = V_T$$

$$\left(-\frac{V_T}{0.2[\Omega]} + I_T\right) 0.2[\Omega] - 0.2[\Omega] \cdot \frac{V_T}{0.2[\Omega]} = V_T$$

$$-V_T + 0.2[\Omega] I_T - V_T = V_T$$

$$3V_T = 0.2[\Omega] I_T$$

$$\frac{V_T}{I_T} = \frac{0.2[\Omega]}{3}$$

$$Z_{Th} = \frac{V_T}{I_T} + [0.1 + j0.1][\Omega]$$

$$= \frac{0.2[\Omega]}{3} + \frac{0.3 + j0.3}{3}[\Omega]$$

$$Z_{Th} = \frac{0.5 + j0.3}{3}[\Omega]$$