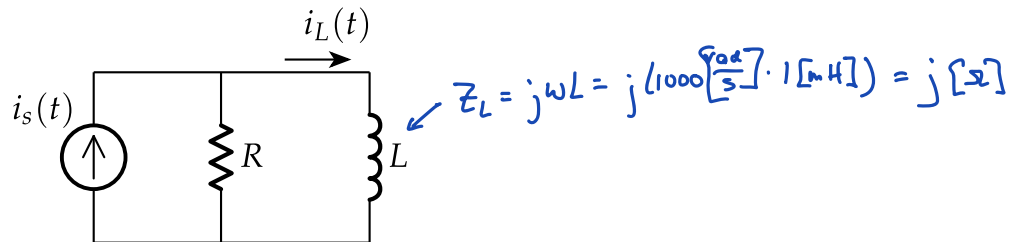


Quiz 9/In-class Assignment

Name: _____ PSID: _____

Problem 1

For the following circuit, $i_s(t) = 12 \cos(1000t - 30^\circ)$ [mA], $R = 2$ [Ω], and $L = 1$ [mH].
Write a solution for $i_L(t)$.



$$\bar{I}_L = \bar{I}_s \frac{R}{R + Z_L} = 12 [\text{mA}] \angle -30^\circ \cdot \frac{2 [\Omega]}{2 [\Omega] + j[2]}$$

$$= 12 [\text{mA}] \angle -30^\circ \cdot \frac{2}{2 + j}$$

$$= \left(12 [\text{mA}] \cos(-30^\circ) + j 12 [\text{mA}] \sin(-30^\circ) \right) \frac{2}{2 + j}$$

$$= (5.91 - j 8.96) [\text{mA}]$$

$$= 10.7 [\text{mA}] \angle -56.6^\circ$$

$$\Rightarrow i_L(t) = 10.7 [\text{mA}] \cos(1000t - 56.6^\circ)$$


$i_L(t) =$ _____

Problem 2

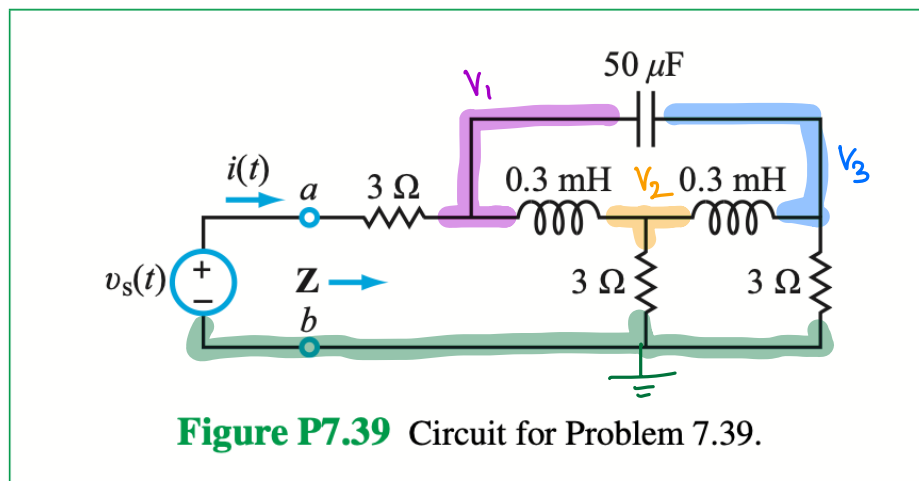7.39 The voltage source in the circuit of **Fig. P7.39** is given by

$$v_s(t) = 12 \cos 10^4 t \text{ V.}$$

- Transform the circuit to the phasor domain and then determine the equivalent impedance $\mathbf{Z}$ at terminals (a, b) . (~~Hint: Application of Δ -Y transformation should prove helpful.~~)
- Determine the phasor $\mathbf{I}$, corresponding to $i(t)$.
- Determine $i(t)$.



$$Z_1 = j \frac{10^4 \left[\frac{1}{5} \right]}{0.3 \text{ [mH]}} = j \frac{10 \cdot 0.3 \text{ [s]}}{0.3} = j 3 \text{ [s]}$$

$$Z_2 = \frac{-j}{10^4 \left[\frac{1}{5} \right] \cdot 50 \text{ [uF]}} = \frac{-j}{50 \cdot 10^{-2}} \text{ [s]} = -j 2 \text{ [s]}$$

$$\left[\frac{\bar{V}_1 - 12 \text{ [v]}}{3 \text{ [s]}} + \frac{\bar{V}_1 - \bar{V}_2}{j 3 \text{ [s]}} + \frac{\bar{V}_1 - \bar{V}_3}{-j 2 \text{ [s]}} = 0 \right] + 6 \text{ [s]}$$

$$2\bar{V}_1 - 24 \text{ [v]} - j2(\bar{V}_1 - \bar{V}_2) + j3(\bar{V}_1 - \bar{V}_3) = 0$$

$$(2+j)\bar{V}_1 + j2\bar{V}_2 - j3\bar{V}_3 = 24 \text{ [v]}$$

using calculator:

$$\bar{V}_1 = \left(\frac{27}{5} + j \frac{9}{5} \right) \text{ [v]} = (5.4 - j 1.8) \text{ [v]}$$

$$\bar{V}_2 = j \frac{12}{5} \text{ [v]} = j 2.4 \text{ [v]}$$

$$\bar{V}_3 = \left(3 + j \frac{33}{5} \right) \text{ [v]} = (3 + j 6.6) \text{ [v]}$$

$$\left[\frac{\bar{V}_2 - \bar{V}_1}{j 3 \text{ [s]}} + \frac{\bar{V}_2}{3 \text{ [s]}} + \frac{\bar{V}_2 - \bar{V}_3}{j 3 \text{ [s]}} = 0 \right] \times 3 \text{ [s]}$$

$$-j\bar{V}_2 + j\bar{V}_1 + \bar{V}_2 - j\bar{V}_2 + j\bar{V}_3 = 0$$

$$j\bar{V}_1 + (1-j2)\bar{V}_2 + j\bar{V}_3 = 0$$

$$\times 6 \text{ [s]} \left[\frac{\bar{V}_3 - \bar{V}_1}{-j 2 \text{ [s]}} + \frac{\bar{V}_3 - \bar{V}_2}{j 3 \text{ [s]}} + \frac{\bar{V}_3}{3 \text{ [s]}} = 0 \right]$$

$$j 3 \bar{V}_3 - j 3 \bar{V}_1 - j 2 \bar{V}_3 + j 2 \bar{V}_2 + 2 \bar{V}_3 = 0$$

$$-j 3 \bar{V}_1 + j 2 \bar{V}_2 + (2+j) \bar{V}_3 = 0$$

$$\begin{aligned}\bar{I} &= \frac{12[V] - (5.4 - j1.8)[V]}{3[\Omega]} = (2.2 + j0.6)[A] \\ &= 2.28[A] \angle 15.2^\circ\end{aligned}$$

$$Z = \frac{\bar{V}}{\bar{I}} = \frac{12[V]}{(2.2 + j0.6)[A]} = (5.08 - j1.38)[\Omega]$$

$$i(t) = 2.28[A] \cos\left(10^4 \left[\frac{\text{rad}}{\text{s}}\right] t + 15.2^\circ\right)$$