

HW 6:

Problem 1:

$$V_0 = \frac{R_2}{R_1} V_{id}$$


$$R_{id} = 10 K\Omega$$

$$A_{cm} = 0.0095$$

$$CMRR = 66.4 dB$$

Problem 2:

Prob 2:

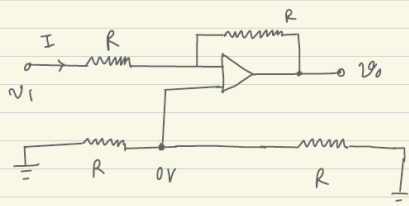

$$V_1 + \frac{V_0 - V_1}{2} = \frac{V_2}{2}$$

$$\text{or, } V_0 = V_2 - V_1$$

$$V_1 \text{ only: } R_i = \frac{V_1}{I} = R$$

$$V_2 \text{ only: } R_i = \frac{V_2}{I} = 2R$$

$$V \text{ between 2 terminals: } R_i = V/I = 2R$$

$$V_1 \text{ connected to both input terminals:}$$

$$I_1 = V_1 / 2R + V_1 / 2R = V_1 / R$$

$$R_i = R$$

Problem 3:

Prove the equation

Problem 4:

$$A_d = 1$$

$$A_{cm} = 0$$

$$-5V \leq V_{cm} \leq 5V$$

$$A_{cm} = 0$$

$$A_d = 10$$

$$-3V \leq V_{cm} \leq 3V$$

Problem 5:



$$R_5 = 756\Omega$$

$$R_6 = 6.8K\Omega$$


Problem 6:

Prove

Problem 7:

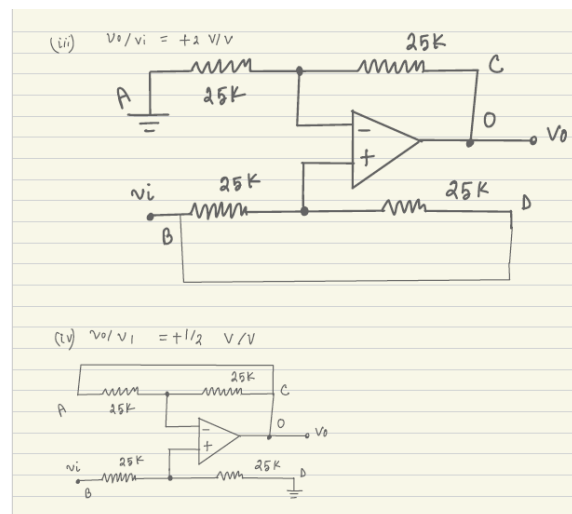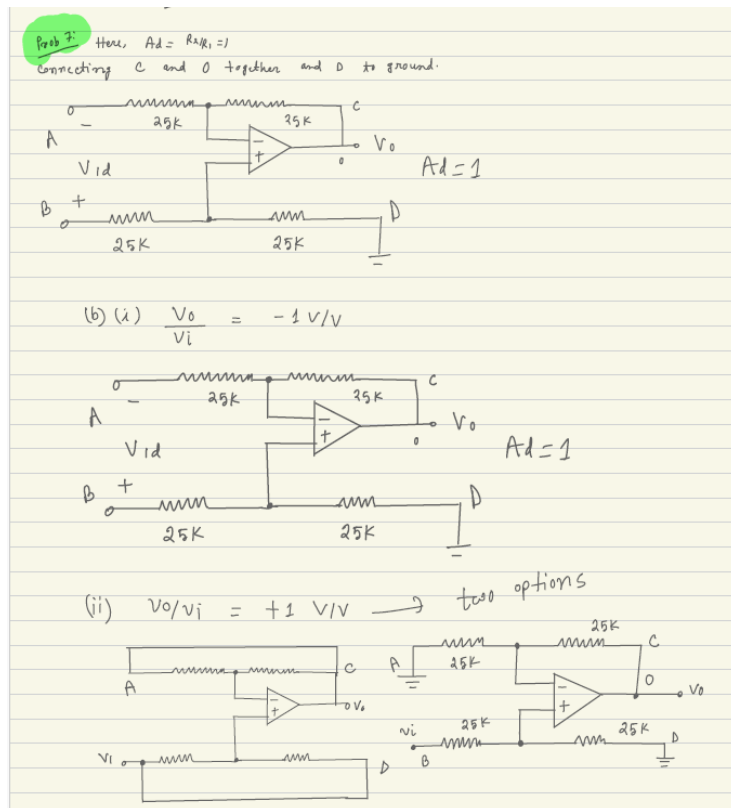

Problem 9:

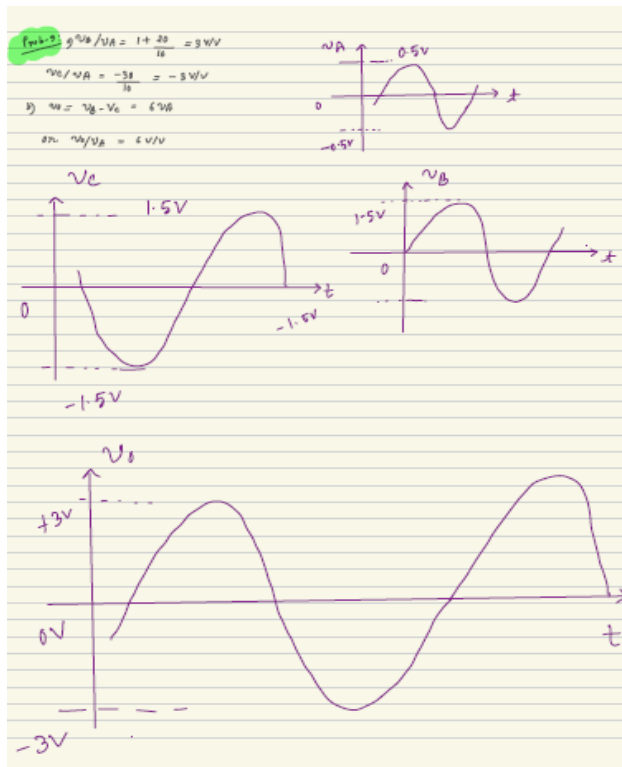

$$-28V \leq V_0 \leq 28V$$

$$56V = V_{p-p}$$

$$V_{r.m.s} = 19.8V$$

Problem 10:

Largest V that can be applied = 14mV

$$V_{rms} = 100mV$$

Problem 11:

$$V_0 = -10V$$

$$V_0 = 4V$$

$$V_p = 40mV$$

$$R_{L_min} = 502 \text{ Ohm}$$

Problem 13:

$$\frac{V_{out}}{V_{in}} = 4.66$$

$$I_{in} = 0A$$

$$R_{in} = \infty$$

$$V = 30V$$

Problem 14:

$$V_{out} = 9.05 \text{ V}$$