





HW 5:



Prob 1:

$$V=2V; I=0.0025A$$

$$V=1V; I=0.001A$$

Prob 2:

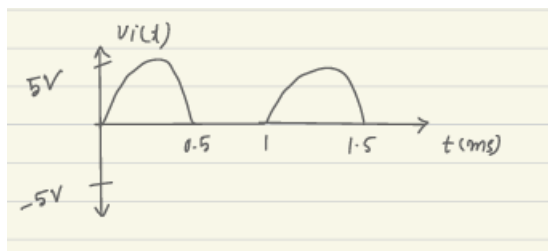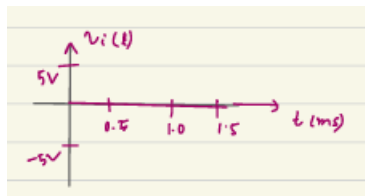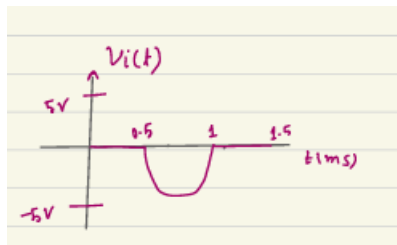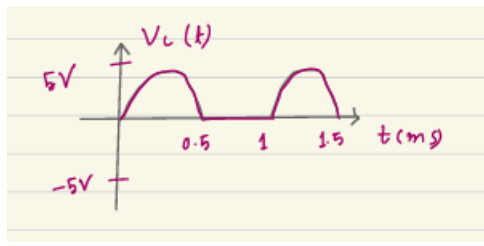

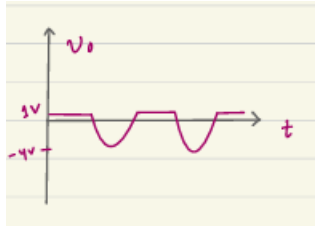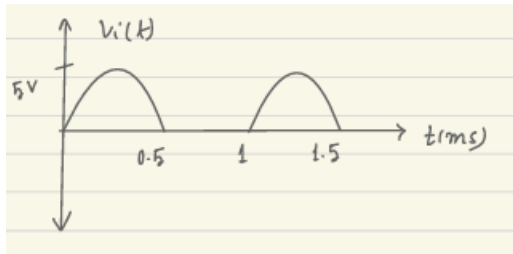

Prob 3:

- a) $V=0V$; $I_{D2}=0.5mA$; $I_{12k}=0.25mA$
- b) $I=0.25mA$; $V=0V$

Prob 4:

- a) $V=1.67V$; $I=0.083mA$
- b) $I=0A$; $V=-1V$

Prob 5:

- a) $V=-2.3V$; $I=0.53mA$
- b) $V=3V$; $I=0A$
- c) $I=0A$; $V=-3V$

Prob 6:

- a) $I_{D2}=0.294mA$; $V=-1.23V$
- b) $V=0V$; $I=0.133mA$

Prob 7:

$V=-1V$; $I=0A$