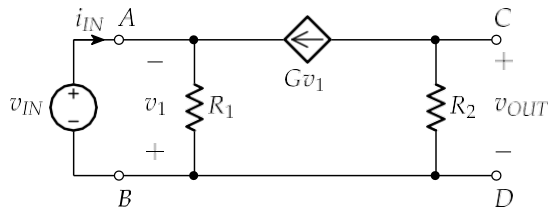



Homework 1

Topic: Amplifier Models


For the following circuits, find the voltage gain and the input and output resistances.




(a)

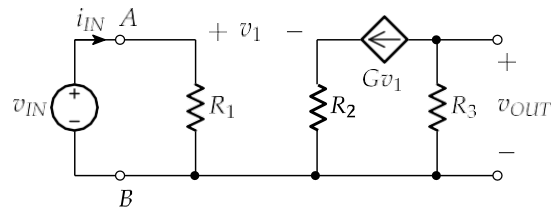


(b)

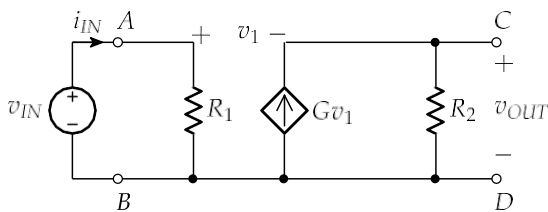


(c)

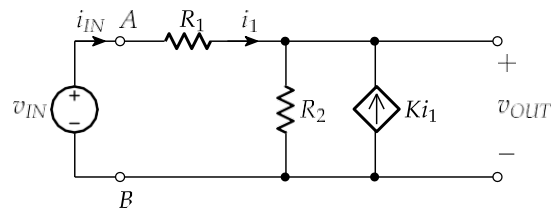


(d)

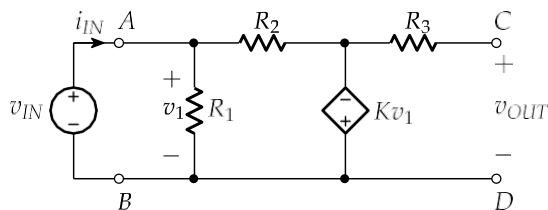


(e)

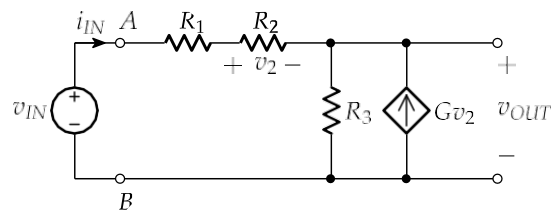


(f)

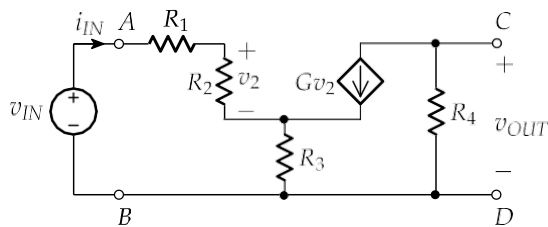


(g)

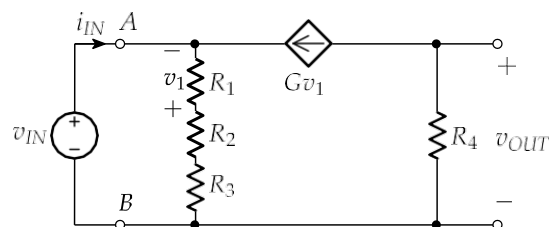

(h)

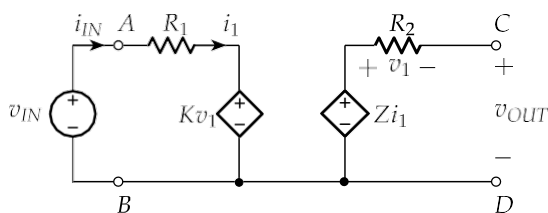

(i)

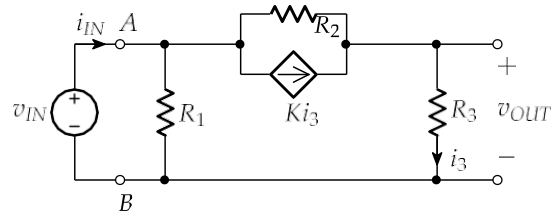

(j)