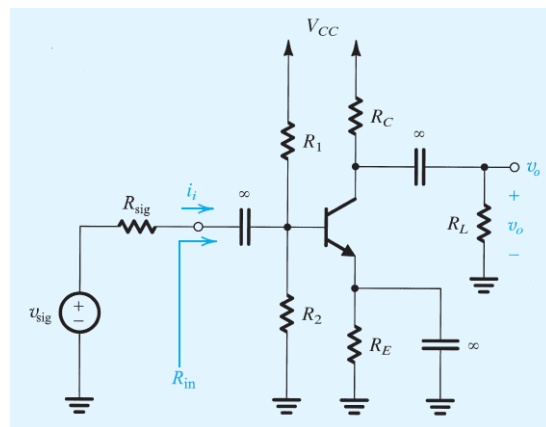



Homework 10

Topic: BJTs Small Signal Analysis


- For the common-emitter amplifier shown below, let $V_{CC}=15\text{ V}$, $R_1=27\text{ k}\Omega$, $R_2=15\text{ k}\Omega$, $R_E=2.4\text{ k}\Omega$, and $R_C=3.9\text{ k}\Omega$. The transistor has $\beta=100$. Calculate the dc bias current I_C . If the amplifier operates between a source for which $R_{sig}=2\text{ k}\Omega$ and a load of $2\text{ k}\Omega$, replace the transistor with its hybrid- π model, and find the values of R_{in} , and the overall voltage gain v_o/v_{sig} .



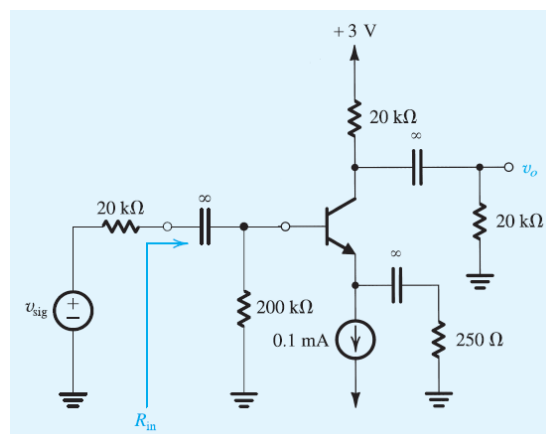
- In the circuit below, the BJT is biased with a constant-current source, and v_{sig} is a small sine-wave signal. Find R_{in} and the gain v_o/v_{sig} . Assume $\beta=100$. If the amplitude of the signal v_{be} is to be limited to 5 mV , what is the largest signal at the input? What is the corresponding signal at the output?



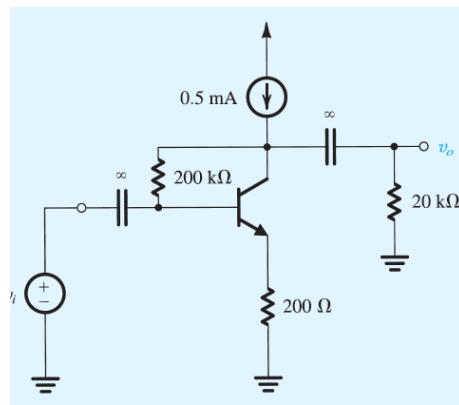
- The BJT in the circuit below has $\beta=100$.
 - Find the dc collector current and the dc voltage at the collector.
 - Replacing the transistor by its π model, draw the small-signal equivalent circuit of the amplifier. Analyze the resulting circuit to determine the voltage gain v_o/v_i .



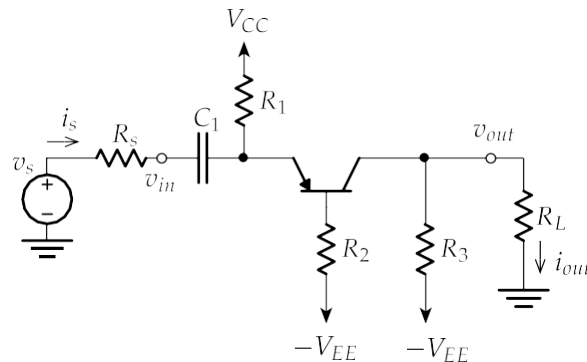
4. For the following circuit, use $R_s = 100 \, \Omega$, $C_1 = 10 \, \mu\text{F}$, $R_1 = 1 \, \text{k}\Omega$, $R_2 = 220 \, \text{k}\Omega$, $R_3 = 1.5 \, \text{k}\Omega$, $R_L = 500 \, \Omega$, $V_{CC} = +15 \, \text{V}$, $-V_{EE} = -15 \, \text{V}$, and $\beta = 100$.
- Confirm that the circuit is in the active mode
 - Draw the small signal model of the circuit
 - Find the amplifier's ac gain (v_{out}/v_{in} with source and load removed)
 - Find the small signal input resistance (with the load attached)
 - Find the small signal output resistance (with the source attached)
 - Sketch the simplified model for the amplifier
 - Find the voltage gain of the circuit (with the source and load attached)
 - Find the current gain of the circuit (with the source and load attached)



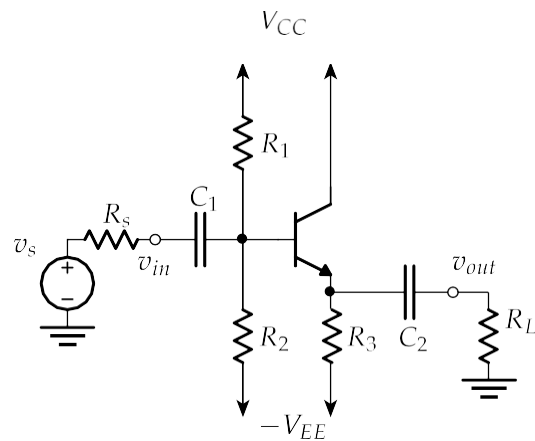
5. For the following circuit, use $R_s = 500 \, \Omega$, $C_1 = 0.1 \, \mu\text{F}$, $C_2 = 1 \, \mu\text{F}$, $R_1 = R_2 = 50 \, \text{k}\Omega$, $R_3 = 1 \, \text{k}\Omega$, and $R_L = 100 \, \Omega$, $V_{CC} = +12 \, \text{V}$, $-V_{EE} = -12 \, \text{V}$, and $\beta = 100$.
- Confirm that the circuit is in the active mode
 - Draw the small signal model of the circuit
 - Find the amplifier's ac gain (v_{out}/v_{in} with source and load removed)
 - Find the small signal input resistance (with the load attached)
 - Find the small signal output resistance (with the source attached)
 - Sketch the simplified model for the amplifier
 - Find the gain of the circuit
 - Sketch the Bode magnitude plot



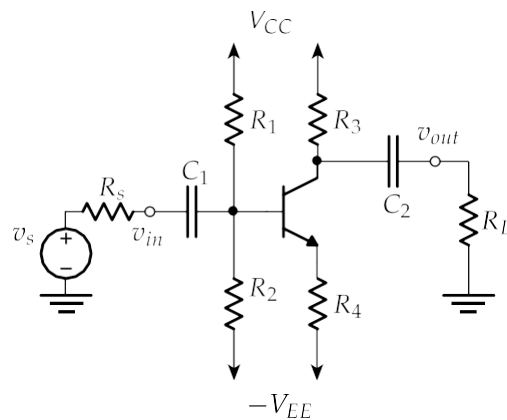6. For the following circuit, use $R_s = 1 \text{ k}\Omega$, $C_1 = C_2 = 1 \mu\text{F}$, $R_1 = 4.7 \text{ k}\Omega$, $R_2 = 2.2 \text{ k}\Omega$, $R_3 = 1 \text{ k}\Omega$, $R_4 = 1 \text{ k}\Omega$, $R_L = 500 \Omega$, $V_{CC} = +15 \text{ V}$, $-V_{EE} = -15 \text{ V}$, and $\beta = 100$.
- Confirm that the circuit is in the active mode
 - Draw the small signal model of the circuit
 - Find the amplifier's ac gain (v_{out}/v_{in} with source and load removed)
 - Find the small signal input resistance (with the load attached)
 - Find the small signal output resistance (with the source attached)
 - Find the gain of the circuit
 - Using the simplified amplifier model, sketch the Bode magnitude plot



7. Solve the following problem.

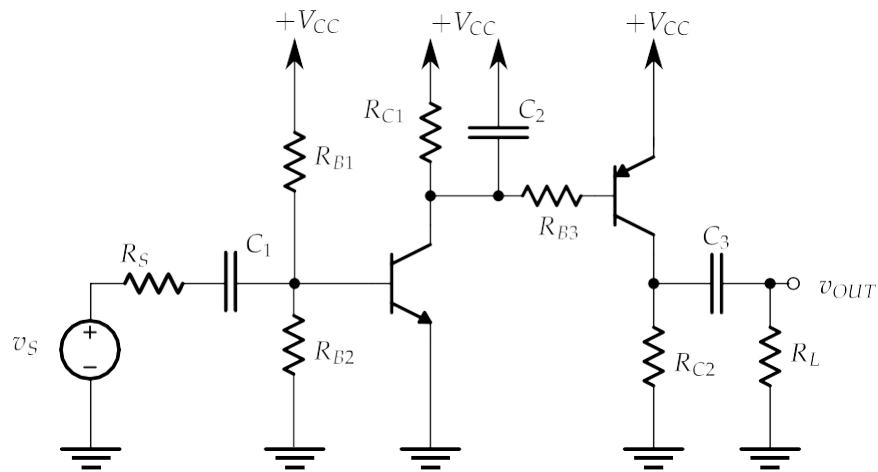

- Complete a DC analysis to find the values of the small signal model and ensure that the transistor is in an active mode using $V_{CC} = 20\text{ V}$, $R_S = 10\ \Omega$, $R_{B1} = R_{B2} = R_{B3} = 100\text{ k}\Omega$, $R_{C1} = 540\ \Omega$, $R_{C2} = 1075\ \Omega$, $R_L = 1000\ \Omega$, $C_1 = 75\ \mu\text{F}$, $C_2 = 186\text{ nF}$, $C_3 = 48\ \mu\text{F}$, and $\beta = 100$. Use the DC analysis to compute the parameters for the small signal analysis.
- Write an expression (no values!) for the *midband* gain, v_{out}/v_{in} , with the source and load removed. Note that v_{in} is the node between R_S and C_1 .
- Find the input and output resistances.
- Estimate the RC time constants for each of the stages of the amplifier.
- Sketch the Bode magnitude plot for the circuit.