

HW 8:

Prob 1:

$$V_{dc} = 10.74V$$

$$\Delta t = 23.5mS$$

$$\underline{I_d^{\max} = 4.915A}$$

Prob 2:

$$V_{z0} = 11.4V$$

$$V_z = 12.15V$$

$$R = 421.04\Omega$$

$$\underline{Line_Regulation = 0.064V / V}$$


Prob 3:

$$a) \quad V_{out} = \frac{V_{IN} - 0.7}{2}$$

Prob 4:

$$V_{out} = \frac{V_{IN} - 0.7}{3}$$

Prob 5:

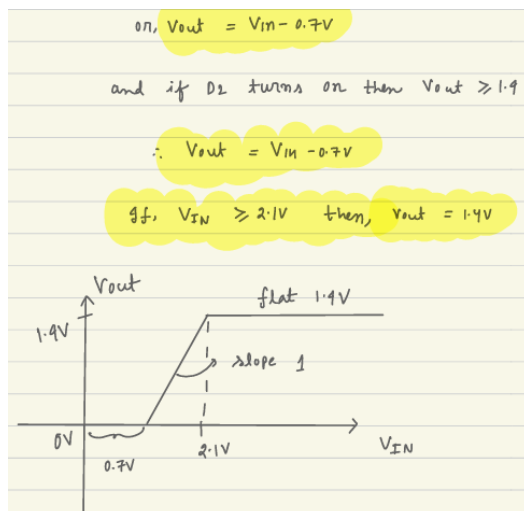

Prob 6:

a)	$I_E = I_B + I_C = 1.01 \text{ mA}$	e)	$I_C = 73.95 \text{ mA}$
	$\alpha = I_C / I_E = 0.99$		$\alpha = 0.986$
	$\beta = I_E / I_B = 100$		$\beta = 70.429$
	$I_S = I_C / e^{V_{BE}/V_T} = 6.91 \times 10^{-16} \text{ A}$		$I_S = 4.208 \times 10^{-16} \text{ A}$
b)	$I_E = I_B + I_C = 2.0 \text{ mA}$		
	$\alpha = I_C / I_E = 0.98$		
	$\beta = I_E / I_B = 50$		
	$I_S = I_C / e^{V_{BE}/V_T} = 1.031 \times 10^{-15} \text{ A}$		
c)	$I_E = I_B + I_C = 0.13 \text{ mA}$		
	$\alpha = I_C / I_E = 0.978$		
	$\beta = I_E / I_B = 46$		
	$I_S = I_C / e^{V_{BE}/V_T} = 19.32 \times 10^{-15} \text{ A}$		
d)	$I_E = I_B + I_C = 10.120 \text{ mA}$		
	$\alpha = I_C / I_E = 0.988$		
	$\beta = I_E / I_B = 84.167$		
	$I_S = I_C / e^{V_{BE}/V_T} = 2.847 \times 10^{-16} \text{ A}$		

Prob 7:

- a) $I_1 = 2 \text{ mA}$
 $V_2 = 0.7 \text{ V}$
- b) $V_3 = -2 \text{ V}$
- c) $I_5 = 0.5 \text{ mA}$
- d) $I_6 = 1.59 \text{ mA}$