

ECE 3355: Electronics

Exam 3

Complete the exam on your own, without the help of your notes, prior examples or solutions, your book, or any communication/interaction with others. You must write a complete solution that shows the relevant steps if you want full credit for the problem. You may use a calculator and a crib sheet is provided as part of this exam. **You will have 1 hr. 15 min. to finish the exam.**

Student's Name: _____

Question	Points	Score
1	45	
2	55	
Total:	100	

$$i_C = I_S e^{v_{BE}/V_T}$$

$$i_B = \frac{i_C}{\beta} = \left(\frac{I_S}{\beta} \right) e^{v_{BE}/V_T}$$

$$i_E = \frac{i_C}{\alpha} = \left(\frac{I_S}{\alpha} \right) e^{v_{BE}/V_T}$$

Note: For the pnp transistor, replace v_{BE} with v_{EB} .

$$i_C = \alpha i_E$$

$$i_C = \beta i_B$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$i_B = (1 - \alpha) i_E = \frac{i_E}{\beta + 1}$$

$$i_E = (\beta + 1) i_B$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$V_T = \text{thermal voltage} = \frac{kT}{q} \simeq 25 \text{ mV}$ at room temperature

Summary of Table 7.3 (Small Signal Model Parameters)

Model Parameters in Terms of DC Bias Currents

$$g_m = \frac{I_C}{V_T} \quad r_e = \frac{V_T}{I_E} = \alpha \frac{V_T}{I_C} \quad r_\pi = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} \quad r_o = \frac{|V_A|}{I_C}$$


In Terms of g_m

$$r_e = \frac{\alpha}{g_m} \quad r_\pi = \frac{\beta}{g_m}$$

In Terms of r_e

$$g_m = \frac{\alpha}{r_e} \quad r_\pi = (\beta + 1) r_e \quad g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$$

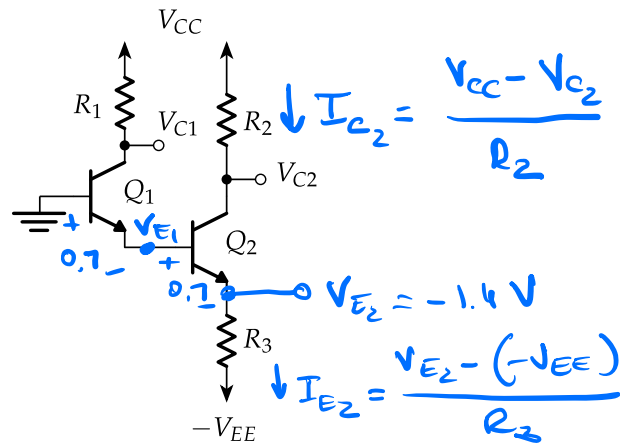1. Consider the following circuit where $R_1 = 10 \text{ k}\Omega$, $R_3 = 300 \Omega$, $V_{CC} = 14 \text{ V}$, $-V_{EE} = -14 \text{ V}$ and $\beta = 99$.



- (a) (15 points) Find R_2 so that $V_{C2} = 1 \text{ V}$. Is Q_2 in an 'active' state?

$$I_{E2} = \frac{-1.4 + 14}{300} = 42 \text{ mA}, \quad I_{C2} = \frac{\beta}{\beta + 1} I_{E2} = \frac{99}{100} \cdot 42 \text{ mA} = 41.58 \text{ mA}$$

$$R_2 = \frac{V_{CC} - V_{C2}}{I_{C2}} = \frac{14 - 1}{41.58 \text{ mA}} = 312.65 \Omega$$

$$V_{C2} - V_{E2} = 1 - (-1.4) = 2.4 > 0.2 \rightarrow \underline{\text{active}}$$

- (b) (15 points) Find V_{C1} . Is Q_1 in an 'active' state?

$$I_{E1} = I_{B1} = \frac{I_{E2}}{\beta + 1} = \frac{42 \text{ mA}}{100} = 0.42 \text{ mA}$$

$$I_{C1} = \frac{\beta}{\beta + 1} I_{E1} = \frac{99}{100} \cdot 0.42 \text{ mA} = 0.4158 \text{ mA}$$

$$V_{C1} = V_{CC} - I_{C1} \cdot R_1 = 14 - 0.4158 \text{ mA} \cdot 10 \text{ k}\Omega$$

$$= 14 - 4.158 = 9.842 \text{ V}$$

$$V_{C1} - V_{E1} = 9.842 - (-0.7) > 0.2 \text{ V} \rightarrow \underline{\text{active}}$$

(c) (15 points) What values of R_2 ensure that Q2 is in an 'active' state?

$$V_{C_2} - V_{E_2} > 0.2 \text{ V}$$


$$V_{CC} - I_{C_2} R_2 - V_{E_2} > 0.2$$

$$V_{CC} - 0.2 - V_{E_2} > I_{C_2} R_2$$


$$R_2 < \frac{V_{CC} - 0.2 - V_{E_2}}{I_{C_2}} = \frac{14 - 0.2 - (-1.4)}{41.58 \mu\text{A}}$$

$$R_2 < 365.6 \, \Omega$$

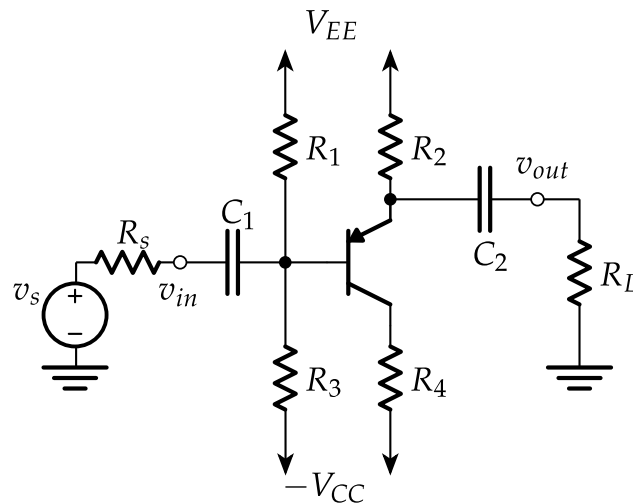3. Use the following circuit to complete this problem.




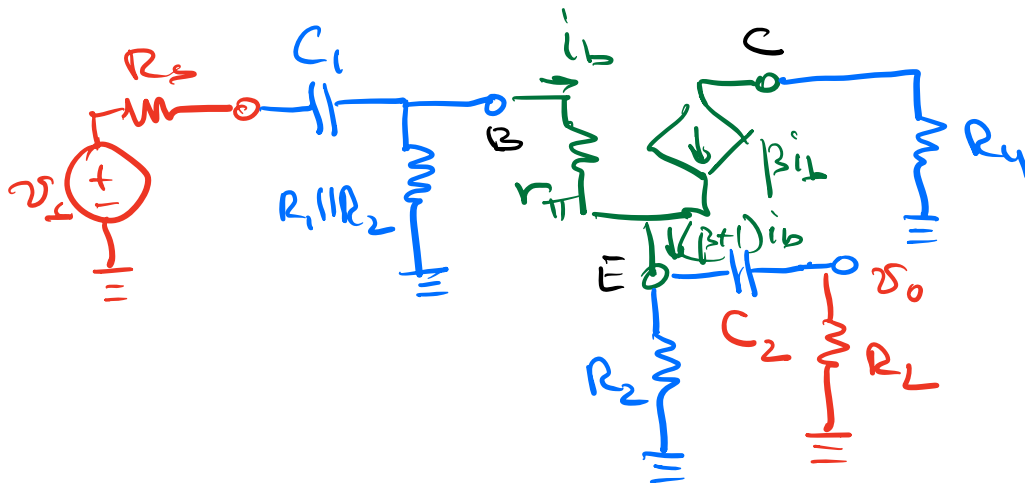- (a) (5 points) Assuming that the transistor is in an active mode, sketch the small signal model for the circuit. *Hint:* You do not need to complete a DC analysis - just the AC analysis.



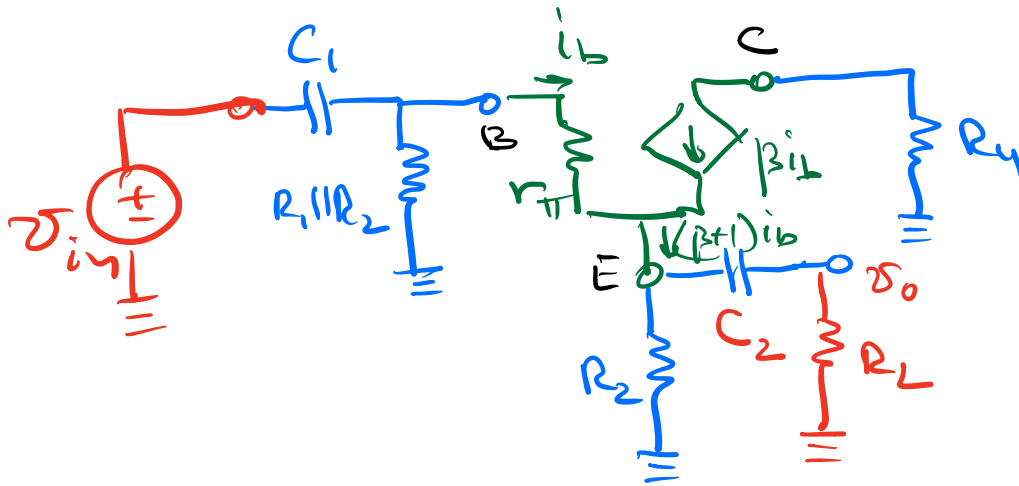- (b) (10 points) Find the expression for the *midband gain*, A , with the load and source removed. The solution should be expressed in terms of resistors, β , r_π .

$$A = \frac{v_o}{v_{in}} = \frac{R_2(\beta+1)i_b}{r_\pi i_b + (\beta+1)i_b R_2} = \frac{R_2(\beta+1)}{r_\pi + (\beta+1)R_2}$$



(c) (10 points) Find expression for the input resistance, R_{in} , for the *midband*.


Hint: attach the load.

$$R_{in} = \frac{v_{in}}{i_{in}} = R_1 \parallel R_2 \parallel \frac{r_{\pi} i_b + (\beta + 1) i_b (R_2 \parallel R_L)}{i_b}$$

$$= R_1 \parallel R_2 \parallel (r_{\pi} + (\beta + 1)(R_2 \parallel R_L))$$


(d) (10 points) Find expression for the output resistance, R_{out} , for the *midband*.

Hint: attach the source.

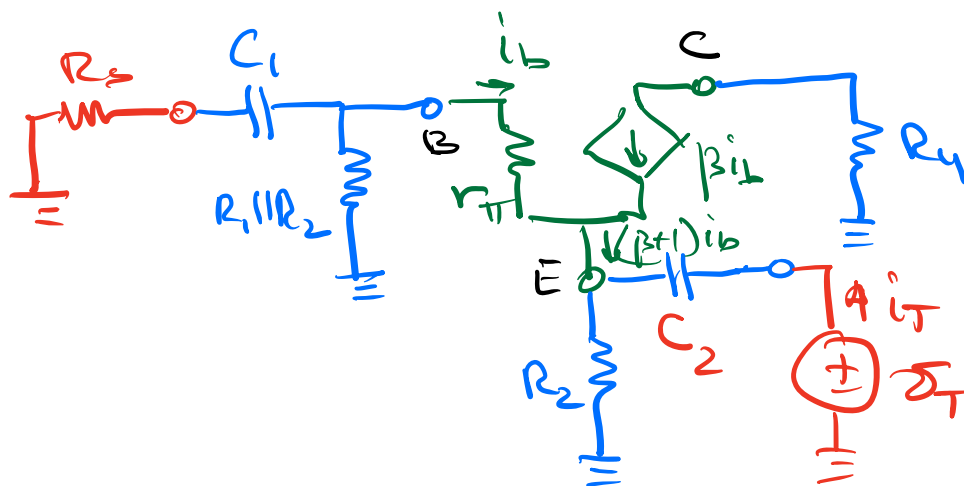

$$R_o = R_2 \parallel \frac{-r_{\pi} i_b - i_b (R_1 \parallel R_2 \parallel R_S)}{-(\beta + 1) i_b} = R_2 \parallel \frac{r_{\pi} + R_1 \parallel R_2 \parallel R_S}{\beta + 1}$$

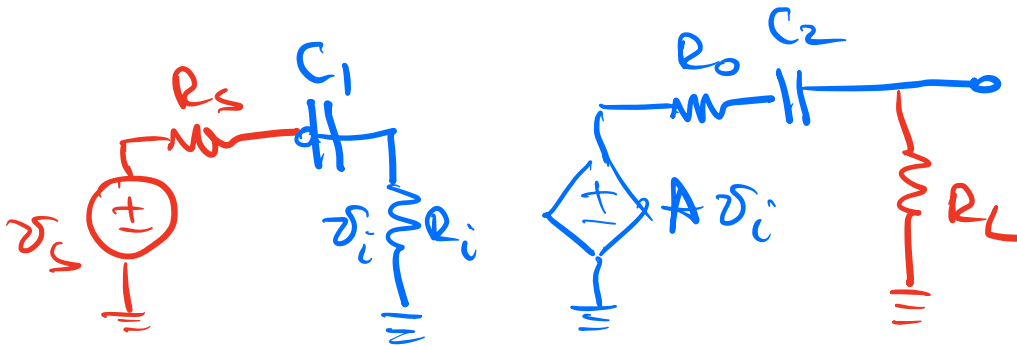
(e) (10 points) Draw the equivalent circuit of the amplifier using the parameters identified above (R_{in} , R_{out} , and A) with the source and load attached. Find expressions for resistances R_{C1} and R_{C2} as seen by capacitors C_1 and C_2 , respectively.



$$R_{C1} = R_s + R_i$$

$$R_{C2} = R_o + R_L$$

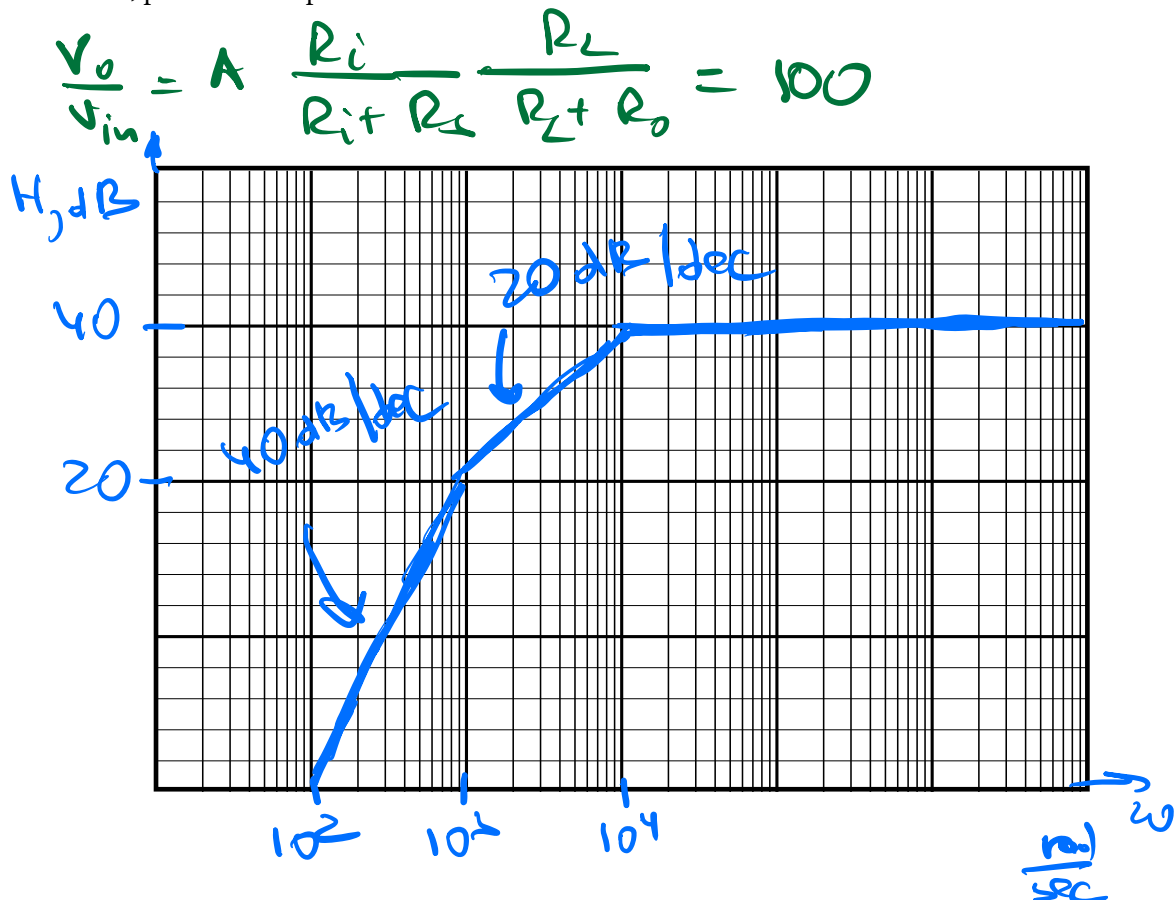(f) (10 points) Assuming $R_{in} = 5k$, $R_{out} = 5k$, $R_S = 5k$, $R_L = 5k$, $C_1 = 10nF$, $C_2 = 0.1\mu F$, and midband gain $A=400$, plot the Bode plot of the transfer function for the circuit. Make sure to label the axes.



$$P_1 = 10^4$$

$$P_2 = 10^3$$

