

ECE 3355: Electronics

Exam 3

Complete the exam on your own, without the help of your notes, prior examples or solutions, your book, or any communication/interaction with others. You must write a complete solution that shows the relevant steps if you want full credit for the problem. You may use a calculator and a crib sheet is provided as part of this exam. **You will have 1 hr. 15 min. to finish the exam.**

Student's Name: _____

Question	Points	Score
1	45	
2	55	
Total:	100	

$$i_C = I_S e^{v_{BE}/V_T}$$

$$i_B = \frac{i_C}{\beta} = \left(\frac{I_S}{\beta} \right) e^{v_{BE}/V_T}$$

$$i_E = \frac{i_C}{\alpha} = \left(\frac{I_S}{\alpha} \right) e^{v_{BE}/V_T}$$

Note: For the pnp transistor, replace v_{BE} with v_{EB} .

$$i_C = \alpha i_E$$

$$i_C = \beta i_B$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$i_B = (1 - \alpha) i_E = \frac{i_E}{\beta + 1}$$

$$i_E = (\beta + 1) i_B$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$V_T = \text{thermal voltage} = \frac{kT}{q} \simeq 25 \text{ mV}$ at room temperature

Summary of Table 7.3 (Small Signal Model Parameters)

Model Parameters in Terms of DC Bias Currents

$$g_m = \frac{I_C}{V_T} \quad r_e = \frac{V_T}{I_E} = \alpha \frac{V_T}{I_C} \quad r_\pi = \frac{V_T}{I_B} = \beta \frac{V_T}{I_C} \quad r_o = \frac{|V_A|}{I_C}$$


In Terms of g_m

$$r_e = \frac{\alpha}{g_m} \quad r_\pi = \frac{\beta}{g_m}$$

In Terms of r_e

$$g_m = \frac{\alpha}{r_e} \quad r_\pi = (\beta + 1) r_e \quad g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$$

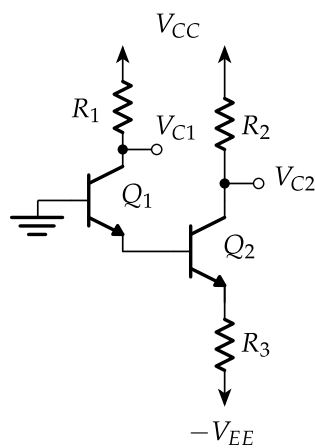1. Consider the following circuit where $R_1 = 10\text{ k}\Omega$, $R_3 = 300\text{ }\Omega$, $V_{CC} = 14\text{ V}$, $-V_{EE} = -14\text{ V}$ and $\beta = 99$.




(a) (15 points) Find R_2 so that $V_{C2} = 1\text{ V}$. Is Q2 in an 'active' state?

(b) (15 points) Find V_{C1} . Is Q1 in an 'active' state?

(c) (15 points) What values of R_2 ensure that Q2 is in an 'active' state?

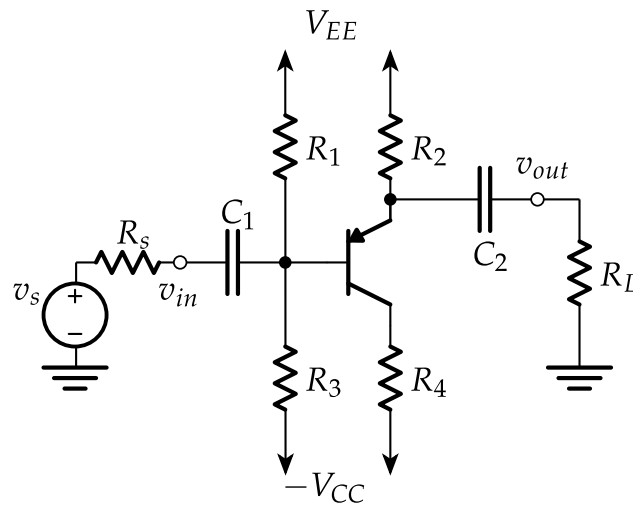3. Use the following circuit to complete this problem.



- (a) (5 points) Assuming that the transistor is in an active mode, sketch the small signal model for the circuit. *Hint:* You do not need to complete a DC analysis - just the AC analysis.
- (b) (10 points) Find the expression for the *midband gain*, A , with the load and source removed. The solution should be expressed in terms of resistors, β , r_π .

- (c) (10 points) Find expression for the input resistance, R_{in} , for the *midband*.
Hint: attach the load.

- (d) (10 points) Find expression for the output resistance, R_{out} , for the *midband*.
Hint: attach the source.

(e) (10 points) Draw the equivalent circuit of the amplifier using the parameters identified above (R_{in} , R_{out} , and A) with the source and load attached. Find expressions for resistances R_{C1} and R_{C2} as seen by capacitors C_1 and C_2 , respectively.

(f) (10 points) Assuming $R_{in} = 5k$, $R_{out} = 5k$, $R_S = 5k$, $R_L = 5k$, $C_1 = 10nF$, $C_2 = 0.1\mu F$, and midband gain $A=400$, plot the Bode plot of the transfer function for the circuit. Make sure to label the axes.

