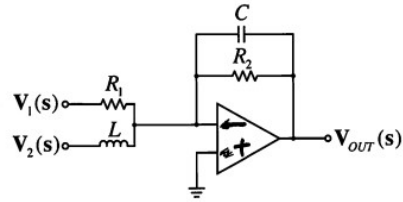
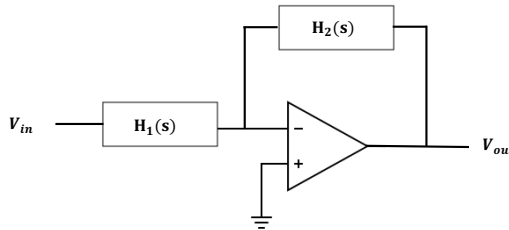


1. (40 points) For the following operational amplifier circuits:



- (5 points) Indicate whether or not each circuit has dc negative feedback. If not directly clear, indicate the conditions that will guarantee dc negative feedback.
 - (10 points) determine the voltages and currents at the op-amp inputs
 - (10 points) Determine the transfer function $\mathbf{H(s)} = \frac{\mathbf{V_o(s)}}{\mathbf{V_i(s)}}$.
 - (15 points) For the input signal $v_i(t) = te^{-t} \sin(t) u(t)$ and $R, L, C = 1$, calculate the s-domain output $V_o(s)$ for the second circuit.
2. (30 points) By combining the basic circuits in Table 4-3 of your textbook, devise an op-amp circuit that performs the following signal calculation:

$$y(t) = x_1(t) - x_2(t) \frac{dx_2(t)}{dt} + \int_{0-}^t x_3(\tau) d\tau$$

2. (30 points) Determine the overall impulse response function $h(t)$ relating the output $y(t)$ to the input $x(t)$ for the following feedback system if
- $$h_1(t) = te^{-2t}u(t)$$
- $$h_2(t) = e^{-5t}u(t)$$

