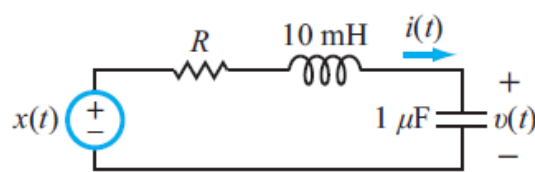


- (20 points) Draw a minimal op-amp circuit that realizes the following transfer function:


$$H(s) = \frac{3s^2 + 4s + 7}{s^2 + 6s + 9}$$

- (30 points) Write down the phasor representation for each of the following signals:
 - (5 pts) $x_1(t) = 4\sin(3t)$
 - (5 pts) $x_2(t) = 3\sin(2t - 60)$
 - (5 pts) $x_3(t) = 4\cos(3t + 30)$
 - (5 pts) $x_3(t) = \sin(5t) + 4\cos(2t + 45)$
 - (10 pts) $\frac{d(\sin(5t) + 4\cos(2t + 45))}{dt}$ Please also express the result in the time domain.
 - (10 pts) $\int_{0-}^t \sin(5\tau) + 4\cos(2\tau + 45) d\tau$. Please also express the result in the time domain.
- (20 points) Given two phasor voltages $V_1 = e^{-j60}$, and $V_2 = e^{j30}$, calculate the following quantities:
 - $V_1 + V_2$
 - $V_1 - V_2$
 - $V_1 V_2$
 - $\frac{V_1}{V_2}$
- (30 points) calculate the first 3 terms of the output voltage, at $(\omega_0, 3\omega_0, 5\omega_0)$ for the following RC circuit ($RC = 1$) when the input shown below is applied:

Input



Output

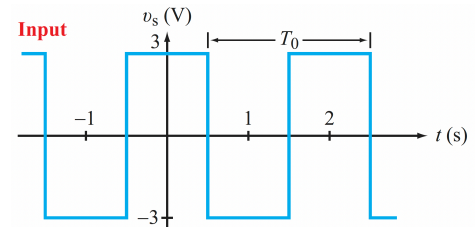

Use the Fourier series expansion in equation 5.13 of the textbook:

$$v_s(t) = \frac{12}{\pi} \left(\cos \omega_0 t - \frac{1}{3} \cos 3\omega_0 t + \frac{1}{5} \cos 5\omega_0 t - \dots \right), \quad (5.13)$$