

6.40 Determine $i_L(t)$ in the circuit of Fig. P6.40 and plot its waveform for $t \geq 0$.


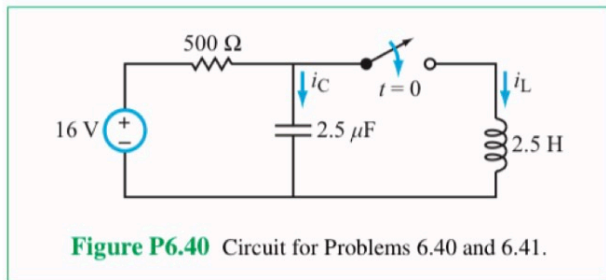



Figure P6.40 Circuit for Problems 6.40 and 6.41.
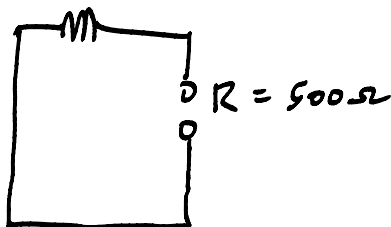
$$\alpha = \frac{1}{2RC} = \frac{1}{2(500)(2.5 \times 10^{-6})} = 400 \text{ s}^{-1}$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = 400 \text{ rad/s}$$


$$i_L(0^-) \quad t = 0^-$$

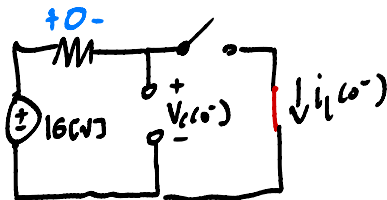

$$V_C(0^-) = 16 \text{ V}$$

$$i_L(0^-) = 0$$

$$V_C(0^+) \quad t = 0^+$$

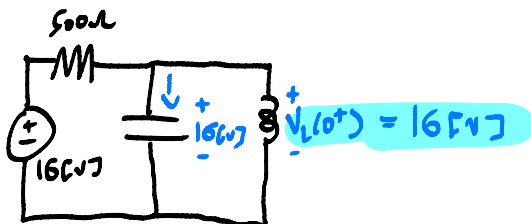


$$\alpha = \omega_0$$

Critically Damped

Table 6-1: Step response of RLC circuits for $t \geq 0$.	
Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$	Input: dc circuit with switch action at $t = 0$
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{\frac{1}{C} [i_C(0) - s_2 [v_C(0) - v_C(\infty)]]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{C} [i_C(0) - s_1 [v_C(0) - v_C(\infty)]]}{s_2 - s_1}$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{\frac{1}{L} [v_L(0) - s_2 [i_L(0) - i_L(\infty)]]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{L} [v_L(0) - s_1 [i_L(0) - i_L(\infty)]]}{s_2 - s_1}$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = i_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} [i_C(0) + \alpha [v_C(0) - v_C(\infty)]]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} [D_1 \cos \omega_d t + D_2 \sin \omega_d t] + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{\frac{1}{C} [i_C(0) + \alpha [v_C(0) - v_C(\infty)]]}{\omega_d}$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} [D_1 \cos \omega_d t + D_2 \sin \omega_d t] + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{\frac{1}{L} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]}{\omega_d}$
Auxiliary Relations $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$ $s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$	

$$t = \infty \cdot i_L(\infty)$$

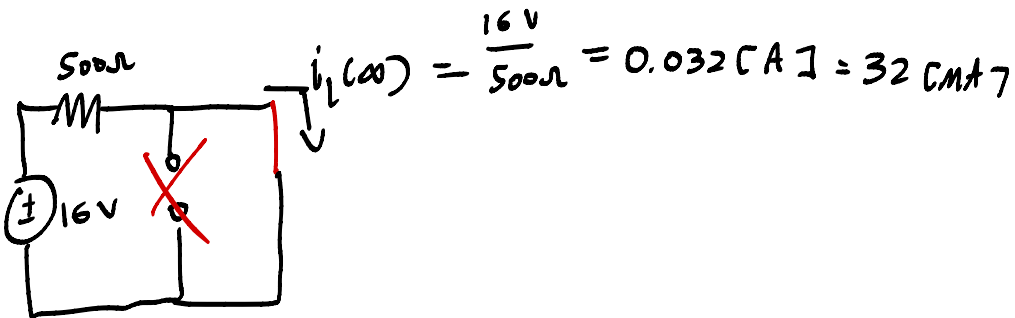

$$B_1 = i_L(0^+) - i_L(\infty) = 0 - 32[mA] = -32[mA]$$

$$B_2 = \frac{1}{L} V_L(0^+) + \alpha (i_L(0^+) - i_L(\infty)) = \frac{16[V]}{2.5[H]} + 400(-32[mA]) = -6.4\left[\frac{A}{s}\right]$$

$$i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$$

$$= (-32[mA] - 6.4\left[\frac{A}{s}\right]) e^{-400[s^{-1}]t} + 32[mA] \quad t \geq 0$$


$$i_L(t) = x(t)$$

$$x'(t) = i_L'(t)$$


$$V_L(t) = L i_L'(t)$$

$$i_L'(t) = \frac{V_L(t)}{L} = \frac{1}{L} V_L(0)$$

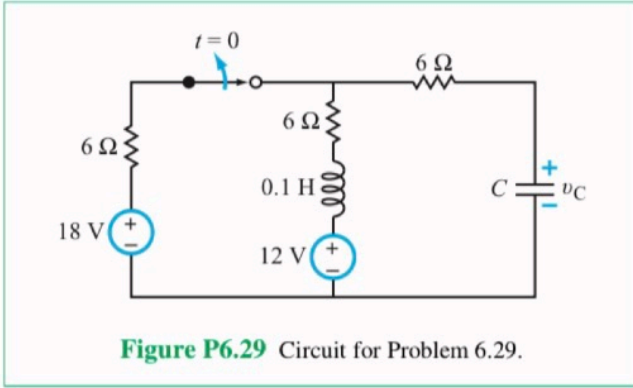*6.29 Choose the value of C in the circuit of Fig. P6.29 so that $v_C(t)$ has a critically damped response for $t \geq 0$. Plot the waveform of $v_C(t)$.



$$\alpha = \frac{R}{2L}$$

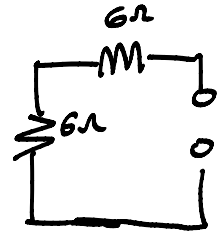

$$R = 12\Omega$$

$$\alpha = \frac{12}{2(0.1)} = 60 \text{ s}^{-1}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\left(\frac{1}{\sqrt{LC}} = 60 \text{ s}^{-1} \right)^2$$

$$\Rightarrow \frac{1}{LC} = 60^2$$

$$C = \frac{1}{L \cdot 60^2} \approx 2.78 \text{ mF}$$

$$t = 0^- \cdot v_C(0^-)$$

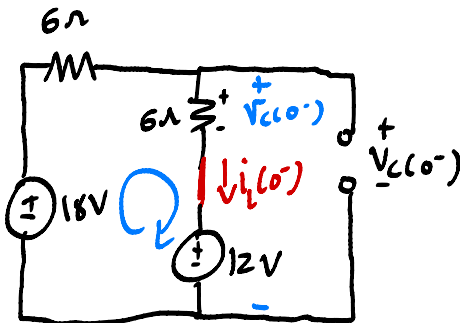

$$\text{KVL}$$


$$-18 \text{ V} + 6\Omega \cdot i_L(0^-) + 6\Omega \cdot i_L(0^-) + 12 \text{ V} = 0$$

$$\Rightarrow 12\Omega i_L(0^-) = 6 \text{ V}$$


$$i_L(0^-) = 0.5 \text{ A}$$

$$V_L(0^-) = 6\Omega \cdot 0.5\text{CA} + 12\text{CV} = 15\text{CV}$$

$$t = 0^+ \cdot i_L(0^+)$$

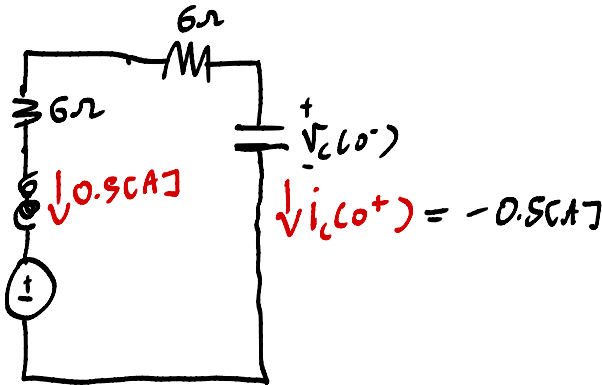

$$t = \infty$$

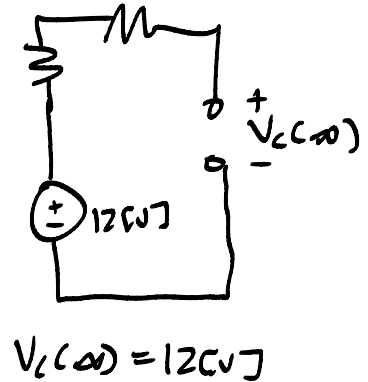

$$B_1 = 15 - 12 = 3\text{CV}$$

$$B_2 = \frac{1}{L} i_L(0^+) \times (B_1) = \frac{1}{2.74 \times 10^{-3}} \cdot (-0.5) + 60(3)$$

$$-180 + 180 = 0$$

$$V_L(t) = 3\text{CV} e^{-60 \times 10^3 t} + 12\text{CV} \quad t \geq 0$$

* 6.46 In the circuit in Fig. P6.46, $v_s = 20$ V.

(a) Determine $i_L(t)$ for $t \geq 0$.

(b) If the source is changed to $v_s(t) = e^{-2t} u(t)$, can you still use the solution method in part (a) to find $i_L(t)$? If not, why not?

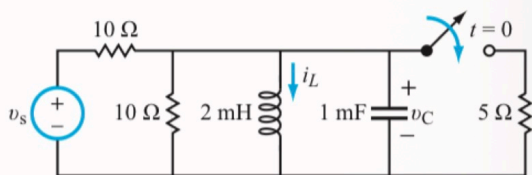



Figure P6.46 Circuit for Problem 6.46.

$$\alpha = \frac{1}{2RC} = \frac{1}{2(2.5)(10^{-3})}$$


$$= 200 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 707.1 \left[\frac{\text{rad}}{\text{s}} \right]$$

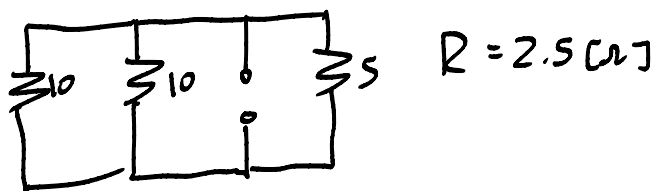
$$\omega_d = \sqrt{707^2 - 200^2} = 678 \left[\frac{\text{rad}}{\text{s}} \right]$$



$$t = 0^- \cdot i_L(0^-)$$

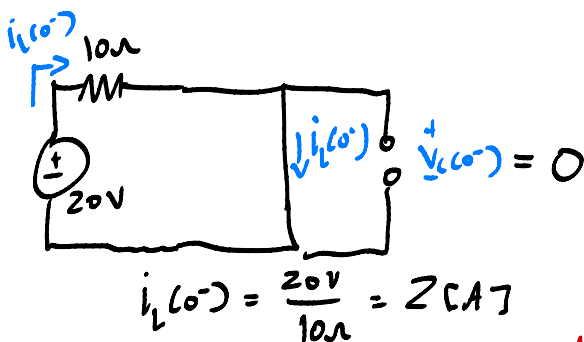

$$t = 0^+$$

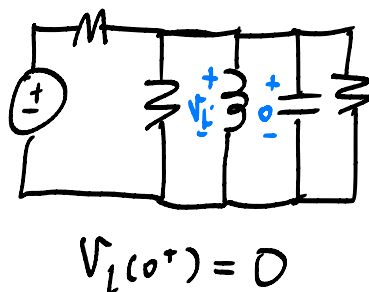

$$t = \infty$$

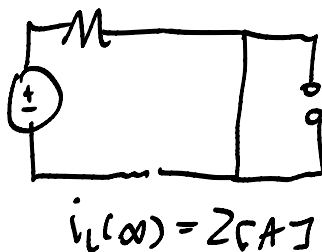
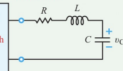
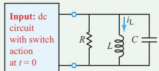


Table 6-1: Step response of RLC circuits for $t \geq 0$.

Series RLC	Parallel RLC
Input: dc circuit with switch action at $t = 0$ 	Input: dc circuit with switch action at $t = 0$ 
Total Response	Total Response
Overdamped ($\alpha > \omega_0$) $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ $A_1 = \frac{\frac{1}{C} [v_C(0) - s_2 [v_C(0) - v_C(\infty)]]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{C} [v_C(0) - s_1 [v_C(0) - v_C(\infty)]]}{s_2 - s_1}$	Overdamped ($\alpha > \omega_0$) $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)$ $A_1 = \frac{\frac{1}{L} [i_L(0) - s_2 [i_L(0) - i_L(\infty)]]}{s_1 - s_2}$ $A_2 = \frac{\frac{1}{L} [i_L(0) - s_1 [i_L(0) - i_L(\infty)]]}{s_2 - s_1}$
Critically Damped ($\alpha = \omega_0$) $v_C(t) = (B_1 + B_2 t) e^{-\alpha t} + v_C(\infty)$ $B_1 = v_C(0) - v_C(\infty)$ $B_2 = \frac{1}{C} [v_C(0) + \alpha [v_C(0) - v_C(\infty)]]$	Critically Damped ($\alpha = \omega_0$) $i_L(t) = (B_1 + B_2 t) e^{-\alpha t} + i_L(\infty)$ $B_1 = i_L(0) - i_L(\infty)$ $B_2 = \frac{1}{L} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]$
Underdamped ($\alpha < \omega_0$) $v_C(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + v_C(\infty)$ $D_1 = v_C(0) - v_C(\infty)$ $D_2 = \frac{\frac{1}{C} [v_C(0) + \alpha [v_C(0) - v_C(\infty)]]}{\omega_d}$	Underdamped ($\alpha < \omega_0$) $i_L(t) = e^{-\alpha t} (D_1 \cos \omega_d t + D_2 \sin \omega_d t) + i_L(\infty)$ $D_1 = i_L(0) - i_L(\infty)$ $D_2 = \frac{\frac{1}{L} [v_L(0) + \alpha [i_L(0) - i_L(\infty)]]}{\omega_d}$
Auxiliary Relations $\alpha = \begin{cases} \frac{R}{2L} & \text{Series RLC} \\ \frac{1}{2RC} & \text{Parallel RLC} \end{cases}$ $\omega_0 = \frac{1}{\sqrt{LC}}$ $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ $s_1 = -\alpha + j\sqrt{\alpha^2 - \omega_0^2}$ $s_2 = -\alpha - j\sqrt{\alpha^2 - \omega_0^2}$	

$$D_1 = 0$$

$$D_2 = \frac{\frac{1}{L} \cdot 0 + \alpha (0)}{678} = 0$$

$$i_L(t) = e^{-200t} (0 + 0) + 2[A]$$

$$i_L(t) = 2[A] \quad t \geq 0$$