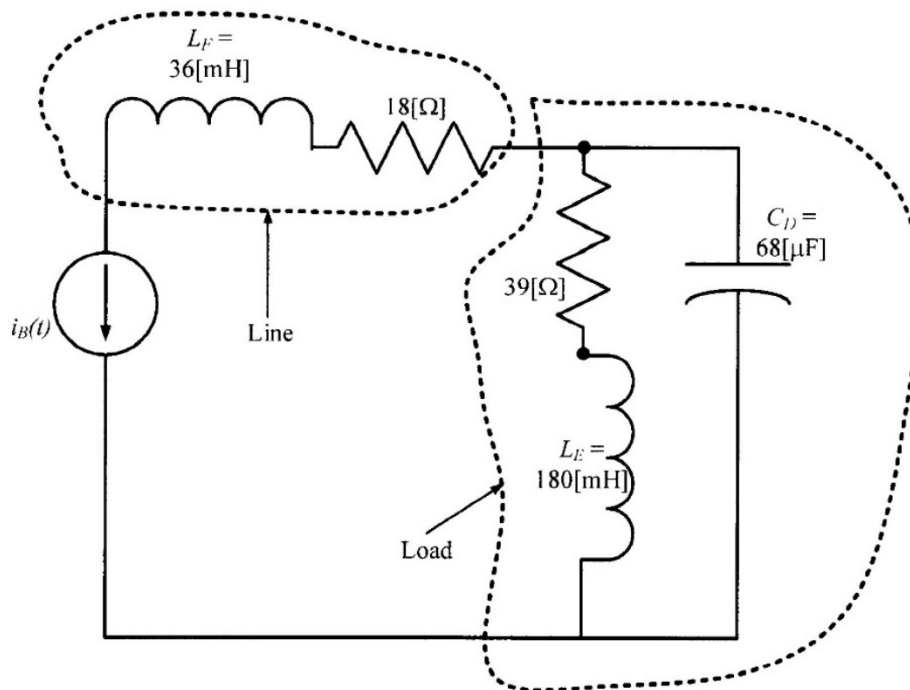


3. {30 Points} The circuit shown below operates in steady state.

- Find the real power absorbed by the load.
- Find the reactive power delivered by the load.
- Find the complex power absorbed by the load.
- Find the power factor for the load, including whether it is leading or lagging.
- Find the susceptance of the line.

$$i_B(t) = 530[\text{A}] \cos\left(420\left[\frac{\text{rad}}{\text{s}}\right]t - 38^\circ\right)$$



$$Z_{\text{LOAD}} = \frac{(39 + 75.6j)(-35.014j)}{39 + (75.6 - 35.014j)} \{\Omega\} = (52.917 \angle -73.43^\circ) \{\Omega\}$$

$$Z_{\text{LOAD}} = (15.091 - 50.719j) \{\Omega\}$$

See next page

$$|\bar{I}_{bm}| = 530 \{A\}$$

We can use this value to find what we want.

$$a) P_{abs. by. load} = \frac{|\bar{I}_{bm}|^2 R_{LOAD}}{2} = \frac{(530 \{A\})^2 (15.091 \{\Omega\})}{2}$$

$$P_{abs. by. load} = 2.1195 \{MW\}$$

$$b) Q_{del. by. load} = \frac{-|\bar{I}_{bm}|^2 X_{LOAD}}{2} = \frac{-(530 \{A\})^2 (-50.719 \{\Omega\})}{2}$$

$$Q_{del. by. load} = 7.1235 \{MVAR\}$$

$$c) S_{abs. by. load} = P_{abs. by. load} + j Q_{abs. by. load}$$

$$S_{abs. by. load} = (2.1195 - 7.1235j) \{MVA\}$$

$$d) pf = \cos(-73.43^\circ) = 0.28519 \text{ leading}$$

It is leading because $\angle Z_{LOAD}$ is negative.

$$e) Z_{LINE} = (18 + 15.12j) \{\Omega\}$$

$$Y_{LINE} = \frac{1}{Z_{LINE}} = 42.539 \{mS\} \angle -40.03^\circ$$

$$= (32.572 - 27.361j) \{mS\}, \text{ so}$$

$$B_{LINE} = -27.361 \{mS\}$$

5. (40 points) The circuit shown operates in steady-state. It is given that Load 1 absorbs $(530 \angle -23^\circ) [\text{VA}]$, and

Load 2 absorbs $390 [\text{W}]$, and delivers $250 [\text{VAR}]$.


It is also given that Load 3 can be modeled by a resistor with a value of $27 [\Omega]$ in series with a capacitor with a value of $150 [\mu\text{F}]$.

a) Find $v_B(t)$.


b) Find the voltage across the current source.

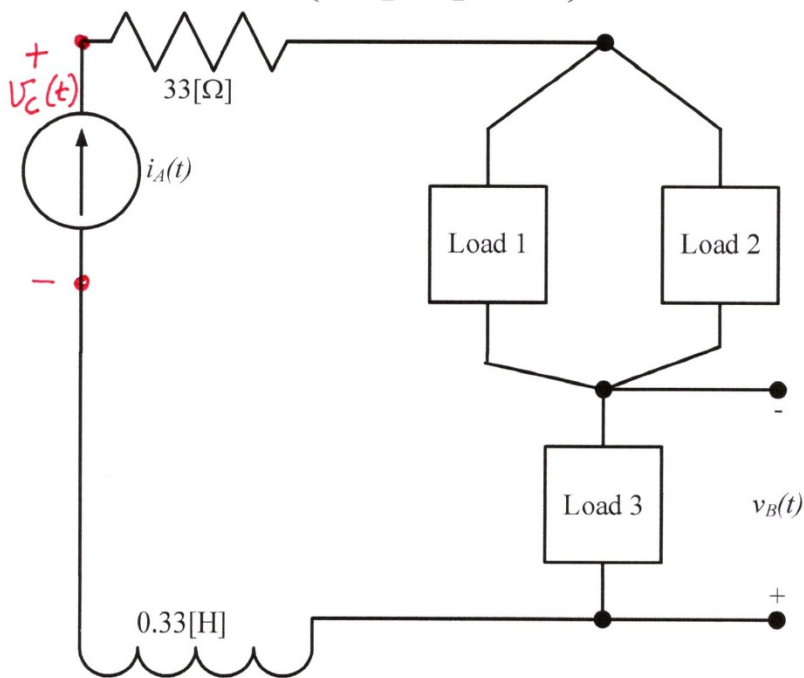c) Find the power factor angle for the combination of the three loads, taken as a single load.

$$i_A(t) = 12.4 [\text{A}] \cos \left(220 \left[\frac{\text{rad}}{\text{s}} \right] t + 75^\circ \right)$$



We redraw in the phasor domain.

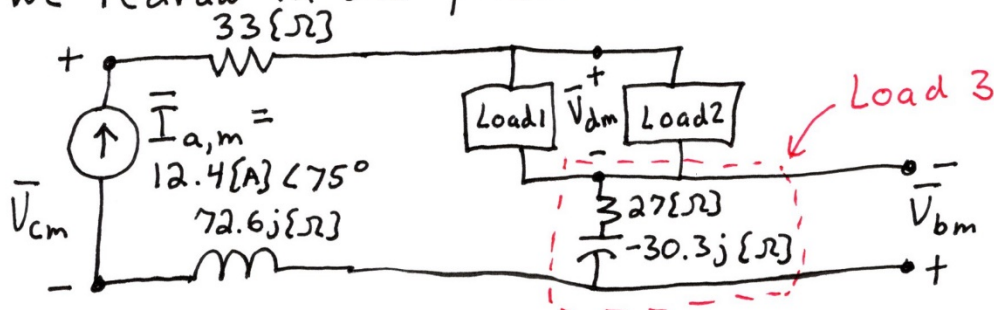

See
next
page

$$\begin{aligned} \text{a) } \bar{V}_{bm} &= - (12.4 \text{ [A]} \angle 75^\circ) (27 - 30.3j) \{\Omega\} \\ &= (503.25 \angle -153.3^\circ) \{V\} \end{aligned}$$

so,

$$v_B(t) = 503.25 \{V\} \cos(220 \{ \frac{\text{rad}}{s} \} t - 153.3^\circ)$$

b) We need the voltage across Load 1 and Load 2.

$$S_{\text{abs. by Load 1}} = (530 \angle -23^\circ) \{VA\}$$

and

$$S_{\text{abs. by Load 2}} = (390 - 250j) \{VA\}.$$

So

$$\begin{aligned} S_{\text{abs. by Loads 1+2}} &= S_{\text{abs. by Load 1}} + S_{\text{abs. by Load 2}} \\ &= (989.74 \angle -27.505^\circ) \{VA\} \end{aligned}$$

$$S_{\text{abs. by Loads 1+2}} = \frac{\bar{V}_{dm} \cdot \bar{I}_{am}^*}{2} = \frac{\bar{V}_{dm} (12.4 \text{ [A]} \angle -75^\circ)}{2}$$

$$\text{so, } \bar{V}_{dm} = \frac{2 (989.74 \angle -27.505^\circ) \{VA\}}{12.4 \text{ [A]} \angle -75^\circ} = 159.64 \{V\} \angle 47.495^\circ$$

KVL

$$\bar{V}_{cm} = \bar{I}_{am} (33 + 72.6j) \{\Omega\} + \bar{V}_{dm} - \bar{V}_{bm} = 993.69 \{V\} \angle 101.98^\circ$$

$$v_C(t) = 993.69 \{V\} \cos(220 \{ \frac{\text{rad}}{s} \} t + 101.98^\circ)$$

see
next
page

Note that we made an arbitrary choice for the polarity of $V_c(t)$. If we had chosen the other polarity, that solution would also have been valid,

$$993.69 \text{ [V]} \cos(220 \left\{ \frac{\text{rad}}{\text{s}} \right\} t - 78.023^\circ)$$

$$\begin{aligned} \text{c) } S_{\text{abs.by.Load 3}} &= \frac{12.4 \text{ [A}^2\text{]}}{2} (27 - 30.3j) \text{ [\Omega]} \\ &= (3.12 \angle -48.296^\circ) \text{ [kVA]} \end{aligned}$$

$$\begin{aligned} S_{\text{abs.by.Loads 1-3}} &= S_{\text{abs.by.Load 3}} + S_{\text{abs.by.Load 1+2}} \\ &= 4.0599 \angle -43.336^\circ \text{ [kVA]} \end{aligned}$$

$$\text{Thus, the power factor angle} = -43.336^\circ$$